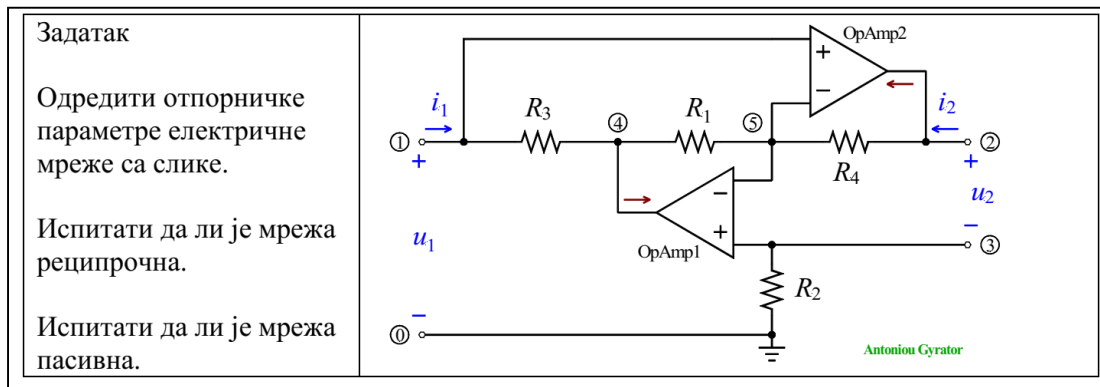


Figure 1:Antoniou Gyrator



```
(%i1) jednacine: [-i1 + (v1-v4)/R3 = 0,
                  -i2 + (v2-v5)/R4 + iopAmp2 = 0, v1-v5 = 0,
                  i2 + v3/R2 = 0,
                  (v4-v1)/R3 + (v4-v5)/R1 + iopAmp1 = 0, v3-v5 = 0,
                  (v5-v4)/R1 + (v5-v2)/R4 = 0];
```

```
(%o1) [ -v1-v4/R3 -i1=0, v2-v5/R4 +iopAmp2-i2=0, v1-v5=0, v3/R2 +
        i2=0, v4-v5/R1 +v4-v1/R3 +iopAmp1=0, v3-v5=0, v5-v4/R1 +v5-v2/R4 =
        0]
```

```
(%i2) promenljive: [v1, v2, v3, v4, v5, iopAmp1, iopAmp2];
```

```
(%o2) [v1, v2, v3, v4, v5, iopAmp1, iopAmp2]
```

```
(%i3) odziv: linsolve(jednacine, promenljive);
```

```
(%o3) [v1=-R2 i2, v2=-R3 R4 i1-R1 R2 i2/R1, v3=-R2 i2, v4=-R2
        i2-R3 i1, v5=-R2 i2, iopAmp1=(R3+R1) i1/R1, iopAmp2=-
        (R3 i1-R1 i2)/R1]
```

```
(%i4) u1: ev(v1, odziv);
```

```
(%o4) -R2 i2
```

```
(%i5) u2: ev(v2-v3, odziv), ratsimp;
```

```
(%o5) R3 R4 i1/R1
```

```
(%i6) r11: u1, [i1 = 1, i2 = 0];
```

```
(%o6) 0
```

```
(%i7) r12: u1, [i1 = 0, i2 = 1];
```

```
(%o7) -R2
```

```
(%i8) r21: u2, [i1 = 1, i2 = 0];
```

```
(%o8) 
$$\frac{R3 R4}{R1}$$

```

```
(%i9) r22: u2, [i1 = 0, i2 = 1];
```

```
(%o9) 0
```

```
(%i10) is(r12 = r21);
```

```
(%o10) false
```

```
(%i11) r: matrix([r11, r12], [r21, r22]);
```

```
(%o11) 
$$\begin{pmatrix} 0 & -R2 \\ \frac{R3 R4}{R1} & 0 \end{pmatrix}$$

```

```
(%i12) assume(R1>0, R2>0, R3>0, R4>0);
```

```
(%o12) [R1>0, R2>0, R3>0, R4>0]
```

```
(%i13) Dis: (r12+r21)^2 - 4*r11*r22;
```

```
(%o13) 
$$\left(\frac{R3 R4}{R1} - R2\right)^2$$

```

```
(%i14) is(r11 >= 0 and r22 >= 0 and Dis <= 0);
```

```
(%o14) unknown
```

```
(%i15) assume(notequal(R3*R4/R1, R2));
```

```
(%o15) [notequal( $\frac{R3 R4}{R1}$ , R2)]
```

```
(%i16) is(r11 >= 0 and r22 >= 0 and Dis <= 0);
```

```
(%o16) false
```