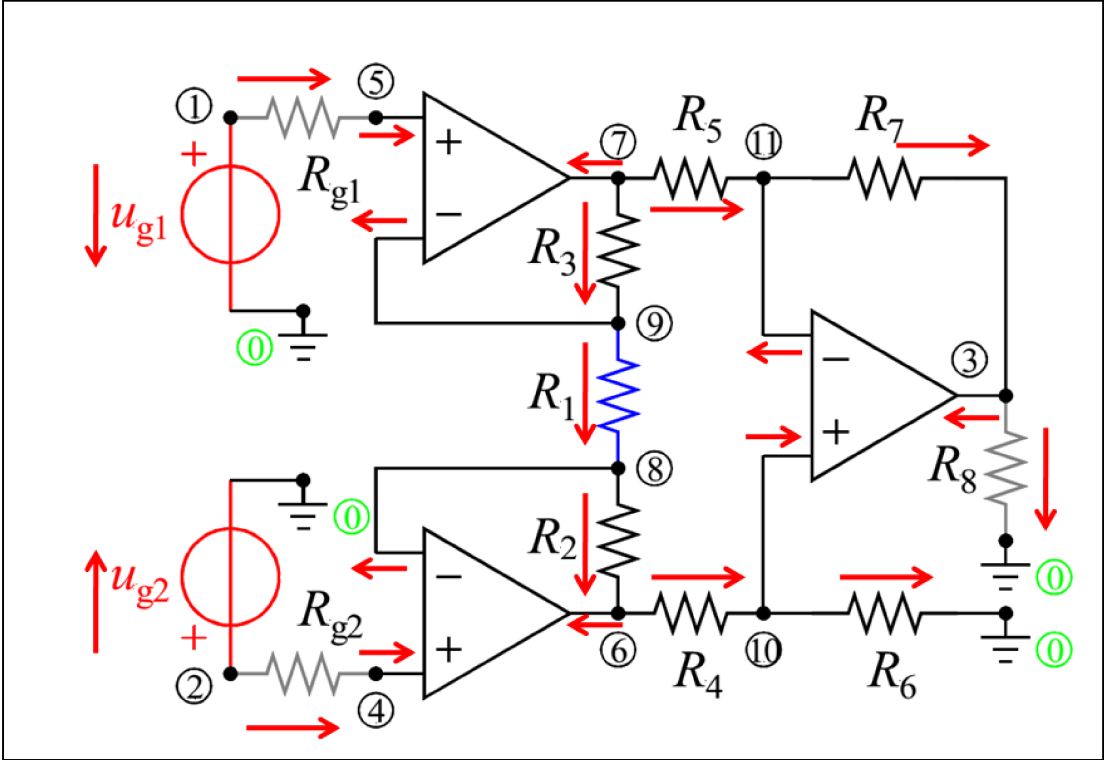


Figure 1:Инструментациони појачавач



```

(%i1) jednacine: [jg1 + (v1-v5)/Rg1 = 0,
                  v1 = ug1,
                  jg2 + (v2-v4)/Rg2 = 0,
                  v2 = ug2,
                  j3 + v3/R8 - (v11-v3)/R7 = 0,
                  -(v2-v4)/Rg2 + iul2 = 0,
                  -(v1-v5)/Rg1 + iul1 = 0,
                  j2 + (v6-v10)/R4 - (v8-v6)/R2 = 0,
                  j1 + (v7-v11)/R5 + (v7-v9)/R3 = 0,
                  -iul2 - (v9-v8)/R1 + (v8-v6)/R2 = 0,
                  -iul1 - (v7-v9)/R3 + (v9-v8)/R1 = 0,
                  -(v6-v10)/R4 + v10/R6 + iul3 = 0,
                  -(v7-v11)/R5 + (v11-v3)/R7 - iul3 = 0,
                  iul1 = 0,
                  iul2 = 0,
                  iul3 = 0,
                  v5 = v9,
                  v4 = v8,
                  v10 = v11];

(%o1) [ $\frac{v1-v5}{Rg1} + jg1 = 0, v1 = ug1, \frac{v2-v4}{Rg2} + jg2 = 0, v2 = ug2,$ 
 $\frac{v3-v11}{R7} + \frac{v3}{R8} + j3 = 0, \frac{v4-v2}{Rg2} + iul2 = 0, \frac{v5-v1}{Rg1} + iul1 = 0, \frac{v6-v8}{R2}$ 
 $+ \frac{v6-v10}{R4} + j2 = 0, \frac{v7-v9}{R3} + \frac{v7-v11}{R5} + j1 = 0, -\frac{v9-v8}{R1} + \frac{v8-v6}{R2} -$ 
 $iul2 = 0, \frac{v9-v8}{R1} - \frac{v7-v9}{R3} - iul1 = 0, \frac{v10-v6}{R4} + \frac{v10}{R6} + iul3 = 0,$ 
 $\frac{v11-v7}{R5} + \frac{v11-v3}{R7} - iul3 = 0, iul1 = 0, iul2 = 0, iul3 = 0, v5 = v9,$ 
 $v4 = v8, v10 = v11]$ 

(%i2) promenljive: [v1, v2, v3, v4, v5, v6, v7, v8, v9, v10, v11,
                    j1, j2, j3, iul1, iul2, iul3, jg1, jg2];

(%o2) [v1, v2, v3, v4, v5, v6, v7, v8, v9, v10, v11, j1, j2, j3,
        iul1, iul2, iul3, jg1, jg2]

```

```
(%i3) odziv: linsolve(jednachine, promenljive);
(%o3) [v1=ug1, v2=ug2, v3=- (
( (-R3 R6-R2 R6-R1 R6-R3 R4) R7-R2 R5 R6-R1 R5 R6) ug2 +
( (R3 R6+R2 R6+R1 R6+(R3+R1) R4) R7+R2 R5 R6) ug1) /
(R1 R5 R6+R1 R4 R5), v4=ug2, v5=ug1, v6=-
(-R2-R1) ug2+R2 ug1
R1, v7=- (R3+R1) ug1-R3 ug2
R1, v8=ug2, v9=
ug1, v10=- (-R2 R6-R1 R6) ug2+R2 R6 ug1
R1 R6+R1 R4, v11=-
(-R2 R6-R1 R6) ug2+R2 R6 ug1
R1 R6+R1 R4, j1=- (
(-R5 R6-R3 R6-R2 R6-R1 R6+R4 (-R5-R3)) ug2 +
(R5 R6+R3 R6+R2 R6+R1 R6+R4 (R5+R3+R1)) ug1) /
(R1 R5 R6+R1 R4 R5), j2=- (-R6-R4-R2-R1) ug2+(R6+R4+R2) ug1
R1 R6+R1 R4
, j3= ( (-R3 R6-R2 R6-R1 R6-R3 R4) R8 +
(-R3 R6-R2 R6-R1 R6-R3 R4) R7-R2 R5 R6-R1 R5 R6) ug2 + (
(R3 R6+R2 R6+R1 R6+(R3+R1) R4) R8 +
(R3 R6+R2 R6+R1 R6+(R3+R1) R4) R7+R2 R5 R6) ug1) /
((R1 R5 R6+R1 R4 R5) R8), iul1=0, iul2=0, iul3=0, jg1=0,
jg2=0]
```

```
(%i4) ev(v3, odziv);
```

```
(%o4) - ( (-R3 R6-R2 R6-R1 R6-R3 R4) R7-R2 R5 R6-R1 R5 R6)
ug2 + ( (R3 R6+R2 R6+R1 R6+(R3+R1) R4) R7+R2 R5 R6) ug1) /
(R1 R5 R6+R1 R4 R5)
```

```
(%i5) zamena: [R2 = R, R3 = R, R4 = R, R5 = R, R6 = R, R7 = R];
```

```
(%o5) [R2=R, R3=R, R4=R, R5=R, R6=R, R7=R]
```

```
(%i6) v3_zamena: ev(v3, odziv), zamena;
```

```
(%o6) -
((R (-R R1-3 R^2) -R^2 R1-R^3) ug2 + (R (R (R1+R) +R R1+2 R^2) +R^3) ug1)
/ (2 R^2 R1)
```

```
(%i7) ratsimp(%);
```

```
(%o7) (R1+2 R) ug2 + (-R1-2 R) ug1
R1
```

```
(%i8) pobude: [ug1 = U*unit_step(t), ug2 = U*unit_step(t-T)],  
              [U = 10, T = 1];  
(%o8) [ug1=10 unit_step(t), ug2=10 unit_step(t-1)]  
  
(%i9) ratsimp(%o7), pobude, [R = 1000, R1 = 2000];  
(%o9) 20 unit_step(t-1)-20 unit_step(t)  
  
(%i10) wxplot2d([%o9], [t,-1,5], [y,-30,40])$
```

(%t10)

