
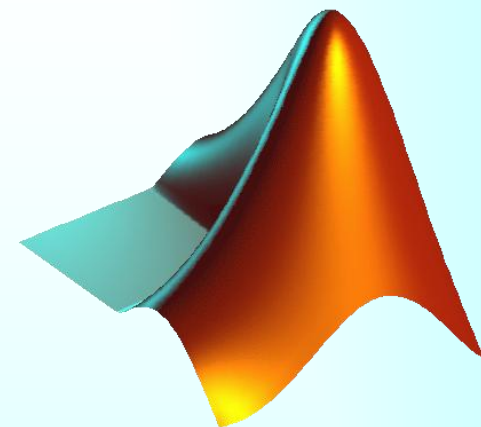



Računarska analiza električnih kola

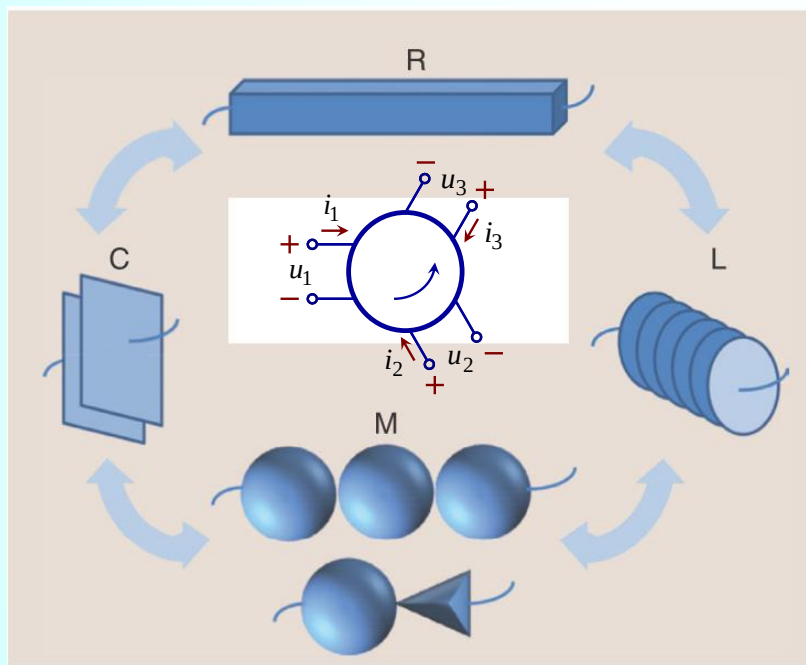

Milka Potrebić

Računarski (softverski) alati

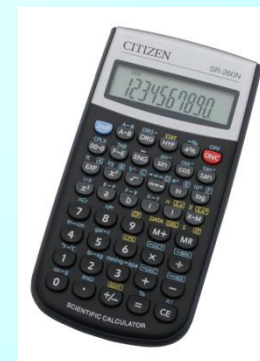
- *Mathematica*, MuPAD, Maxima, SymPy
- MATLAB, Scilab, Octave, FreeMat
- LTspice, ngspice, QucsStudio, XCircuit
- Python, MathCAD, MAPLE, SpeQ Mathematics...



Free/Libre Open Source Software (FLOSS)

Pratilac napona

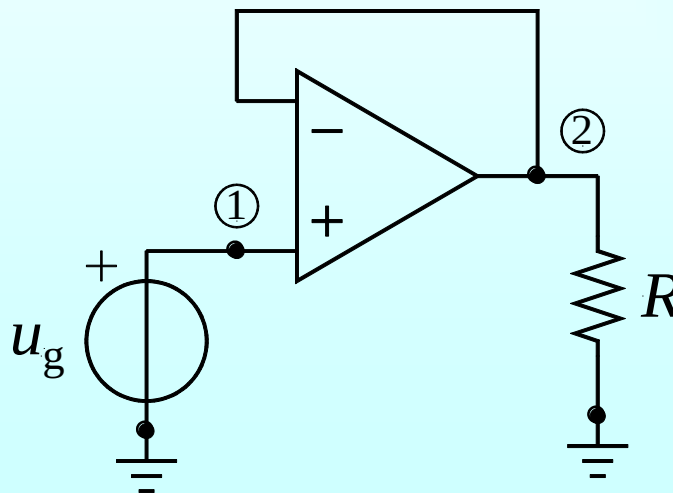Odrediti naponsko pojačanje kola sa slike, koje se naziva pratilac napona (voltage follower).



SymPy Live

Symbolic Python Live, <http://live.sympy.org/>

SymPy Live

Python console for SymPy 0.7.1 (Python 2.5.2)

These commands were executed:

```
>>> from __future__ import division
>>> from sympy import *
>>> x, y, z, t = symbols('x y z t')
>>> k, m, n = symbols('k m n', integer=True)
>>> f, g, h = symbols('f g h', cls=Function)
```

Documentation can be found at <http://docs.sympy.org/>.

```
>>> # Pratilac napona (voltage follower)
... var('iug, iR, i1OP, i2OP, ug, uR, u1OP, u2OP, R')
... jednacine = [
...   Eq(iug + i1OP, 0), Eq(i2OP - i1OP + iR, 0),
...   Eq(ug - u1OP - u2OP, 0), Eq(u2OP - uR, 0),
...   Eq(u1OP, 0), Eq(i1OP, 0), Eq(uR - R*iR, 0)
... ]
... promenljive = [
...   iug, iR, i1OP, i2OP, uR, u1OP, u2OP
... ]
>>> odziv = solve(jednacine, promenljive)
>>> odziv
```

$$\left\{ i1OP: 0, i2OP: -\frac{ug}{R}, iR: \frac{ug}{R}, iug: 0, u1OP: 0, u2OP: ug, uR: ug \right\}$$

```
>>> pojacanje = (uR/ug).subs(odziv)
>>> pojacanje
```

1

>>> |

▼ < >

Evaluate

Clear

Fullscreen

SymPy Live

Python console for SymPy 0.7.1 (Python 2.5.2)

These commands were executed:

```
>>> from __future__ import division
>>> from sympy import *
>>> x, y, z, t = symbols('x y z t')
>>> k, m, n = symbols('k m n', integer=True)
>>> f, g, h = symbols('f g h', cls=Function)
```


Documentation can be found at <http://docs.sympy.org/>.

```
>>> # Pratilac napona (voltage follower)
... var('iug, iR, i1OP, i2OP, ug, uR, u1OP, u2OP, R')
... jednacine = [
... Eq(iug + i1OP, 0), Eq(i2OP - i1OP + iR, 0),
... Eq(ug - u1OP - u2OP, 0), Eq(u2OP - uR, 0),
... Eq(u1OP, 0), Eq(i1OP, 0), Eq(uR - R*iR, 0)
... ]
... promenljive = [
... iug, iR, i1OP, i2OP, uR, u1OP, u2OP
... ]
>>> odz = solve(jednacine, promenljive)
>>> odz
```

$$\left\{ i1OP : 0, \quad i2OP : -\frac{ug}{R}, \quad iR : \frac{ug}{R}, \quad iug : 0, \quad u1OP : 0, \quad u2OP : ug, \quad uR : ug \right\}$$

```
>>> pojacanje = (uR/ug).subs(odz)
>>> pojacanje
```



1

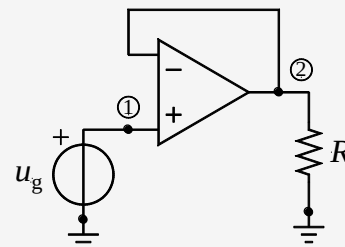

```
D:\eKolaVbirka\lati3\Pratilac\PratilacNapona.py - Notepad++
File Edit Search View Encoding Language Settings Macro Run Plugins Window ?
PratilacNapona.py
1 # Pratilac napona (voltage follower)
2 var('iug, iR, i1OP, i2OP, ug, uR, u1OP, u2OP, R')
3 jednacine = [
4 Eq(iug + i1OP, 0), Eq(i2OP - i1OP + iR, 0),
5 Eq(ug - u1OP - u2OP, 0), Eq(u2OP - uR, 0),
6 Eq(u1OP, 0), Eq(i1OP, 0), Eq(uR - R*iR, 0)
7 ]
8 promenljive = [
9 iug, iR, i1OP, i2OP, uR, u1OP, u2OP
10 ]
11 odziv = solve(jednacine, promenljive)
12 pojacanje = (uR/ug).subs(odziv)
```

Notepad++, <http://notepad-plus-plus.org/>


MATLAB: Symbolic Math Toolbox

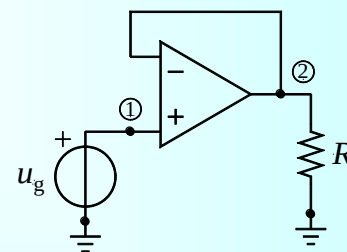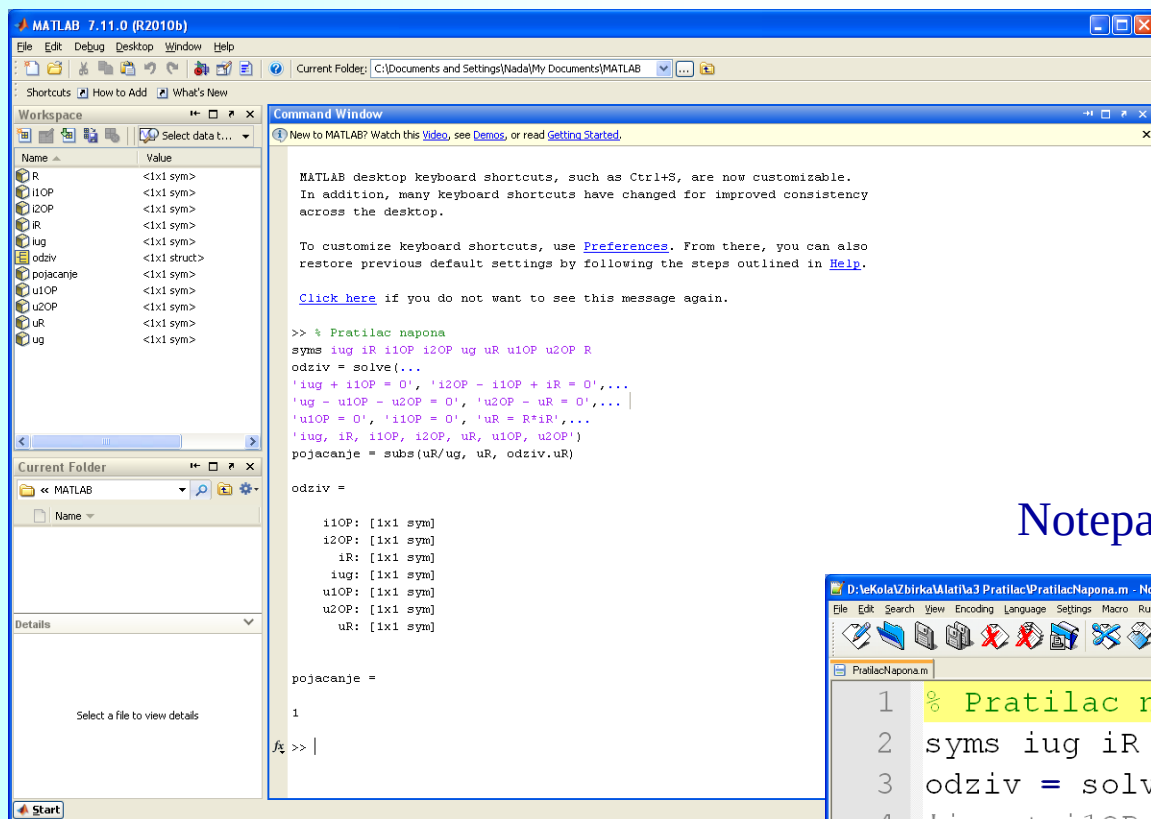

Notepad++, <http://notepad-plus-plus.org/>

```
pojacanje =

1
```

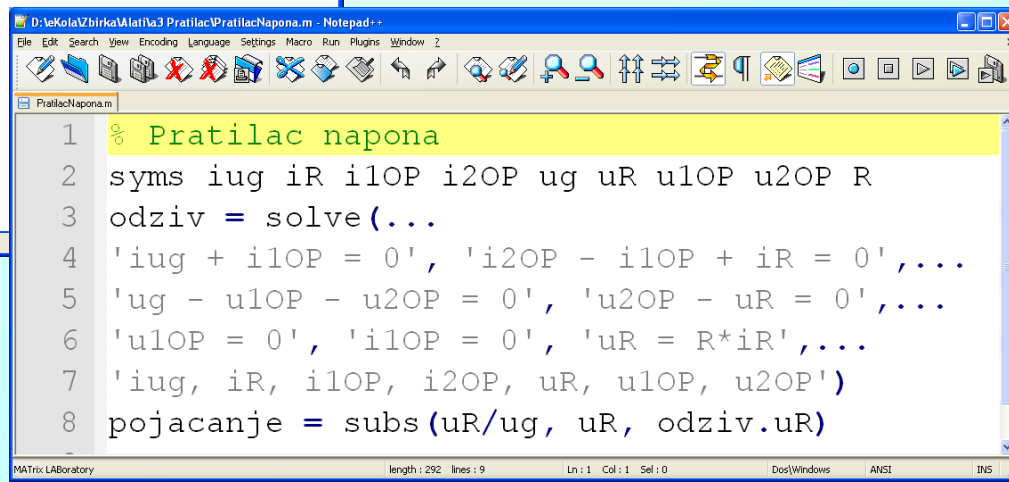

MATLAB: MuPAD

```
Pratilač napona (voltage follower)
[// Pratilač napona

jednacine := {iug + i1OP = 0, i2OP - i1OP + iR = 0,
ug - u1OP - u2OP = 0, u2OP - uR = 0, u1OP = 0, i1OP = 0, uR = R*iR}

{u2OP - uR = 0, i2OP - i1OP + iR = 0, i1OP + iug = 0, i1OP = 0, u1OP = 0, ug - u2OP - u1OP = 0, uR = R*iR}

assume(R>0)


promenljive := {iug, iR, i1OP, i2OP, uR, u1OP, u2OP}

{i1OP, i2OP, iR, iug, u1OP, u2OP, uR}

odziv := solve(jednacine, promenljive)

{[i1OP = 0, i2OP = -ug/R, iR = ug/R, iug = 0, u1OP = 0, u2OP = ug, uR = ug]}

pojacanje := uR/ug | odziv
1
```

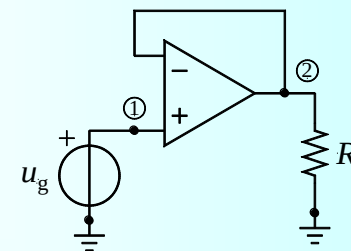

```
jednacine := {iug + i1OP = 0, i2OP - i1OP + iR = 0,
ug - u1OP - u2OP = 0, u2OP - uR = 0, u1OP = 0, i1OP = 0, uR = R*iR}

{u2OP - uR = 0, i2OP - i1OP + iR = 0, i1OP + iug = 0, i1OP = 0, u1OP = 0, ug - u2OP - u1OP = 0, uR = R*iR}
```

```
assume(R>0)

promenljive := {iug, iR, i1OP, i2OP, uR, u1OP, u2OP}

{i1OP, i2OP, iR, iug, u1OP, u2OP, uR}

odziv := solve(jednacine, promenljive)

{[i1OP = 0, i2OP = -ug/R, iR = ug/R, iug = 0, u1OP = 0, u2OP = ug, uR = ug]}
```

```
pojacanje := uR/ug | odziv
1
```

Maxima

Maxima, <http://maxima.sourceforge.net/>


wxMaxima, <http://andrejv.github.com/wxmaxima/index.html>

wxMaxima 12.01.0 [PratilacNapona.wmx]

File Edit Cell Maxima Equations Algebra Calculus Simplify Plot Numeric Help

Pratilac napona (voltage follower)

Figure 1:

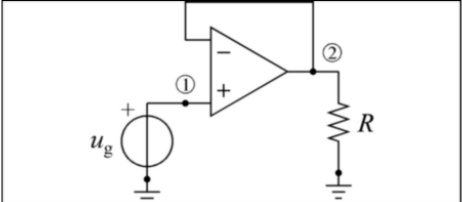

```
(%i1) jednacine: [iug + i1OP = 0, i2OP - i1OP + iR = 0,
ug - u1OP - u2OP = 0, u2OP - uR = 0,
u1OP = 0, i1OP = 0, uR = R*iR];

(%o1) [i1OP+iug=0,iR+i2OP-i1OP=0,-u2OP-u1OP+ug=0,u2OP-uR
=0,u1OP=0,i1OP=0,uR=iRR]

(%i2) odziv: linsolve(jednacine,
[iug, iR, i1OP, i2OP, uR, u1OP, u2OP]);

(%o2) [iug=0,iR=ug/R,i1OP=0,i2OP=-ug/R,uR=ug,u1OP=0,u2OP=ug]


(%i3) pojacanje: uR/ug, odziv;

(%o3) 1
```

Ready for user input





MATLAB: Simscape

Foundation Library, Utilities, Simulink

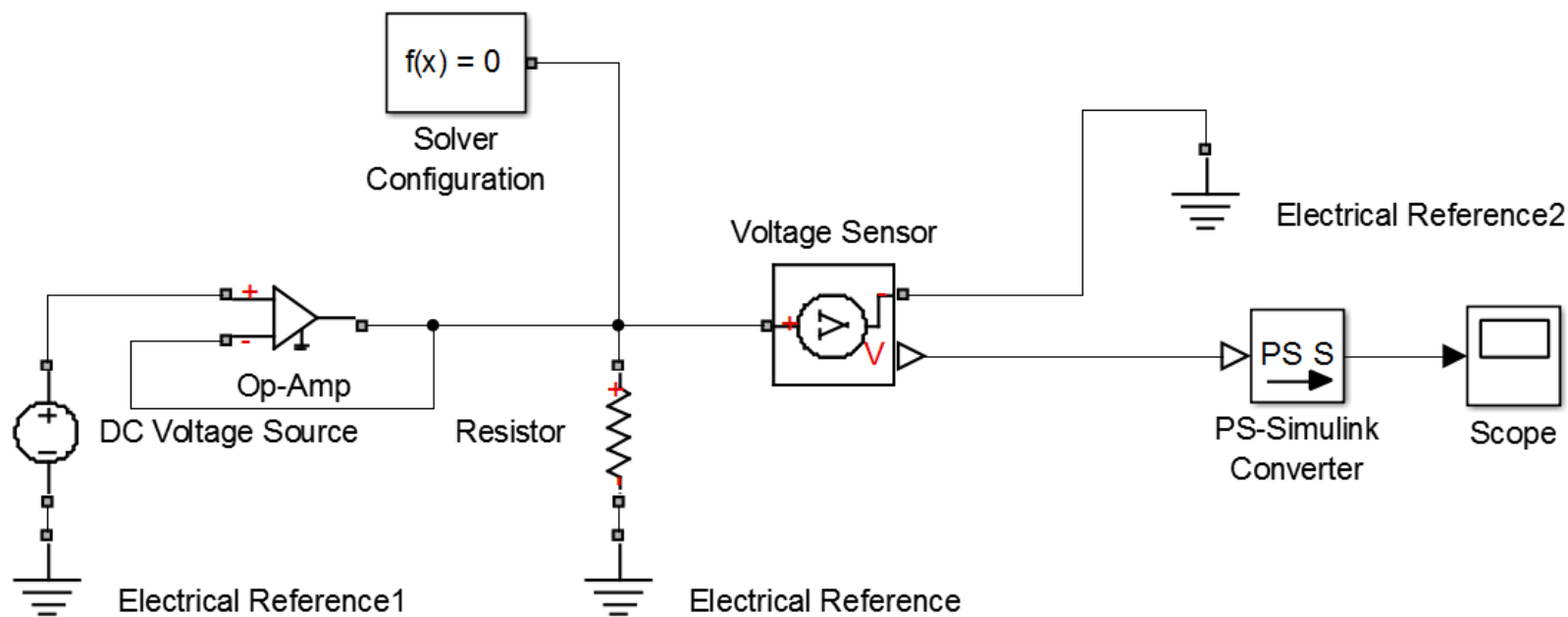


MATLAB: Simscape

Foundation Library, Utilities, Simulink

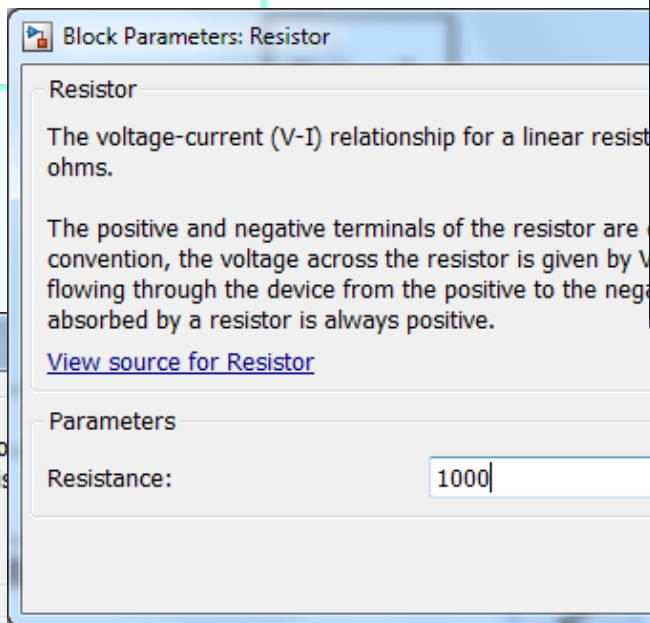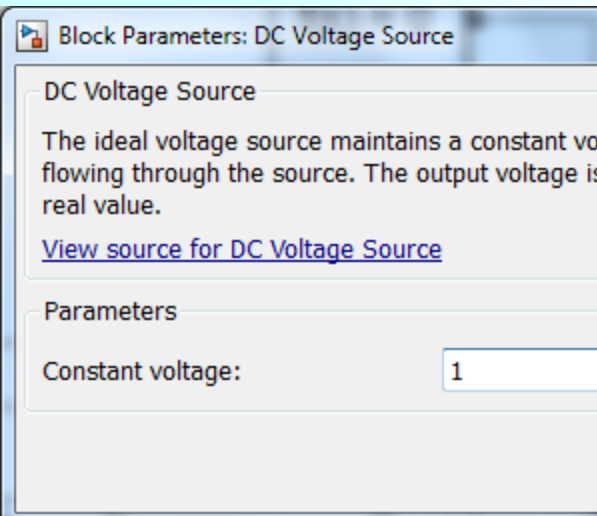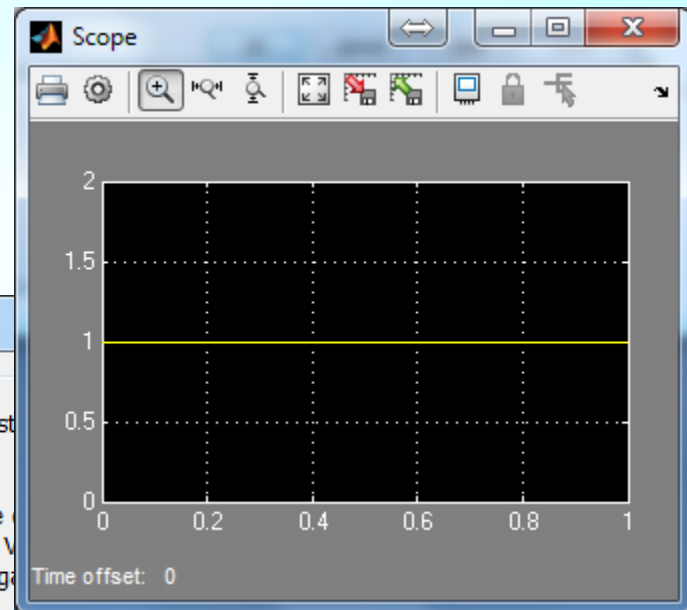
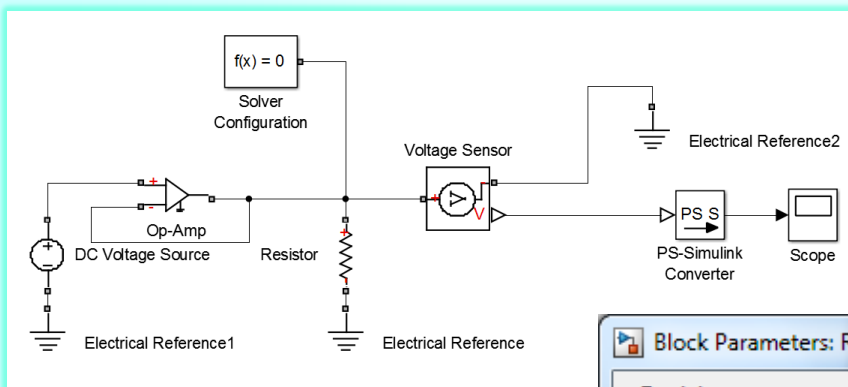


MATLAB: Simscape

Electronics, Utilities, Simulink

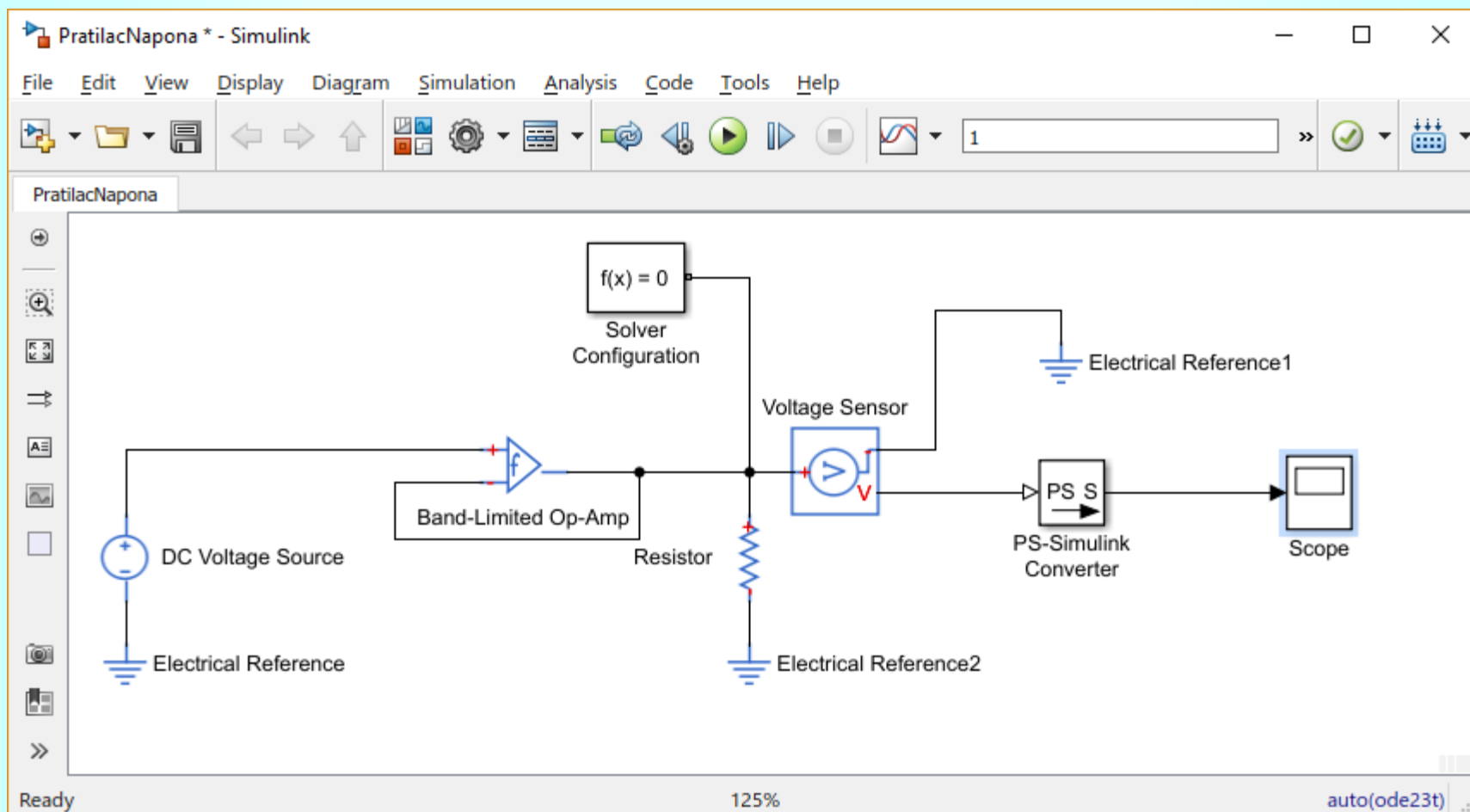

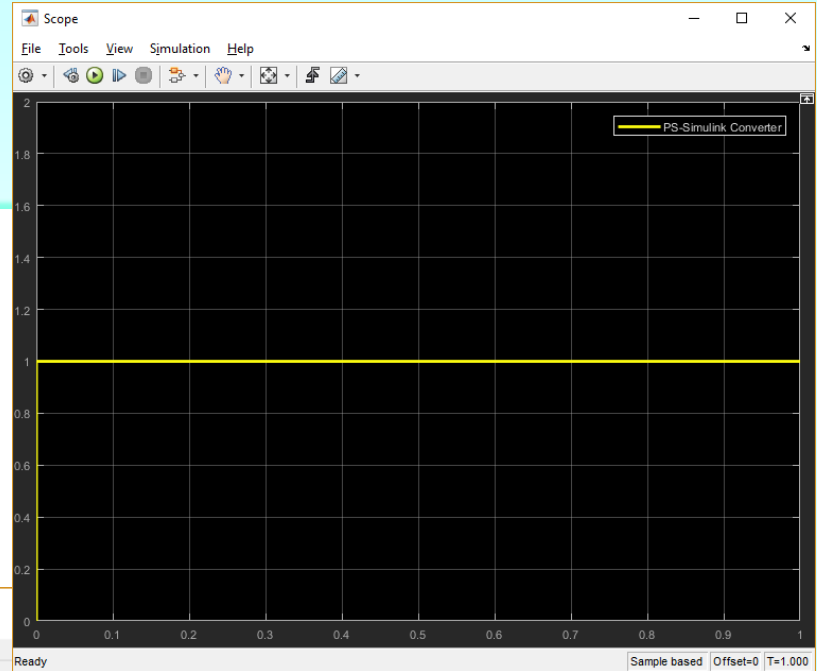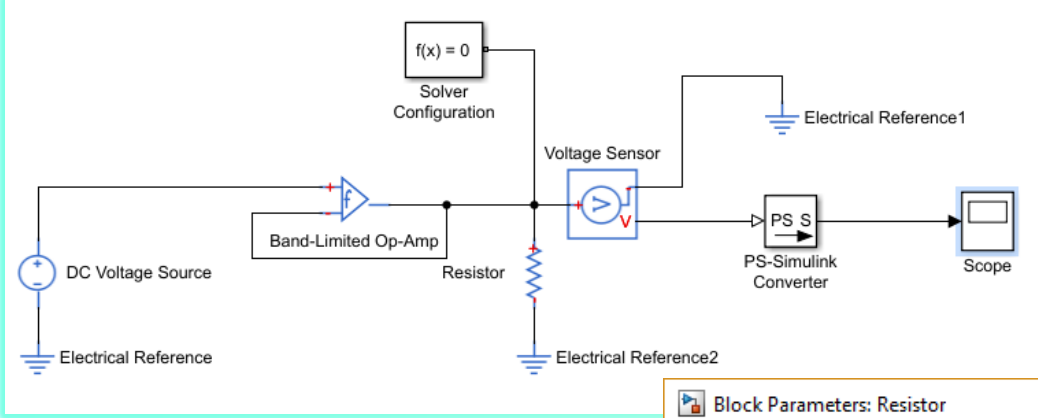MATLAB: Simscape Electronics, Utilities, Simulink



Block Parameters: Resistor

Resistor

This block models a resistor with optional tolerance, operational limits, fault and thermal noise modeling. To model temperature effects, select the thermal variant of this block by right-clicking on the block and selecting Simscape block choices and Show thermal port.

Settings

Main Operating Limits Faults Noise

Resistance: 1 kOhm

Tolerance (%): 5

Tolerance application: None - use nominal value

OK Cancel Help Apply

Block Parameters: DC Voltage Source

DC Voltage Source

The ideal voltage source maintains a constant voltage across its flowing through the source. The output voltage is defined by the real value.

[Source code](#)

Settings

Parameters

Constant voltage: 1 V

OK Cancel Help Apply

Operational Amplifier LM7301




LM7301

SNOS879I – AUGUST 1999 – REVISED MAY 2016

LM7301 Low Power, 4-MHz GBW, Rail-to-Rail Input-Output Operational Amplifier in SOT-23 Package

1 Features

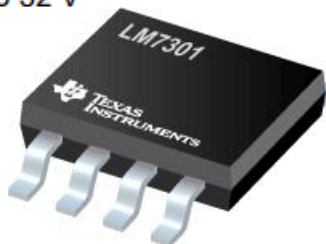- At $V_S = 5\text{ V}$ (Typical Unless Otherwise Noted)
- Tiny, Space-Saving, 5-Pin SOT-23 Package
- Greater than Rail-to-Rail Input CMVR: -0.25 V to 5.2 V
- Rail-to-Rail Output Swing: 0.07 V to 4.93 V
- Wide Gain-Bandwidth: 4 MHz
- Low Supply Current: 0.6 mA
- Wide Supply Range: 1.8 V to 32 V
- High PSRR: 104 dB
- High CMRR: 93 dB
- Excellent Gain: 97 dB



2 Applications

- Portable Instrumentation
- Signal Conditioning Amplifiers/ADC Buffers
- Active Filters
- Modems
- PCMCIA Cards

3 Description

The LM7301 provides high performance in a wide range of applications. The LM7301 offers greater than rail-to-rail input range, full rail-to-rail output swing, large capacitive load driving ability, and low distortion.

With only 0.6-mA supply current, the 4-MHz gain-bandwidth of this device supports new portable applications where higher power devices unacceptably drain battery life.

The LM7301 can be driven by voltages that exceed both power supply rails, thus eliminating concerns over exceeding the common-mode voltage range. The rail-to-rail output swing capability provides the maximum possible dynamic range at the output. This is particularly important when operating on low supply voltages.



Operating on supplies of 1.8 V to 32 V , the LM7301 is excellent for a very wide range of applications in low power systems.

Placing the amplifier right at the signal source reduces board size and simplifies signal routing. The LM7301 fits easily on low profile PCMCIA cards.

9 Power Supply Recommendations

The LM7301 is specified for operation from 1.8 V to 32 V ($\pm 0.9\text{ V}$ to $\pm 16\text{ V}$). Being a rail-to-rail input and output device, any operating voltage conditions within the supply voltage range can be accommodated.

Op-Amp LM7301

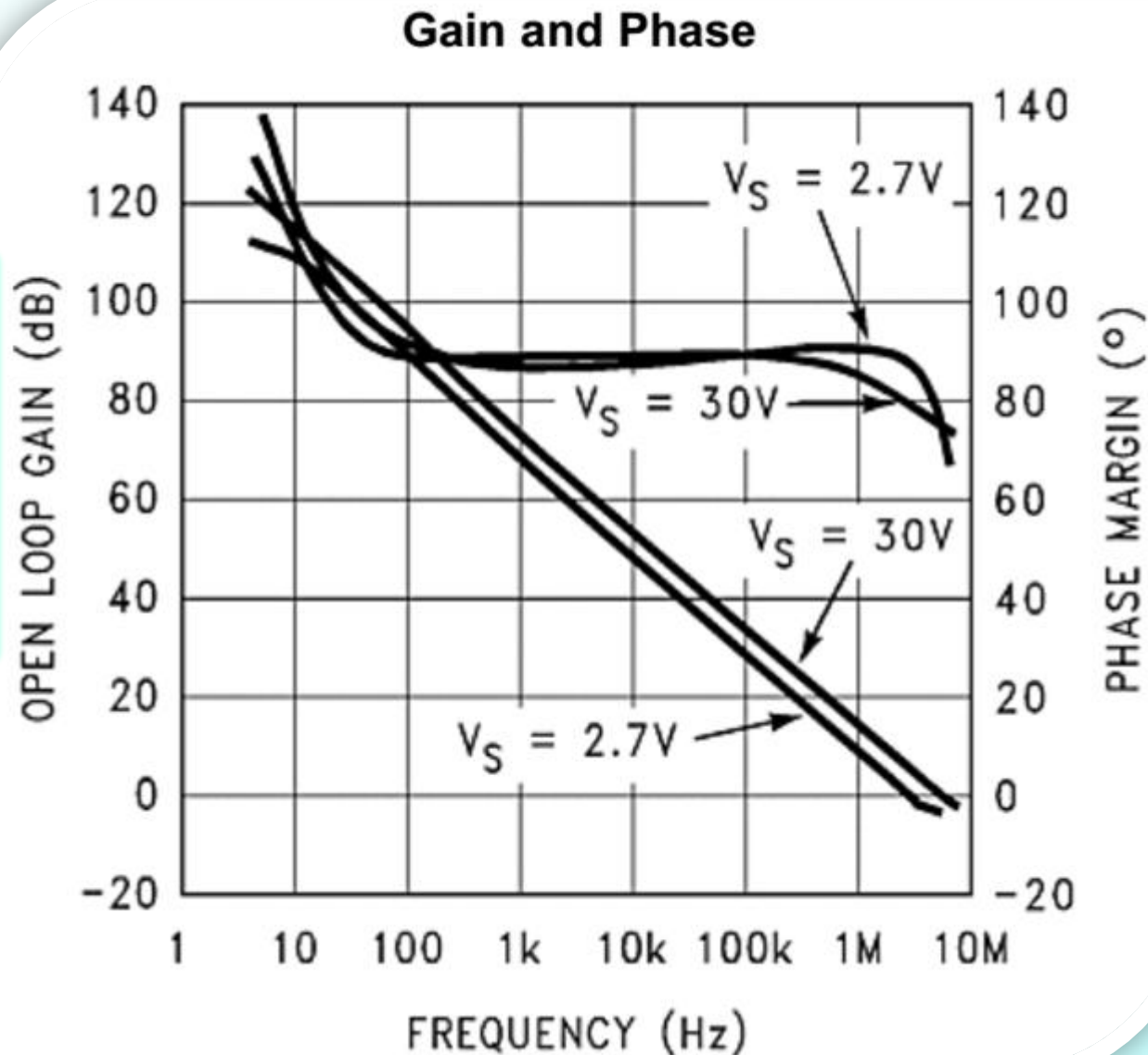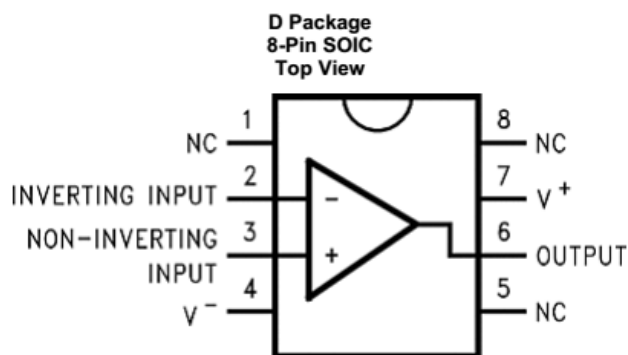

Parametrizacija realnog operacionog pojačavača na osnovu dokumentacije proizvođača

The screenshot shows the MathWorks documentation website. The browser address bar displays the URL: <https://www.mathworks.com/help/physmod/elec/ug/parameterize-an-op-amp-from-a-datasheet.html>. The page header includes the MathWorks logo and a search bar labeled 'Search R2017b Documentation'. A left sidebar contains a 'CONTENTS' menu with links to 'Documentation Home', 'Simscape Electronics', and 'Integrated Circuits'. The main content area is titled 'Parameterize an Op-Amp from a Datasheet' and includes a brief description of the 'Triangle Wave Generator' example model, which uses an LM7301 op-amp. A table lists the device's specifications: Gain (97dB = 7.1e4), Input resistance (39MΩ), Slew rate (1.25V/μs), and Bandwidth (4MHz). The text below the table explains that the Band-Limited Op-Amp and Finite-Gain Op-Amp blocks are designed for use with manufacturer datasheets, while detailed SPICE models are not recommended for accuracy and simulation speed.

MathWorks®

Documentation

Search R2017b Documentation

Documentation

CONTENTS Close

- < Documentation Home
- < Simscape Electronics
- < Integrated Circuits

Parameterize an Op-Amp from a Datasheet

Parameterize an Op-Amp from a Datasheet R2017b

The [Triangle Wave Generator](#) example model, also described in [Triangle Wave Generator Model](#), contains two op-amps, parameterized based on a datasheet for an LM7301. The National Semiconductor datasheet gives the following data for this device:

Gain	97dB = 7.1e4
Input resistance	39MΩ
Slew rate	1.25V/μs
Bandwidth	4MHz

The Band-Limited Op-Amp and Finite-Gain Op-Amp blocks have been designed to work from manufacturer datasheets. Implementing detailed op-amp device models, derived from manufacturer SPICE netlist models, is not recommended, because it provides more accuracy than is typically warranted and slows down simulations. The simple parameterization of the Simscape™ Electronics™ op-amp blocks allows you to determine the sensitivity of your circuit to abstracted performance values,

Block Parameters: Band-Limited Op-Amp

Band-Limited Op-Amp

This block models a band-limited op-amp. If the voltages at the positive and negative pins are denoted V_p and V_m , then the output voltage is given by

$$V_{out} = A \cdot (V_p - V_m) \cdot \frac{1}{(s / (2 \cdot \pi \cdot f) + 1) - I_{out} \cdot R_{out}}$$

where A is the gain, R_{out} is the output resistance, I_{out} is the output current, s is the Laplace operator, and f is the 3dB bandwidth. The input current is given by $(V_p - V_m) / R_{in}$ where R_{in} is the input resistance. The no-load output voltage is limited the range V_{min} to V_{max} , and the slew rate is limited to $\pm V_{dot}$.

The Initial output voltage, V_0 , sets the initial op-amp output voltage. Note that this does not take account of any voltage drop across R_{out} . The initial condition is not used if you select the Start simulation from steady state option in the Solver Configuration block.

Settings

Parameters

Gain, A :	7.1e4	
Input resistance, R_{in} :	39	MOhm
Output resistance, R_{out} :	0	Ohm
Minimum output, V_{min} :	-20	V
Maximum output, V_{max} :	20	V
Maximum slew rate, V_{dot} :	1.25/1e-6	V/s
Bandwidth, f :	4e6	Hz
Initial output voltage, V_0 :	0	V

OK

Cancel

Help

Apply



Third-Party Products & Services ▼

Search Third-Party P


Cadence PSpice Systems Option

Cadence® PSpice® integrated with MATLAB and Simulink to provide a complete system-level simulation solution for PCB design and implementation

Highlights

- Co-simulate Simulink and PSpice together for complete system simulation
- View PSpice simulation results in MATLAB
- Use MATLAB functions directly in measurement expressions within PSpice
- Export behavioral models from Simulink to PSpice using Cadence's Device

Integracija PSpice & Simulink

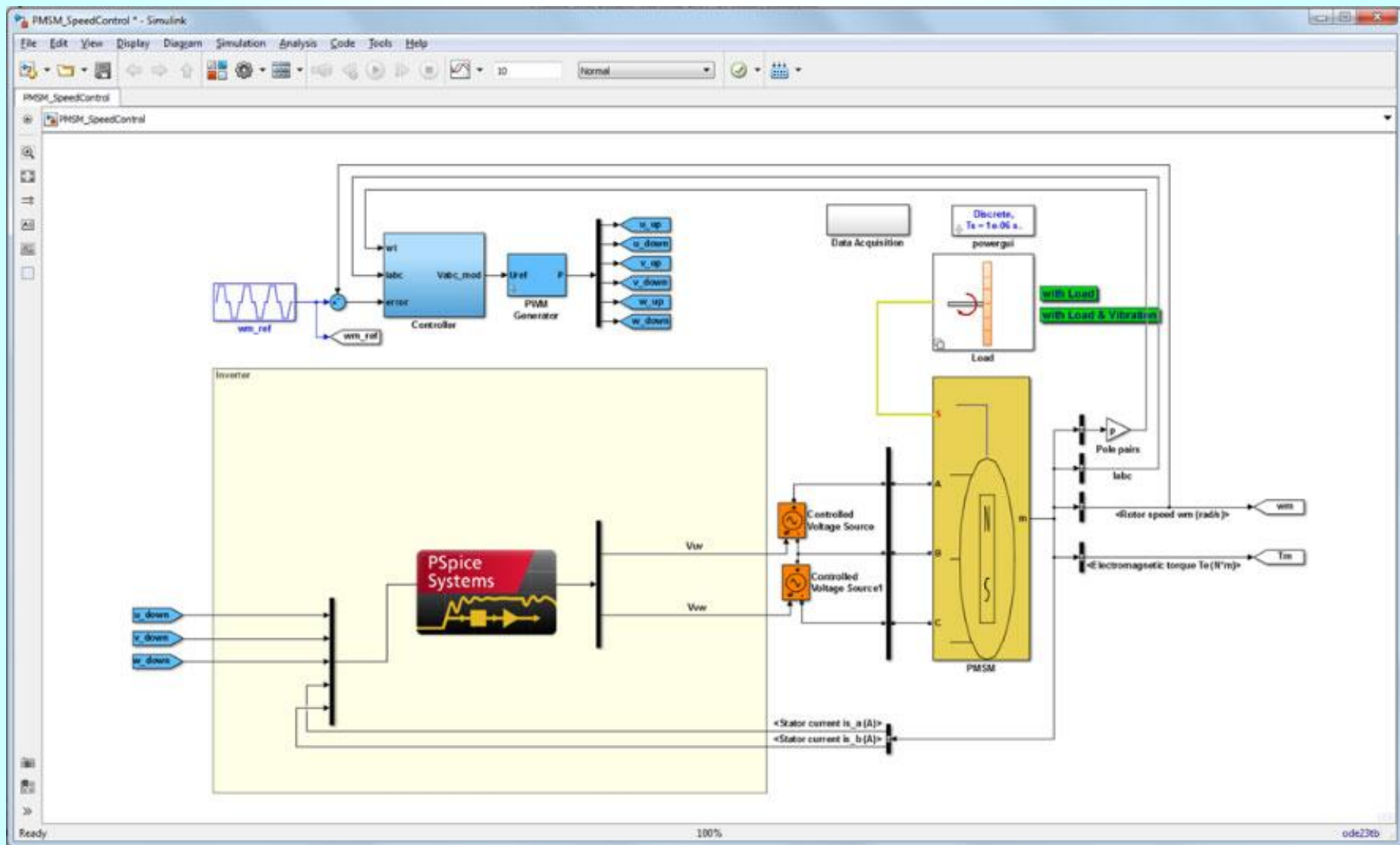

Instrumentacioni pojačavač

- Odrediti napon v_3 otpornika R_8 ?
- Nacrtati grafik napona v_3 otpornika R_8 u funkciji vremena?
- Kolika je snaga izvora?


Vrednosti elemenata su poznate.


$$R_2 = R_3 = R_4 = R_5 = R_6 = R_7 = R_8 = R$$

$$R = 1 \text{ k}\Omega, R_1 = 2 \text{ k}\Omega, R_{g1} = R_{g2} = 1 \text{ k}\Omega$$

$$u_{g1}(t) = U h(t), u_{g2}(t) = U h(t-T)$$

$$U = 10 \text{ V}, T = 1 \text{ s}$$

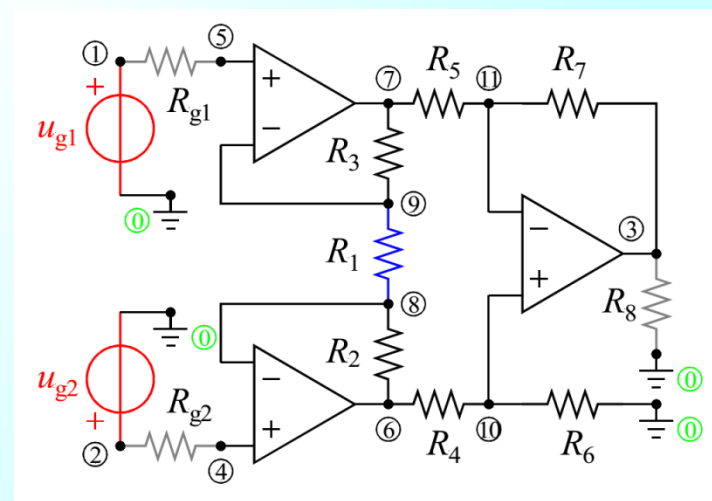

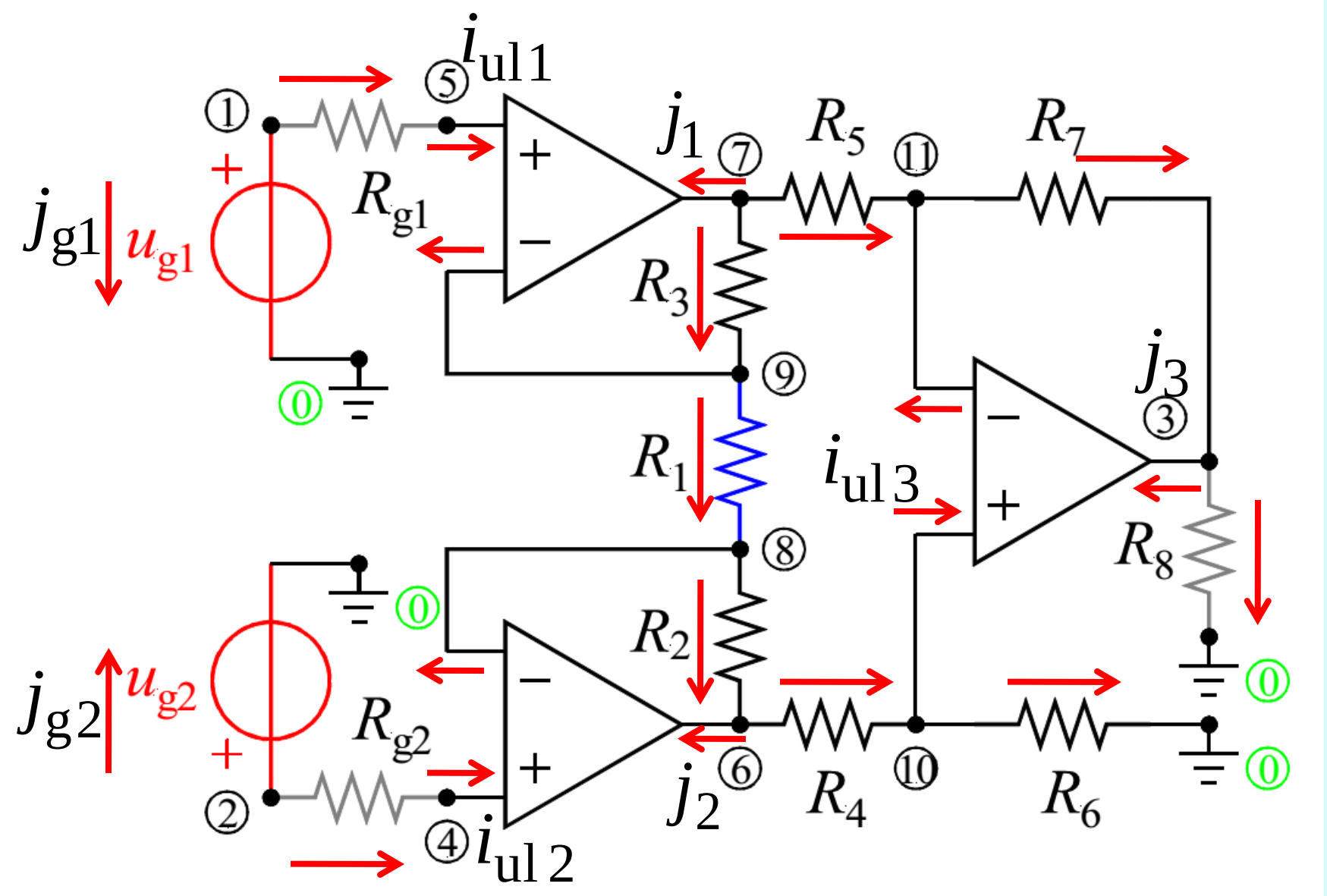

Modifikovana metoda potencijala čvorova

$$(1) j_{g1} + (V_1 - V_5)/R_{g1} = 0$$

$$(2) j_{g2} + (V_2 - V_4)/R_{g2} = 0$$

$$(3) j_3 - (V_{11} - V_3)/R_7 + V_3/R_8 = 0$$

$$(4) -(V_2 - V_4)/R_{g2} + i_{ul2} = 0$$

$$(5) -(V_1 - V_5)/R_{g1} + i_{ul1} = 0$$

$$(6) j_2 + (V_6 - V_{10})/R_4 - (V_8 - V_6)/R_2 = 0$$


$$(7) j_1 + (V_7 - V_9)/R_3 + (V_7 - V_{11})/R_5 = 0$$

$$(8) -i_{ul2} - (V_9 - V_8)/R_1 + (V_8 - V_6)/R_2 = 0$$

$$(9) -i_{ul1} - (V_7 - V_9)/R_3 + (V_9 - V_8)/R_1 = 0$$

$$(10) -(V_6 - V_{10})/R_4 + i_{ul3} + V_{10}/R_6 = 0$$
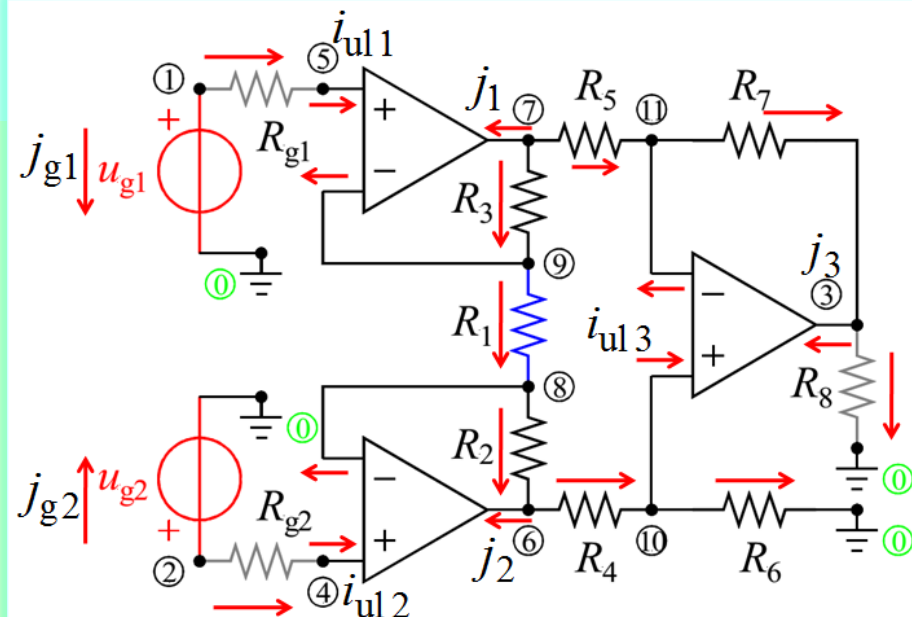
$$(11) -(V_7 - V_{11})/R_5 - i_{ul3} + (V_{11} - V_3)/R_7 = 0$$



$$i_{ul1} = 0$$

$$i_{ul2} = 0$$

$$i_{ul3} = 0$$

$$V_5 = V_9$$

$$V_4 = V_8$$


$$V_{10} = V_{11}$$

$$V_1 = u_{g1}$$

$$V_2 = u_{g2}$$

MATLAB: MuPAD


Jednačine

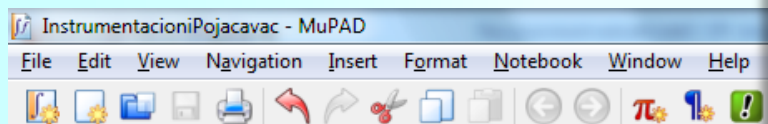

```
jednacine:= {jg1 + (v1-v5)/Rg1 = 0,
v1 = ug1,
jg2 + (v2-v4)/Rg2 = 0,
v2 = ug2,
j3 + v3/R8 - (v11-v3)/R7 = 0,
-(v2-v4)/Rg2 + iul2 = 0, -(v1-v5)/Rg1 + iul1 = 0,
j2 + (v6-v10)/R4 - (v8-v6)/R2 = 0,
j1 + (v7-v11)/R5 + (v7-v9)/R3 = 0,
-iul2 - (v9-v8)/R1 + (v8-v6)/R2 = 0,
-iul1 - (v7-v9)/R3 + (v9-v8)/R1 = 0,
-(v6-v10)/R4 + v10/R6 + iul3 = 0,
-(v7-v11)/R5 + (v11-v3)/R7 -iul3 = 0,
iul1 = 0, iul2 = 0, iul3 = 0, v5=v9, v4=v8, v10 = v11}
```

$$\left\{ v1 = ug1, v2 = ug2, v4 = v8, v5 = v9, v10 = v11, iul3 + \frac{v10}{R6} - \frac{v6-v10}{R4} = 0, j3 + \frac{v3}{R8} + \frac{v3-v11}{R7} = 0, j2 + \frac{v6-v8}{R2} + \frac{v6-v10}{R4} = 0, j1 + \frac{v7-v9}{R3} + \frac{v7-v11}{R5} = 0, iul1 = 0, iul2 = 0, \right.$$
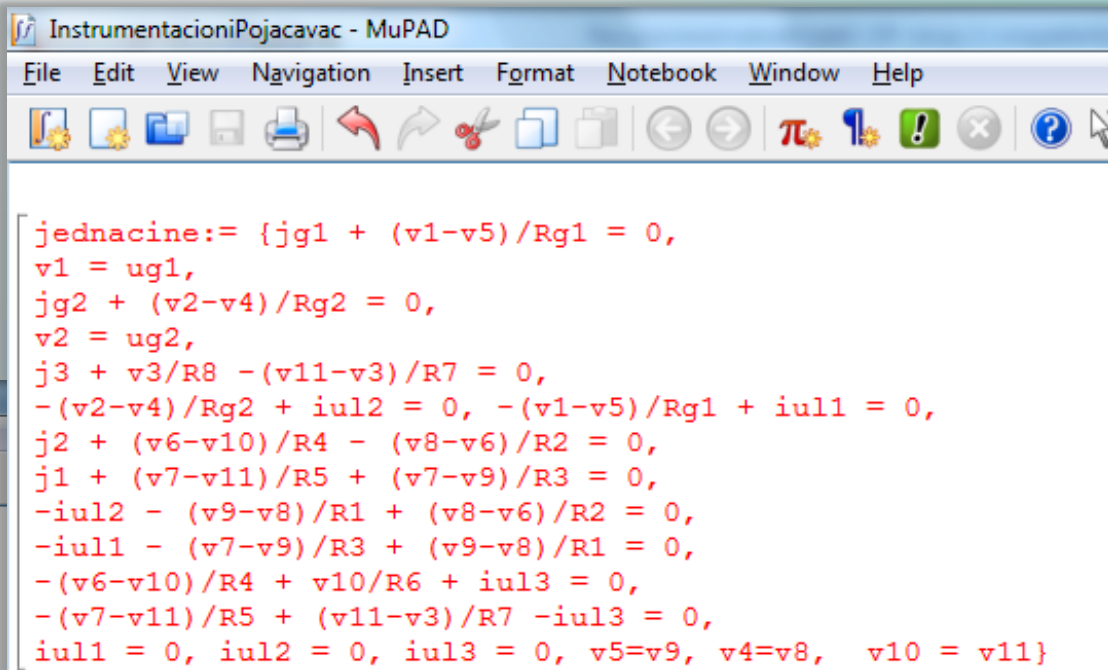
$$\left. iul3 = 0, iul1 - \frac{v1-v5}{Rg1} = 0, iul2 - \frac{v2-v4}{Rg2} = 0, jg1 + \frac{v1-v5}{Rg1} = 0, jg2 + \frac{v2-v4}{Rg2} = 0, \frac{v8-v9}{R1} - \frac{v6-v8}{R2} - iul2 = 0, -iul1 - \frac{v8-v9}{R1} - \frac{v7-v9}{R3} = 0, -iul3 - \frac{v3-v11}{R7} - \frac{v7-v11}{R5} = 0 \right\}$$



MATLAB: MuPAD

assume, Promenljive, solve...

```
[ assume(Rg1>0 and Rg2>0 and R1>0 and R2>0 and R3>0 and R4>0 and R5>0 and R6>0 and R7>0 and R8>0 and R>0)
promenljive:={v1, v2, v3, v4, v5, v6, v7, v8, v9, v10, v11, j1, j2, j3, iul1, iul2, iul3, jg1, jg2}
{iul1, iul2, iul3, j1, j2, j3, jg1, jg2, v1, v2, v3, v4, v5, v6, v7, v8, v9, v10, v11}
odziv:=solve(jednacine, promenljive)
```

```
[ assume(Rg1>0 and Rg2>0 and R1>0 and R2>0 and R3>0 and R4>0 and R5>0 and R6>0 and R7>0 and R8>0 and R>0)
promenljive:={v1, v2, v3, v4, v5, v6, v7, v8, v9, v10, v11, j1, j2, j3, iul1, iul2, iul3, jg1, jg2}
{iul1, iul2, iul3, j1, j2, j3, jg1, jg2, v1, v2, v3, v4, v5, v6, v7, v8, v9, v10, v11}
odziv:=solve(jednacine, promenljive)
{ iul1 = 0, iul2 = 0, iul3 = 0, j1 = -  $\frac{R1 R4 ug1 + R1 R6 ug1 + R3 R4 ug1 - R1 R6 ug2 + R2 R6 ug1 - R3 R4 ug2 - R2 R6 ug2 + R3 R6 ug1 + R4 R5 ug1 - R3 R6 ug2 - R4 R5 ug2 + R5 R6 ug1 - R5 R6 ug2}{\sigma_1}$ ,
j2 = -  $\frac{R1 ug2 - R2 ug1 + R2 ug2 - R4 ug1 + R4 ug2 - R6 ug1 + R6 ug2}{R1 (R4 + R6)}$ , j3 = (R1 R4 R7 ug1 + R1 R4 R8 ug1 - R1 R5 R6 ug2 + R2 R5 R6 ug1 + R1 R6 R7 ug1 - R2 R5 R6 ug2 + R3 R4 R7 ug1 - R1 R6 R7 ug2
+ R1 R6 R8 ug1 + R2 R6 R7 ug1 - R3 R4 R7 ug2 + R3 R4 R8 ug1 - R1 R6 R8 ug2 - R2 R6 R7 ug2 + R2 R6 R8 ug1 - R3 R4 R8 ug2 + R3 R6 R7 ug1 - R2 R6 R8 ug2 - R3 R6 R7 ug2 + R3 R6 R8 ug1
- R3 R6 R8 ug2)/(R1 R5 R8 (R4 + R6)), jg1 = 0, jg2 = 0, v1 = ug1, v2 = ug2,
v3 = -  $\frac{R1 R4 R7 ug1 - R1 R5 R6 ug2 + R2 R5 R6 ug1 + R1 R6 R7 ug1 - R2 R5 R6 ug2 + R3 R4 R7 ug1 - R1 R6 R7 ug2 + R2 R6 R7 ug1 - R3 R4 R7 ug2 - R2 R6 R7 ug2 + R3 R6 R7 ug1 - R3 R6 R7 ug2}{\sigma_1}$ , v4 = ug2, v5 = ug1, v6 =  $\frac{\sigma_3}{R1}$ ,
v7 =  $\frac{R1 ug1 + R3 ug1 - R3 ug2}{R1}$ , v8 = ug2, v9 = ug1, v10 =  $\sigma_2$ , v11 =  $\sigma_2$  }
```

where

$$\sigma_1 = R1 R5 (R4 + R6)$$

$$\sigma_2 = \frac{R6 \sigma_3}{R1 (R4 + R6)}$$

$$\sigma_3 = R1 ug2 - R2 ug1 + R2 ug2$$

MATLAB: MuPAD

Zamena..., simplify, heaviside, plot...

```
zamena:={R2=R, R3=R, R4=R, R5=R, R6=R, R7=R}
{R2 = R, R3 = R, R4 = R, R5 = R, R6 = R, R7 = R}

v3|odziv
- 
$$\frac{R_1 R_4 R_7 u_{g1} - R_1 R_5 R_6 u_{g2} + R_2 R_5 R_6 u_{g1} + R_1 R_6 R_7 u_{g1} - R_2 R_5 R_6 u_{g2} + R_3 R_4 R_7 u_{g1} - R_1 R_6 R_7 u_{g2} + R_2 R_6 R_7 u_{g1} - R_3 R_4 R_7 u_{g2} - R_2 R_6 R_7 u_{g2} + R_3 R_6 R_7 u_{g1} - R_3 R_6 R_7 u_{g2}}{R_1 R_5 (R_4 + R_6)}$$


v3|odziv|zamena
- 
$$\frac{4 R^3 u_{g1} - 4 R^3 u_{g2} + 2 R^2 R_1 u_{g1} - 2 R^2 R_1 u_{g2}}{2 R^2 R_1}$$


simplify(v3|odziv|zamena)
- 
$$\frac{(2 R + R_1) (u_{g1} - u_{g2})}{R_1}$$

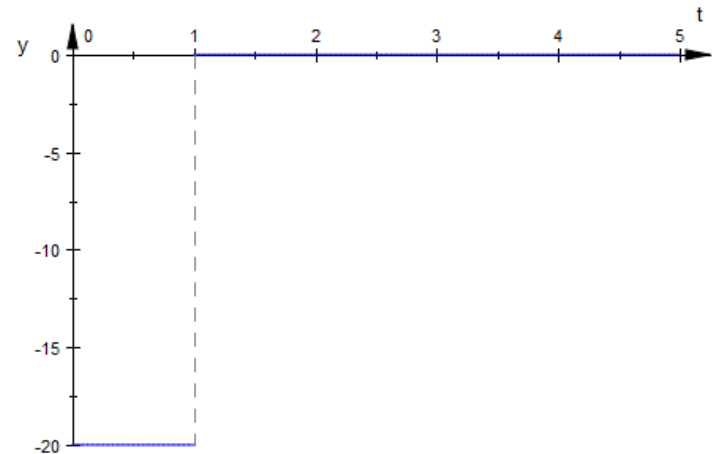

assume(U>0 and T>0 and t>0): pobude:={ug1=U*heaviside(t),ug2=U*heaviside(t-T)}
{ug1 = U, ug2 = U heaviside(t-T)}

simplify(v3|odziv|zamena)|pobude
- 
$$\frac{(U - U \text{heaviside}(t-T)) (2 R + R_1)}{R_1}$$


vrednosti:={U=10, T=1, R=1000, R1=2000}
{R = 1000, R1 = 2000, T = 1, U = 10}

ur8(t):=simplify(v3|odziv|zamena)|pobude|vrednosti
20 heaviside(t-1) - 20
```



```
plot(ur8(t), t=0..5)
```



```
pg:=jg1*ug1+jg2*ug2|odziv
0
```


MATLAB: Simulink




Sources

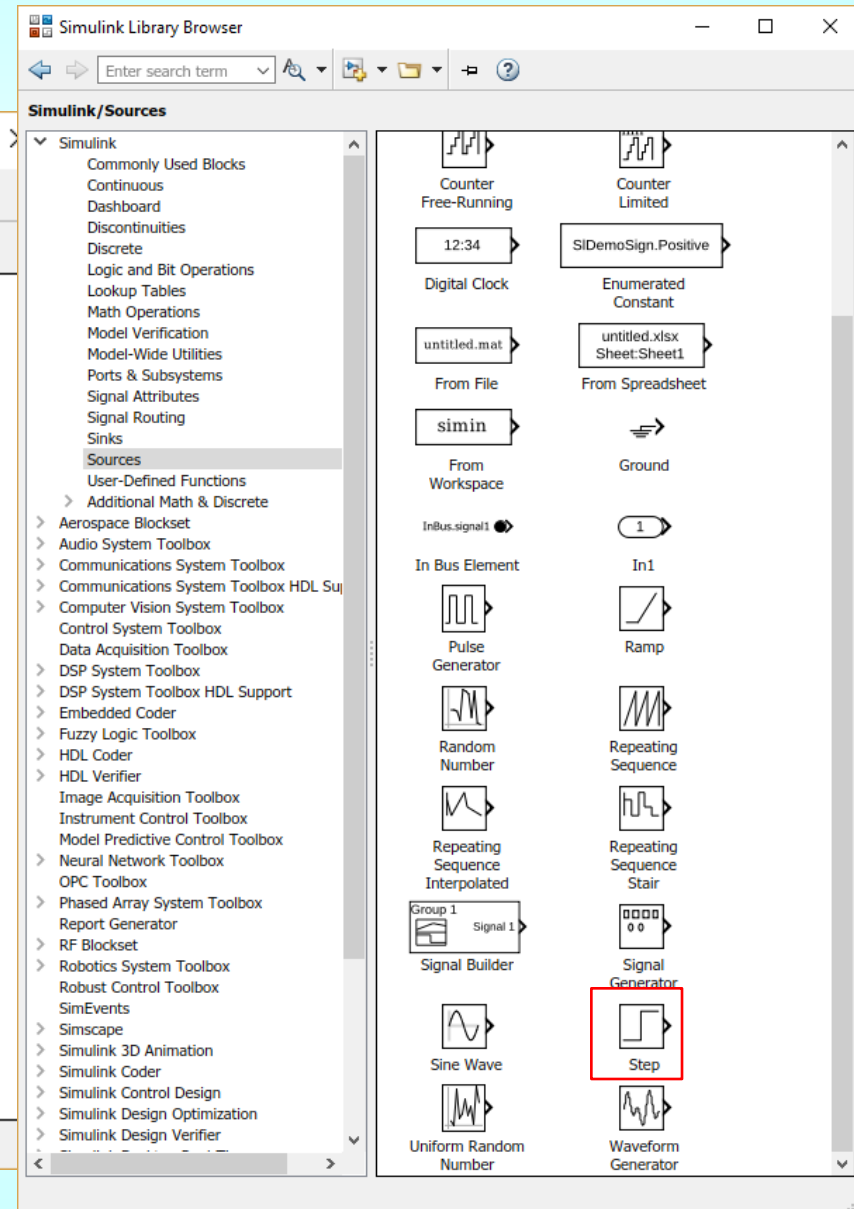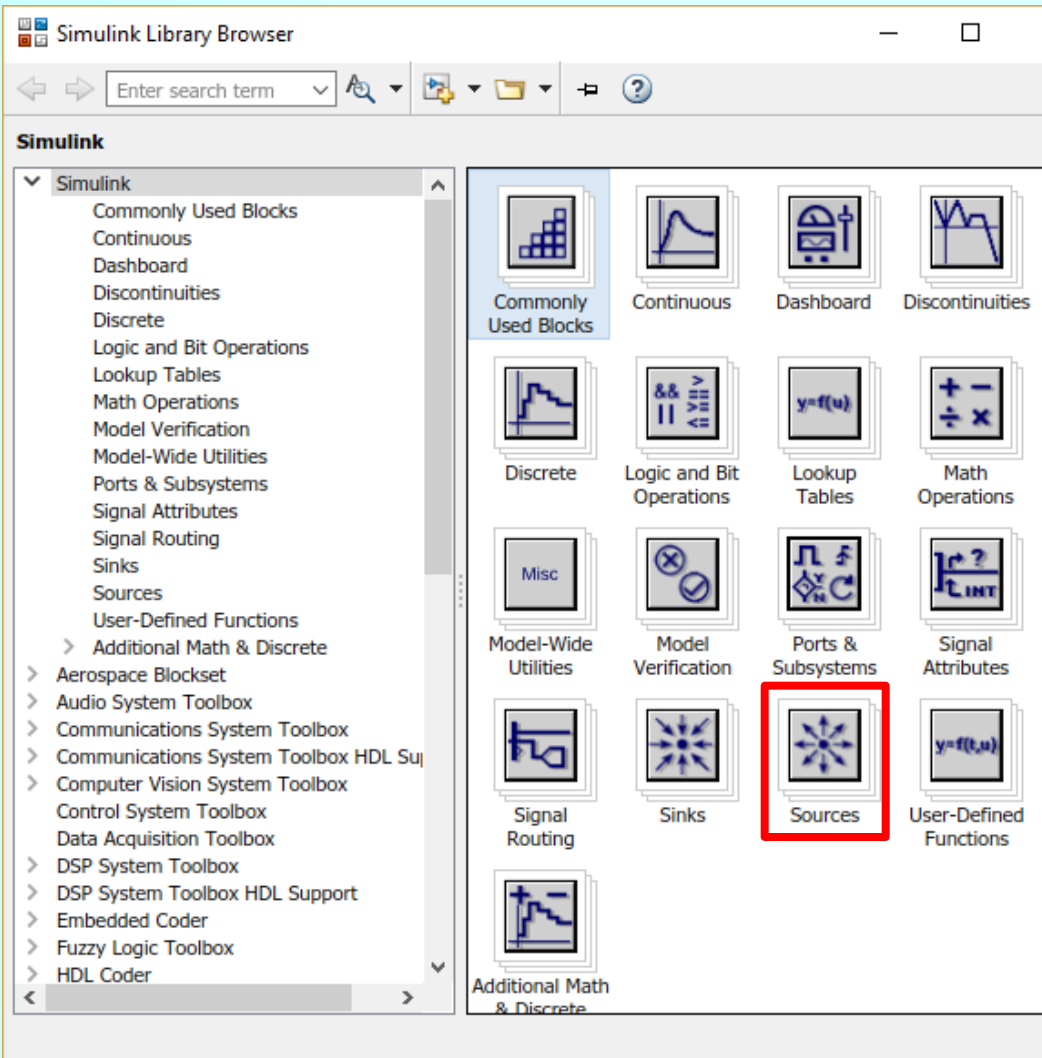

MATLAB: Simscape


Foundation Library

Electrical, Electrical Sources

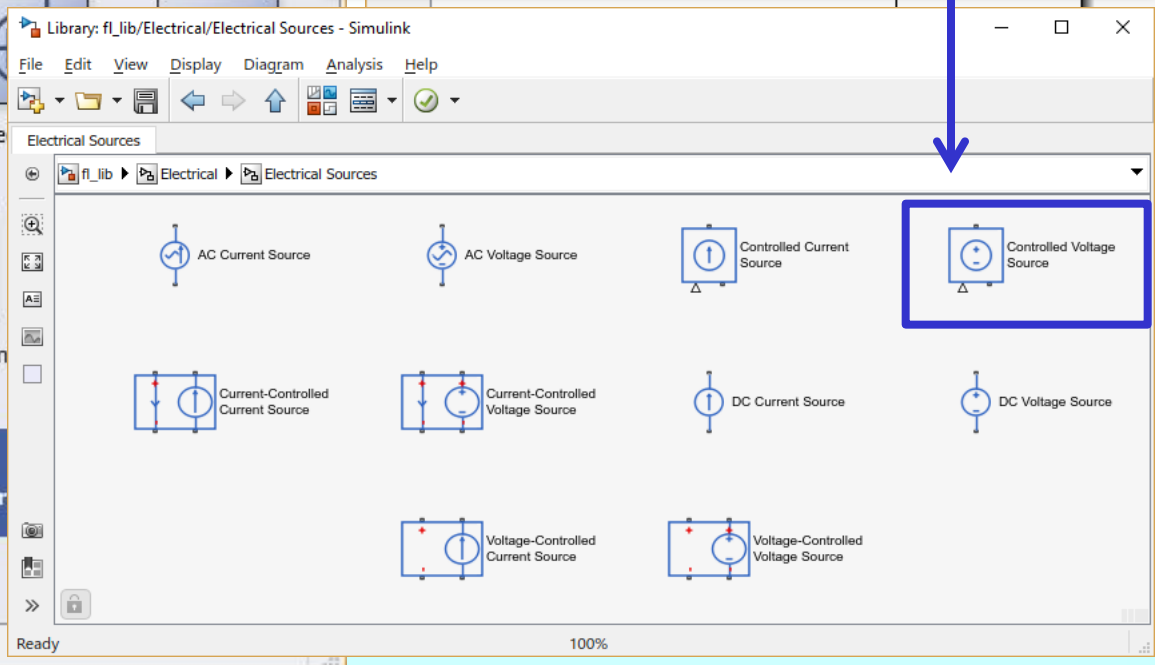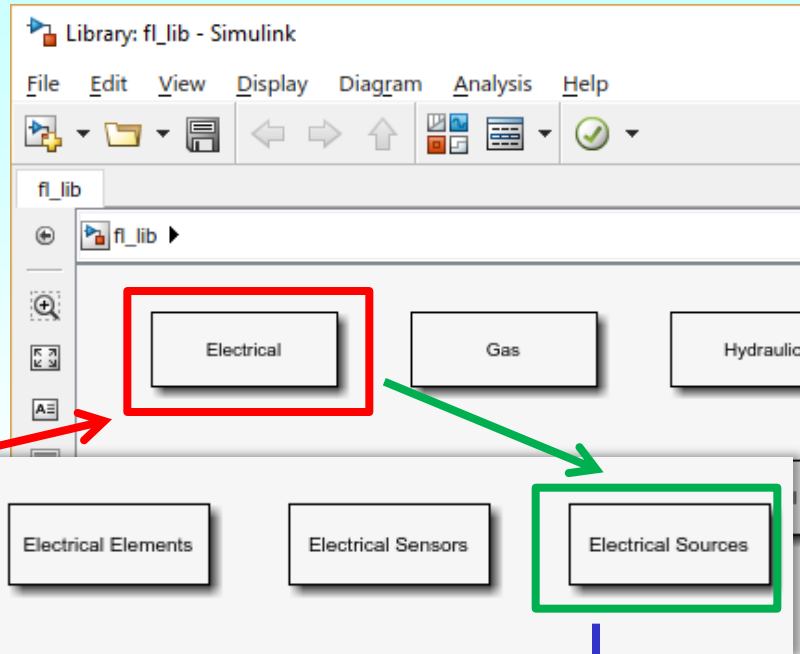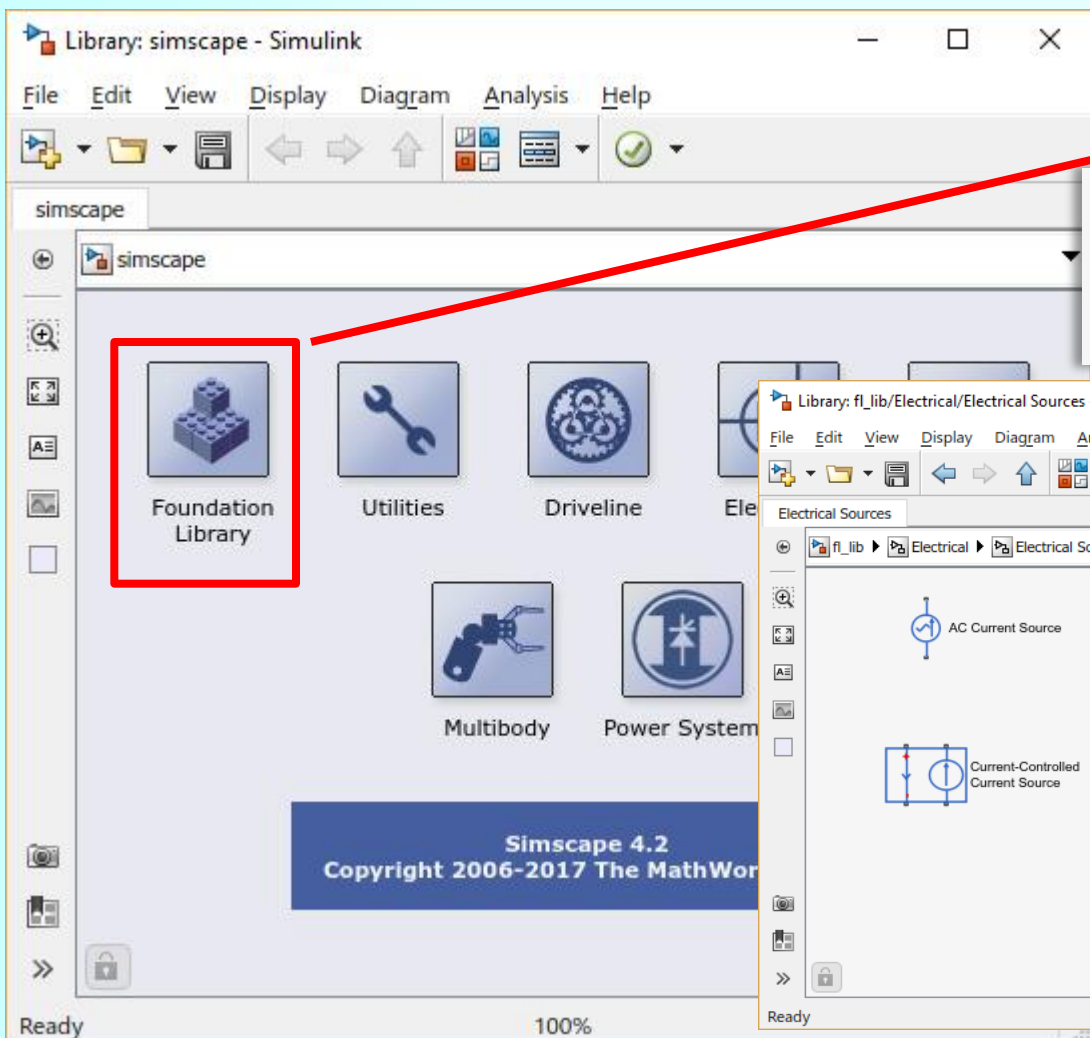




MATLAB: Simscape


Utilities

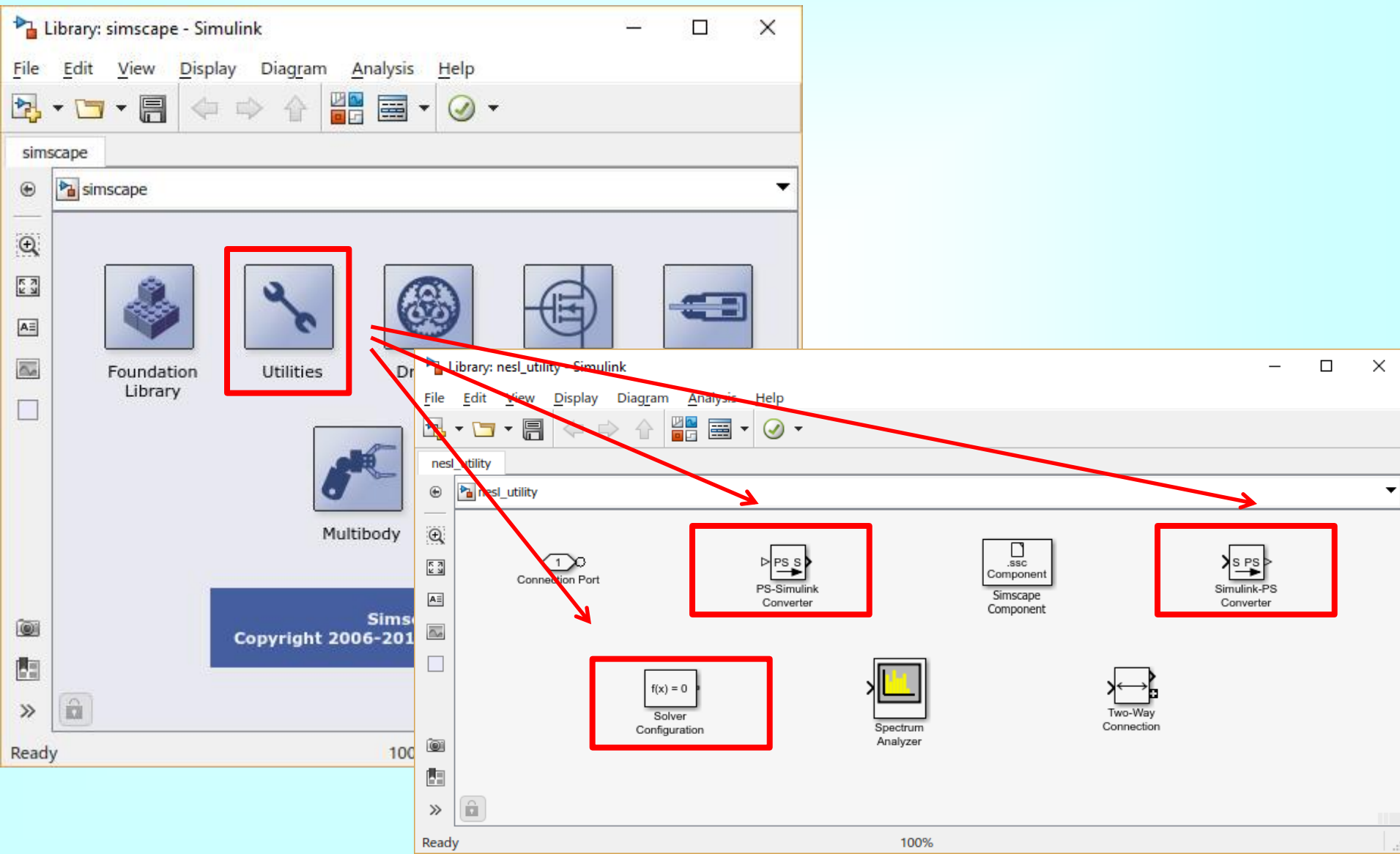

MATLAB: Simscape


Foundation Library, Utilities, Simulink

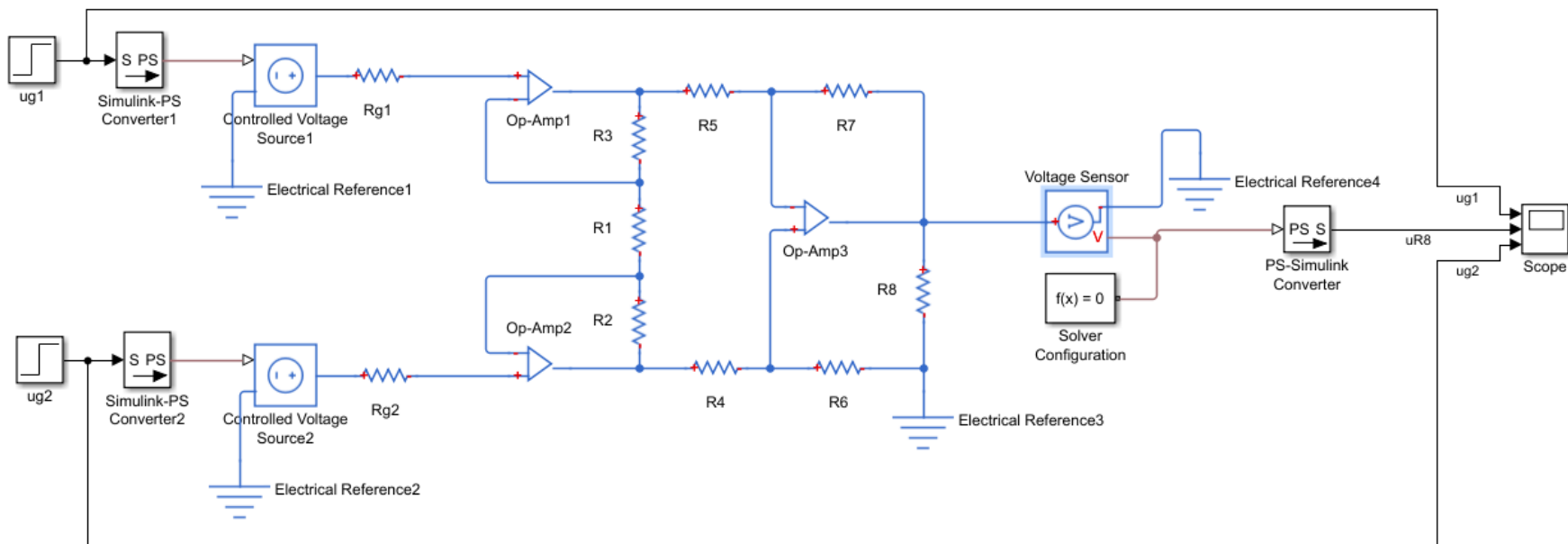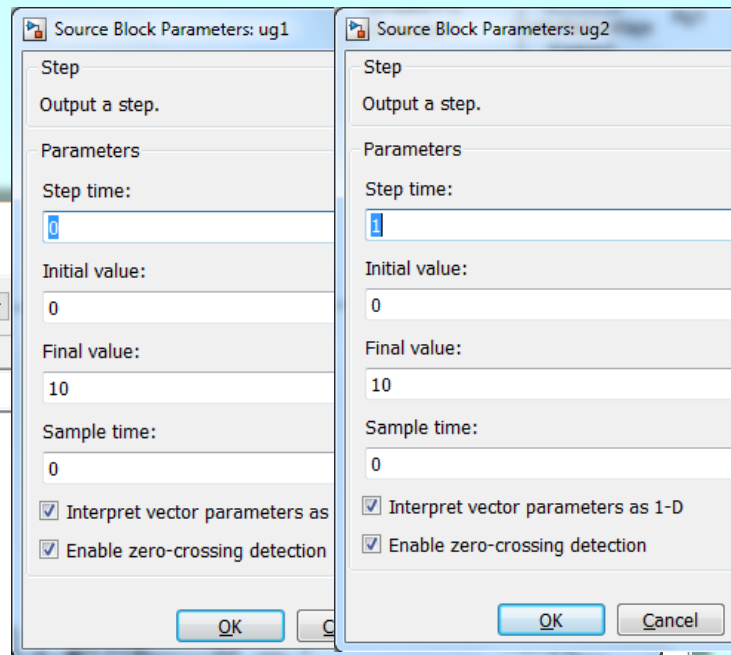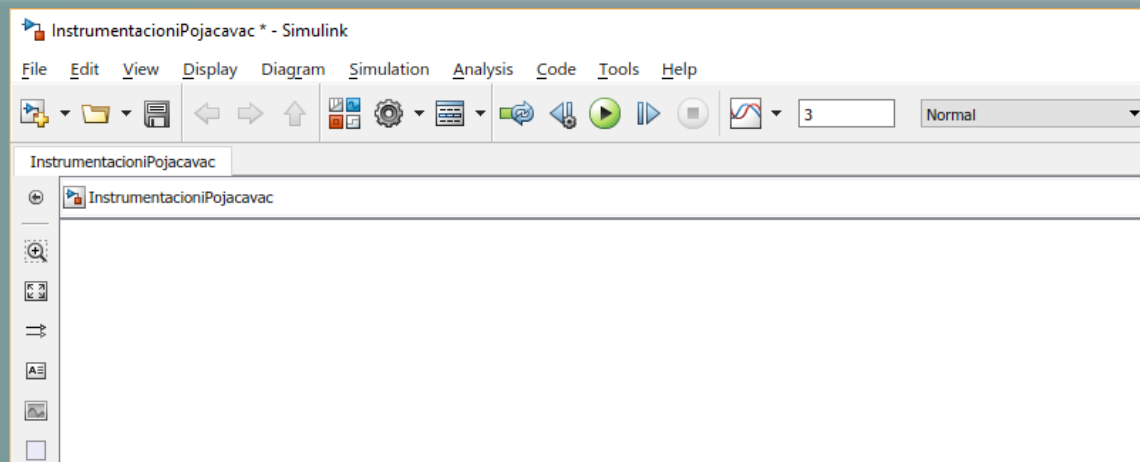

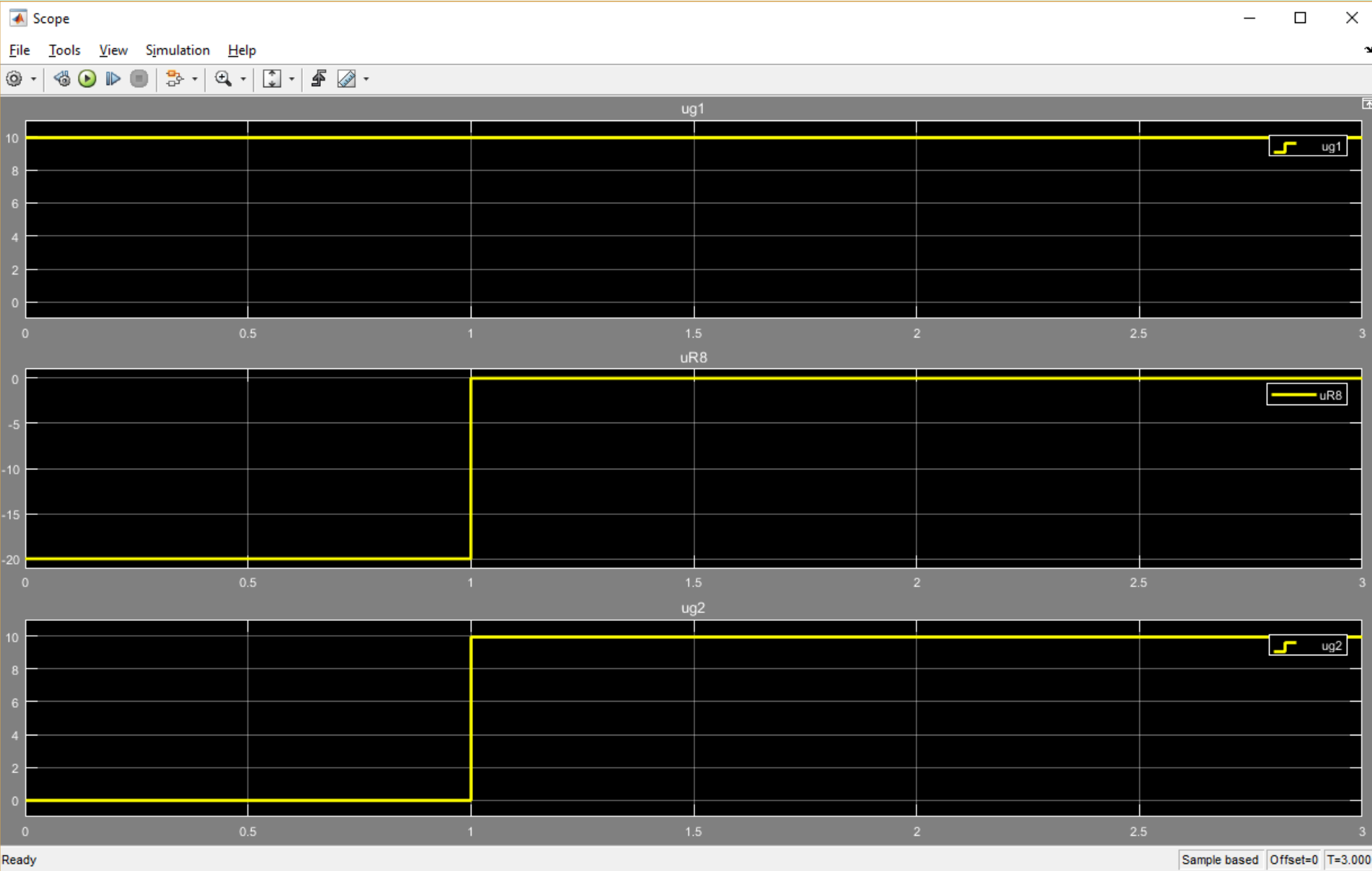




MATLAB: Simscape

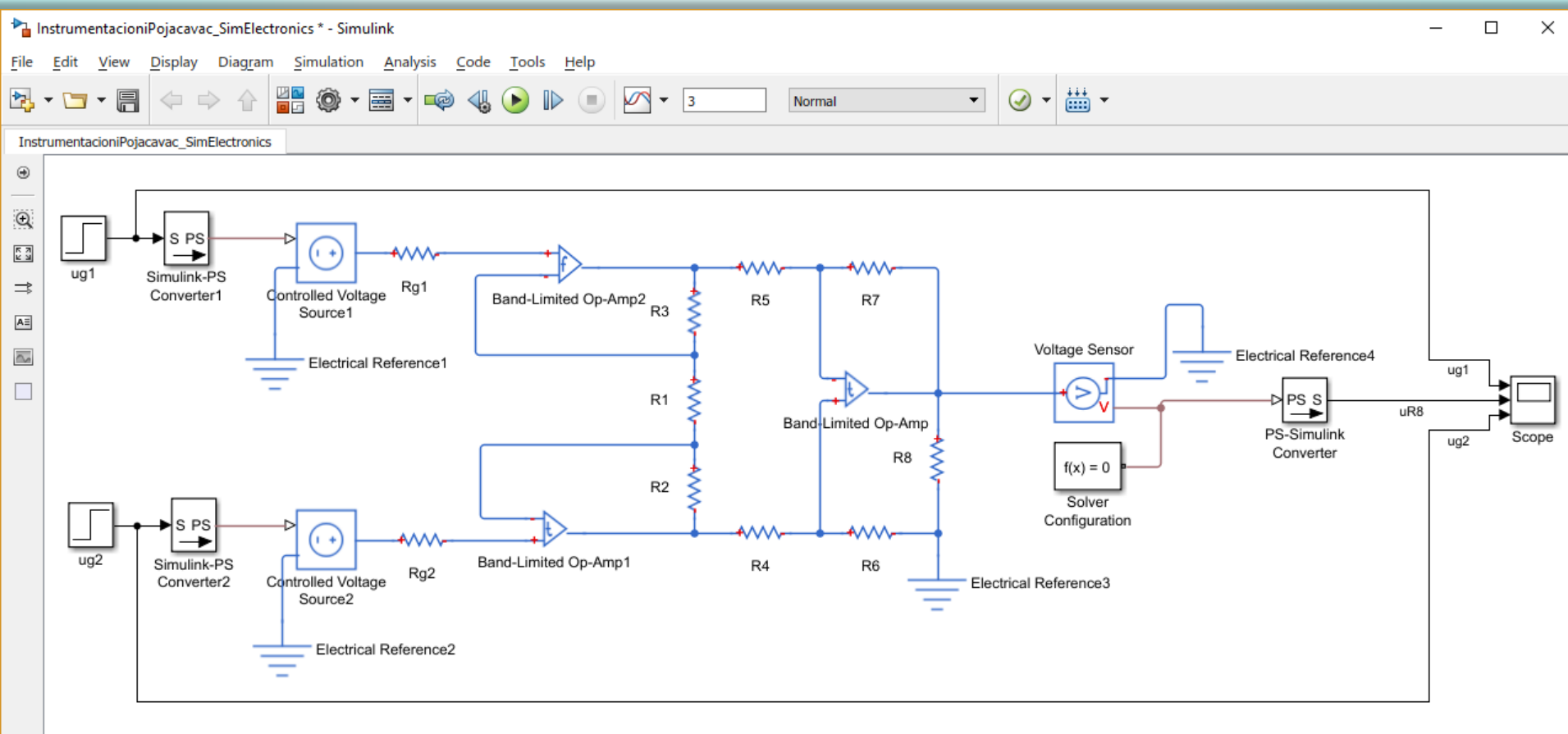Foundation Library, Electronics, Utilities, Simulink



MATLAB: Simscape

Electronics, Integrated Circuits

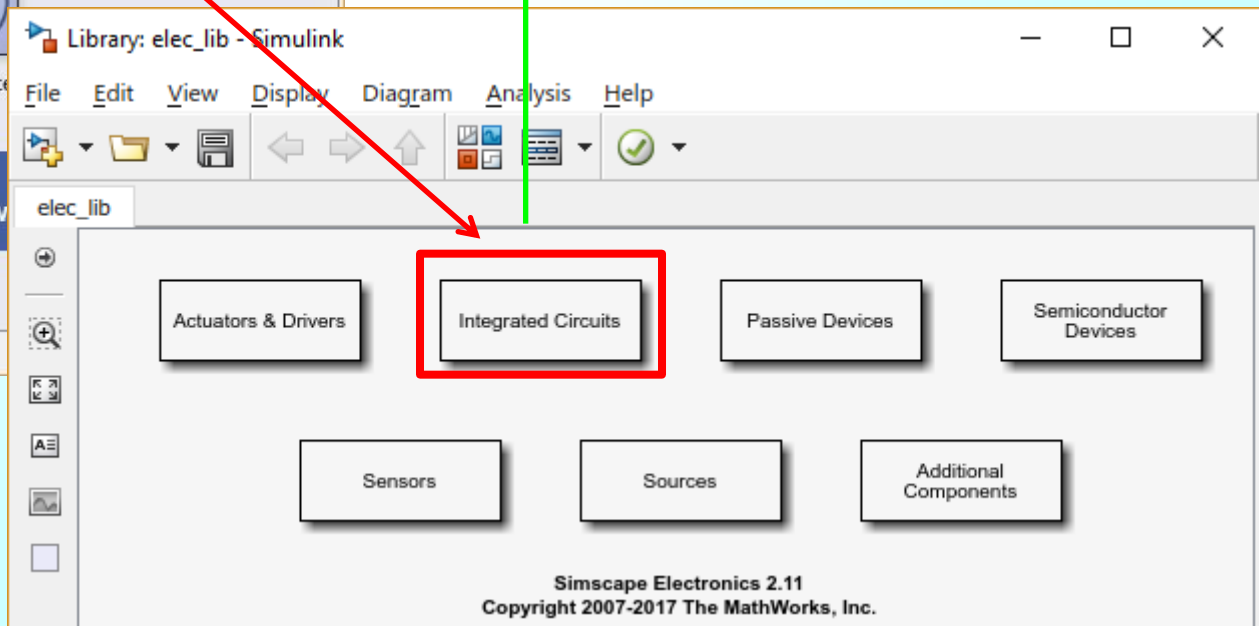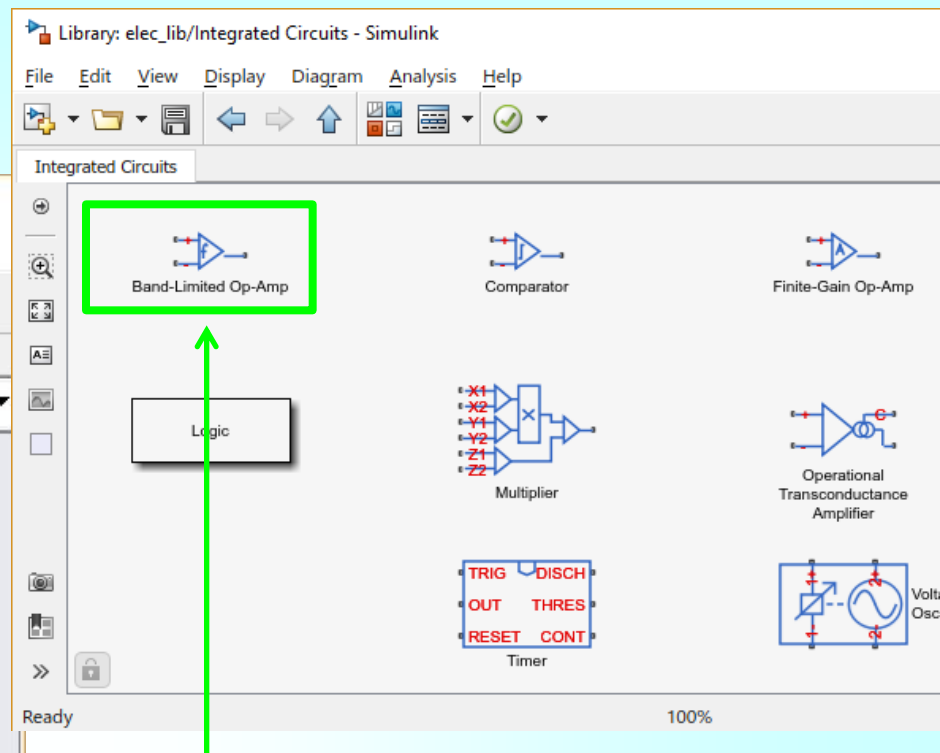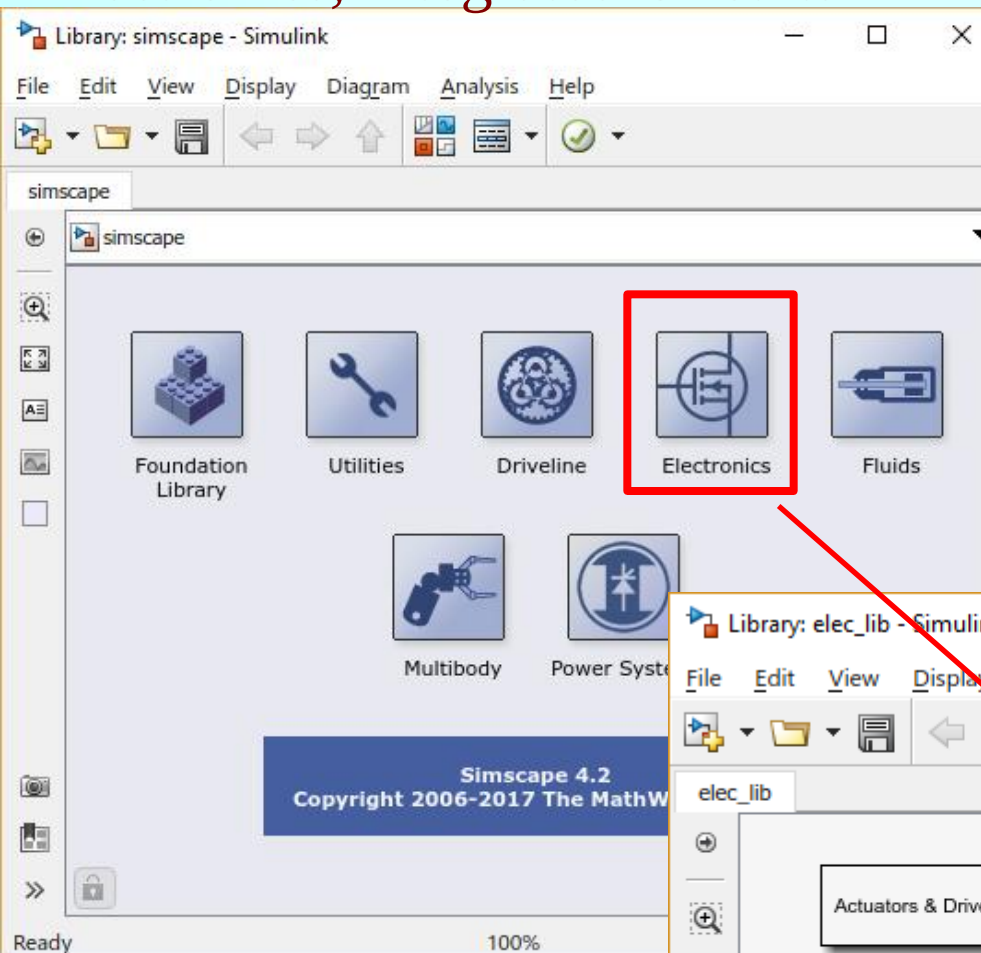

Band-Limited Op-Amp: LM7301

Block Parameters: Band-Limited Op-Amp

Band-Limited Op-Amp

This block models a band-limited op-amp. If the voltages at the positive and negative pins are denoted V_p and V_m , then the output voltage is given by

$$V_{out} = A \cdot (V_p - V_m) \cdot 1 / (s / (2 \cdot \pi \cdot f) + 1) - I_{out} \cdot R_{out}$$


where A is the gain, R_{out} is the output resistance, I_{out} is the output current, s is the Laplace operator, and f is the 3dB bandwidth. The input current is given by $(V_p - V_m) / R_{in}$ where R_{in} is the input resistance. The no-load output voltage is limited the range V_{min} to V_{max} , and the slew rate is limited to $\pm V_{dot}$.


The Initial output voltage, V_0 , sets the initial op-amp output voltage. Note that this does not take account of any voltage drop across R_{out} . The initial condition is not used if you select the Start simulation from steady state option in the Solver Configuration block.

Settings

Parameters


Gain, A:	7.1e4	
Input resistance, R_{in} :	39	MOhm ▾
Output resistance, R_{out} :	0	Ohm ▾
Minimum output, V_{min} :	-20	V ▾
Maximum output, V_{max} :	20	V ▾
Maximum slew rate, V_{dot} :	1.25/1e-6	V/s ▾
Bandwidth, f :	4e6	Hz ▾
Initial output voltage, V_0 :	0	V ▾

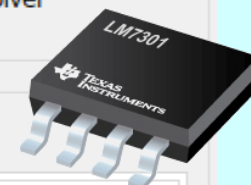


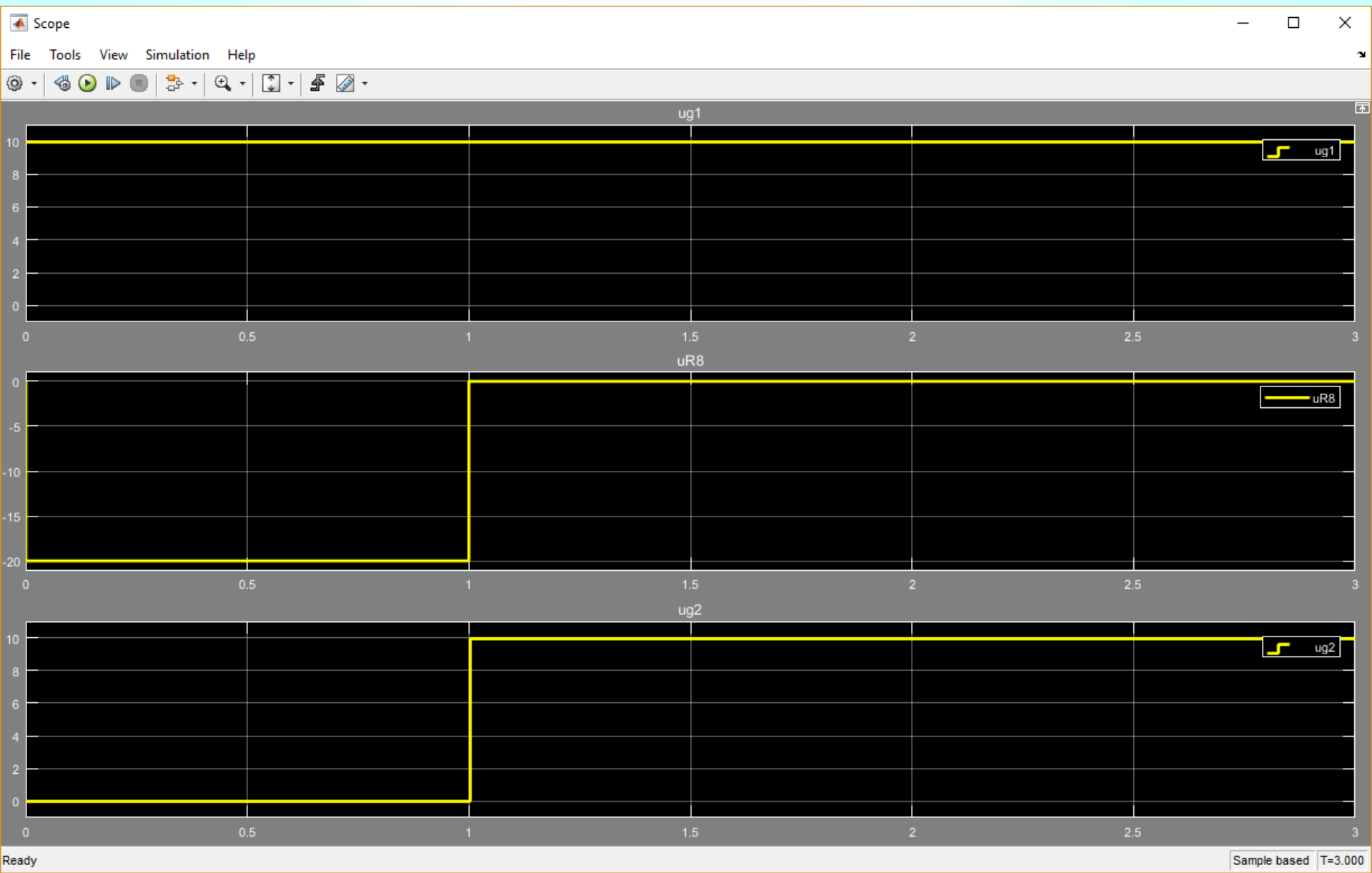

ABCD parametri mreže

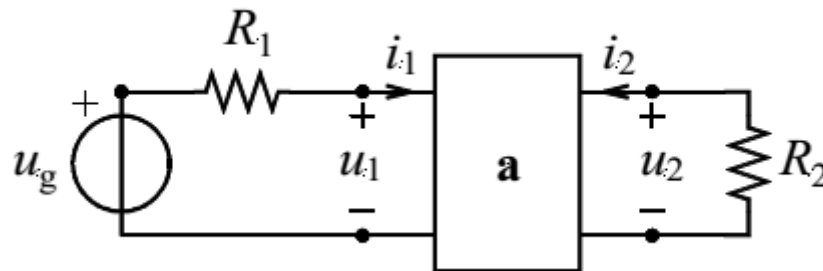- Otpornosti otpornika i a -parametri (ABCD-parametri) mreže sa dva pristupa su poznati.
- Odrediti:
 - Količnik napona $A = u_2 / u_g$
 - Ulaznu otpornost mreže $R_u = u_1 / i_1$
 - Struju i_1
- Smatrati da su a -parametri mreže realni i različiti od nule



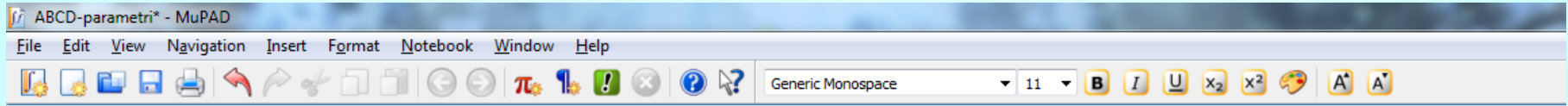

MATLAB: MuPAD

```
jednacine:= {ug = R1*i1 + u1,
u2 + R2*i2 = 0,
u1 = a11*u2 + a12*(-i2),
i1 = a21*u2 + a22*(-i2)}

{u2+R2 i2 = 0, i1 = a21 u2 - a22 i2, u1 = a11 u2 - a12 i2, ug = u1 + R1 i1}

promenljive:={u1, u2, i1, i2}
{i1, i2, u1, u2}
```

```
odziv:=solve(jednacine, promenljive)
```

$\left\{ \begin{aligned} &[i1 = 0, i2 = z, u1 = 0, u2 = 0] \\ &\left[i1 = \frac{ug}{R1}, i2 = -\frac{ug}{R1 a22}, u1 = 0, u2 = 0 \right] \\ &[i1 = -a22 z, i2 = z, u1 = 0, u2 = 0] \\ &\left[i1 = \frac{a22 ug}{a12 + R1 a22}, i2 = -\frac{ug}{a12 + R1 a22}, u1 = \frac{a12 ug}{a12 + R1 a22}, u2 = 0 \right] \\ &\left[i1 = \frac{a22 z}{a12}, i2 = -\frac{z}{a12}, u1 = z, u2 = 0 \right] \\ &\left[i1 = \frac{a22 ug + R2 a21 ug}{\sigma_1}, i2 = -\frac{ug}{\sigma_1}, u1 = \frac{ug (a12 + R2 a11)}{\sigma_1}, u2 = \frac{R2 ug}{\sigma_1} \right] \\ &\left[i1 = \frac{z (a22 + R2 a21)}{R2}, i2 = -\frac{z}{R2}, u1 = \frac{z (a12 + R2 a11)}{R2}, u2 = z \right] \end{aligned} \right.$	if $R2 = 0 \wedge a12 = 0 \wedge a22 = 0 \wedge ug = 0$ if $R2 = 0 \wedge R1 \neq 0 \wedge a12 = 0 \wedge a22 \neq 0$ if $R2 = 0 \wedge a12 = 0 \wedge (R1 = 0 \vee a22 = 0) \wedge ug = 0$ if $a12 + R1 a22 \neq 0 \wedge R2 = 0 \wedge a12 \neq 0$ if $a12 + R1 a22 = 0 \wedge R2 = 0 \wedge a12 \neq 0 \wedge ug = 0$ if $\sigma_1 \neq 0 \wedge R2 \neq 0$ if $\sigma_1 = 0 \wedge R2 \neq 0 \wedge ug = 0$ if $(\sigma_1 = 0 \wedge (R2 = 0 \vee ug \neq 0)) \vee ((a12 + R1 a22 = 0 \vee (a12 = 0 \wedge (R1 = 0 \vee a22 = 0))) \wedge R2 = 0 \wedge ug \neq 0)$
---	--

where

$$\sigma_1 = a12 + R2 a11 + R1 a22 + R1 R2 a21$$

```
odziv[6]
```

$$\left\{ \left[i1 = \frac{a22 ug + R2 a21 ug}{\sigma_1}, i2 = -\frac{ug}{\sigma_1}, u1 = \frac{ug (a12 + R2 a11)}{\sigma_1}, u2 = \frac{R2 ug}{\sigma_1} \right] \right\}$$

where

$$\sigma_1 = a12 + R2 a11 + R1 a22 + R1 R2 a21$$

```
odziv[6]
```

$$\left\{ \left[i1 = \frac{a22 ug + R2 a21 ug}{\sigma_1}, i2 = -\frac{ug}{\sigma_1}, u1 = \frac{ug (a12 + R2 a11)}{\sigma_1}, u2 = \frac{R2 ug}{\sigma_1} \right] \right\}$$

where

$$\sigma_1 = a12 + R2 a11 + R1 a22 + R1 R2 a21$$

```
A:=(u2|odziv[6])/ug
      R2
-----
a12 + R2 a11 + R1 a22 + R1 R2 a21
```

```
Ru:=simplify((u1/i1)|odziv[6])
      a12 + R2 a11
-----
a22 + R2 a21
```

```
simplify(i1|odziv[6])
      ug (a22 + R2 a21)
-----
a12 + R2 a11 + R1 a22 + R1 R2 a21
```

MATLAB: MuPAD

assume...

```
ABCD-parametri_assumption* - MuPAD
File Edit View Navigation Insert Format Notebook Window Help
[Icons]

jednacine:= {ug = R1*i1 + u1,
u2 + R2*i2 = 0,
u1 = a11*u2 + a12*(-i2),
i1 = a21*u2 + a22*(-i2)}

{u2 + R2 i2 = 0, i1 = a21 u2 - a22 i2, u1 = a11 u2 - a12 i2, ug = u1 + R1 i1}

promenljive:={u1, u2, i1, i2}
{i1, i2, u1, u2}

[assume(a11*a22-a12*a21<>0 and R1>0 and R2>0 and ug<>0):
odziv:=solve(jednacine, promenljive)

{
if  $\sigma_1 = 0$ 
 $\emptyset$ 
if  $\sigma_1 \neq 0$ 
 $\left\{ \left[ i1 = \frac{a22 ug + R2 a21 ug}{\sigma_1}, i2 = -\frac{ug}{\sigma_1}, u1 = \frac{ug (a12 + R2 a11)}{\sigma_1}, u2 = \frac{R2 ug}{\sigma_1} \right] \right\}$ 
}

where

 $\sigma_1 = a12 + R2 a11 + R1 a22 + R1 R2 a21$ 
```

odziv[2]

$$\left\{ \left[i1 = \frac{a22 ug + R2 a21 ug}{\sigma_1}, i2 = -\frac{ug}{\sigma_1}, u1 = \frac{ug (a12 + R2 a11)}{\sigma_1}, u2 = \frac{R2 ug}{\sigma_1} \right] \right\}$$

where

$$\sigma_1 = a12 + R2 a11 + R1 a22 + R1 R2 a21$$

```
A:=(u2|odziv[2])/ug
      R2
a12 + R2 a11 + R1 a22 + R1 R2 a21

Ru:=simplify((u1/i1)|odziv[2])
      a12 + R2 a11
a22 + R2 a21

simplify(i1|odziv[2])
      ug (a22 + R2 a21)
a12 + R2 a11 + R1 a22 + R1 R2 a21
```