
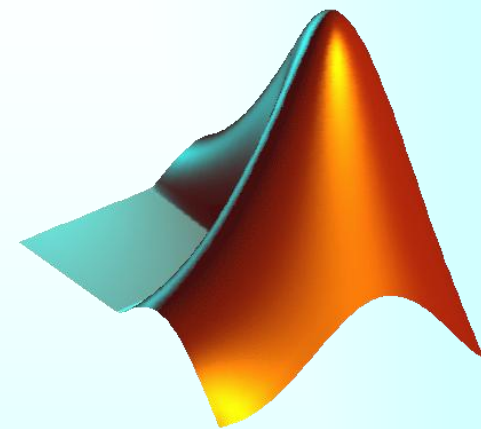


Рачунарска анализа електричних кола

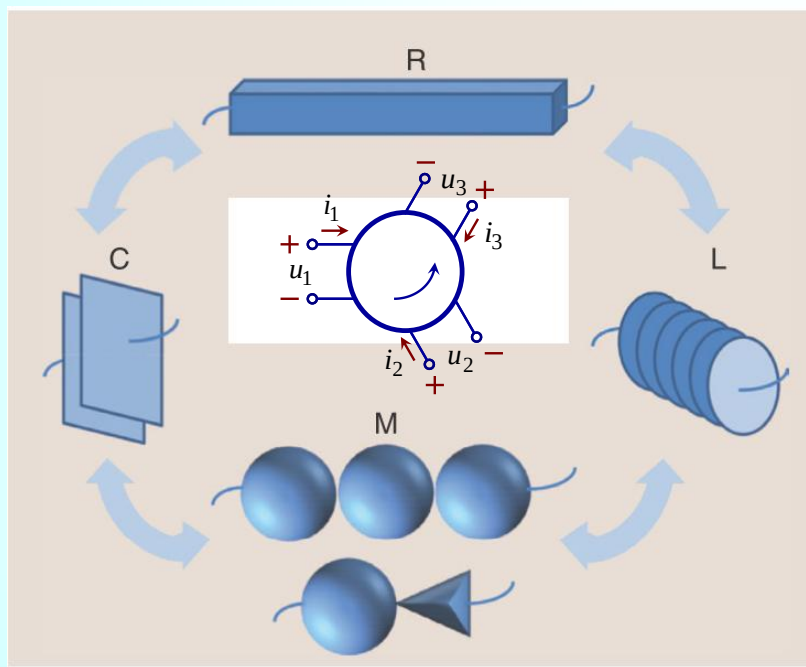


Милка Потребих



Рачунарски (софтверски) алати

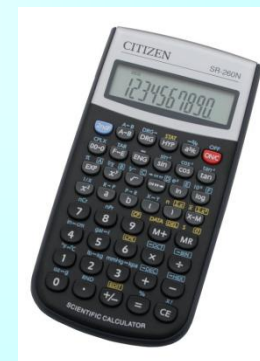- *Mathematica*, MuPAD, Maxima, SymPy
- MATLAB, Scilab, Octave, FreeMat
- LTspice, ngspice, QucsStudio, XCircuit
- Python, MathCAD, MAPLE, SpeQ Mathematics...



Free/Libre Open Source Software (FLOSS)

Одзив на побуду

Вредности елемената електричног кола са слике су познате.


(а) Одредити једначине стања у скаларном и матричном облику.

Који је ред кола?

(б) Одредити импулсни одзив (Гринову функцију) за напон u ако је


$$R_1 = R_2 = R ,$$

$$L = CR^2 .$$

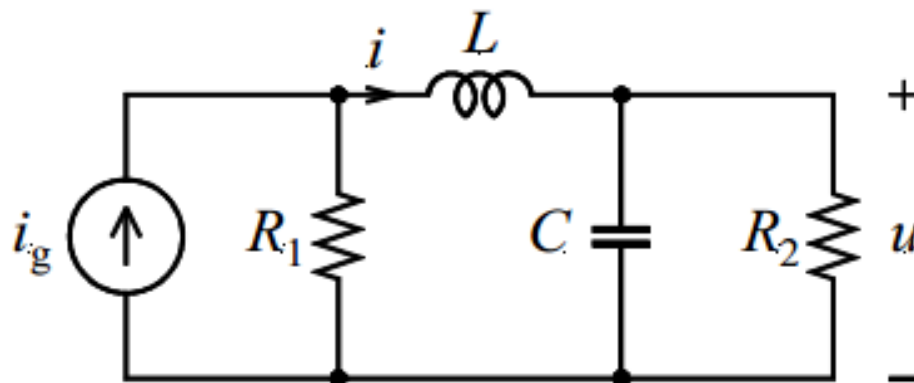

MATLAB: MuPAD

Једначине стања

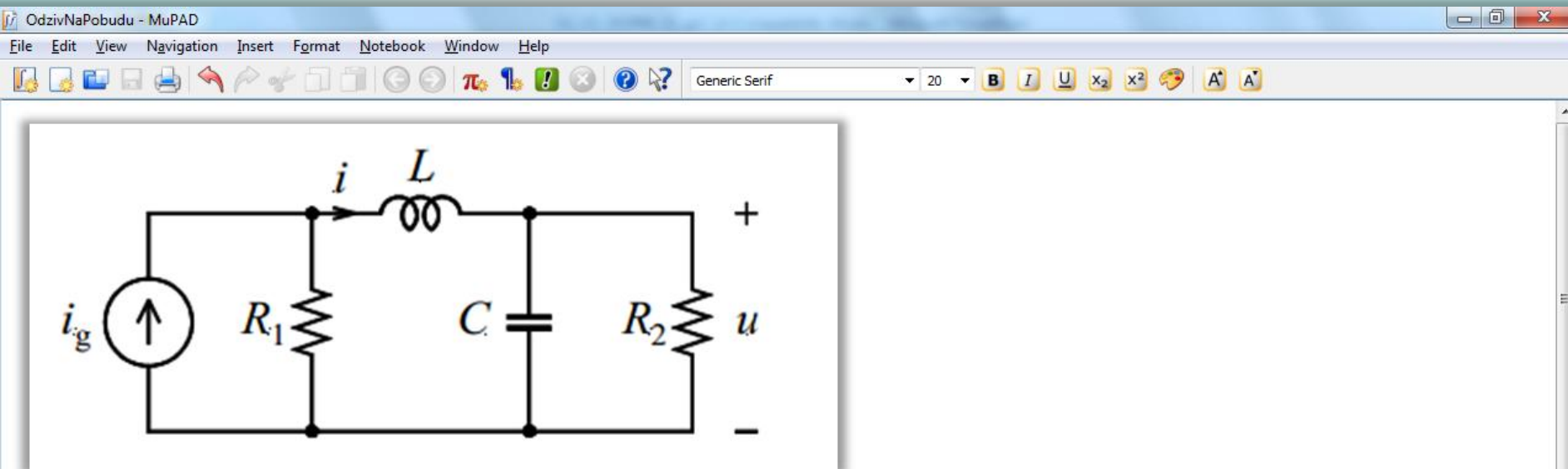

jednacine:={ $i_g = i_1 + i_L$,

$i_L = i_C + i_2$,

$u_1 = u_L + u_C$,

$u_C = u_2$,

$u_1 = R_1 * i_1$,

$u_2 = R_2 * i_2$,

$u_L = L * DiL$,

$i_C = C * DuC$ }

{ $u_1 = u_C + u_L$, $u_C = u_2$, $i_C = C DuC$, $u_L = DiL L$, $u_1 = R_1 i_1$, $u_2 = R_2 i_2$, $i_L = i_2 + i_C$, $i_g = i_1 + i_L$ }

MATLAB: MuPAD

```
jednacine:={ig = i1 + iL,  
iL = iC + i2,  
u1 = uL + uC,  
uC = u2,  
u1 = R1 * i1,  
u2 = R2 * i2,  
uL = L * DiL,  
iC = C*DuC}  
  
{u1 = uC + uL, uC = u2, iC = C DuC, uL = DiL L, u1 = R1 i1, u2 = R2 i2, iL = i2 + iC, ig = i1 + iL}  
  
jednacineIzvoda:=groebner::eliminate(jednacine,{i1, i2, iC, u1, u2, uL})  
[uC + R1 iL - R1 ig + DiL L, R2 iL - uC - C DuC R2, R1 R2 ig - R2 uC - DiL L R2 - R1 uC - C DuC R1 R2]  
  
assume({R1, R2, C, L, R, t} in R_)  
assumeAlso( R1>0 and R2>0 and C>0 and L>0 and R>0 )  
  
jednacineStanje := solve(jednacineIzvoda, {DiL, DuC})  
  
{  
  [DiL = -  $\frac{uC + R1 iL - R1 ig}{L}$ , DuC = -  $\frac{uC - R2 iL}{C R2}$ ]  
}  
  
PromenljiveStanjaIzvodi:={uC=uC(t), iL=iL(t), DiL=D(iL)(t), DuC=D(uC)(t)}  
  
{iL = iL(t), uC = uC(t), DiL = iL'(t), DuC = uC'(t)}
```

MATLAB: MuPAD

```
zamene := {R1=R, R2=R, L=C*R^2}
```

```
{R1 = R, R2 = R, L = C R^2}
```

```
JS:=jednacineStanje | PromenljiveStanjaIzvodi | zamene
```

```
{ [ iL'(t) = - (uC(t) - R ig + R iL(t)) / (C R^2), uC'(t) = - (uC(t) - R iL(t)) / (C R) ] }
```

```
JednacineDiffExpand := expand(JS)
```

```
{ [ iL'(t) = ig / (C R) - iL(t) / (C R) - uC(t) / (C R^2), uC'(t) = iL(t) / C - uC(t) / (C R) ] }
```

```
rhsJednacineDiff:=map(op(JednacineDiffExpand), rhs)
```

```
[ ig / (C R) - iL(t) / (C R) - uC(t) / (C R^2), iL(t) / C - uC(t) / (C R) ]
```

```
Acol1 := coeff(rhsJednacineDiff[i], iL(t),1)$ i = 1..2
```

```
- 1 / (C R), 1 / C
```

```
Acol2 := coeff(rhsJednacineDiff[i], uC(t),1)$ i = 1..2
```

```
- 1 / (C R^2), - 1 / (C R)
```

$\text{Atr} := \text{matrix}([\text{Acol1}], [\text{Acol2}])$

$$\begin{pmatrix} -\frac{1}{CR} & \frac{1}{C} \\ -\frac{1}{CR^2} & -\frac{1}{CR} \end{pmatrix}$$

$\text{A} := \text{transpose}(\text{Atr})$

$$\begin{pmatrix} -\frac{1}{CR} & -\frac{1}{CR^2} \\ \frac{1}{C} & -\frac{1}{CR} \end{pmatrix}$$

$\text{X} := \text{matrix}([\text{iL}(t)], [\text{uC}(t)])$

$$\begin{pmatrix} \text{iL}(t) \\ \text{uC}(t) \end{pmatrix}$$

$\text{Ftr} := \text{coeff}(\text{rhsJednachineDiff}[i], \text{uC}(t)=0, \text{iL}(t), 0) \$ i = 1..2$

$$\frac{\text{ig}}{CR}, 0$$

$\text{F} := (\text{matrix}([\text{Ftr}]))$

$$\begin{pmatrix} \frac{\text{ig}}{CR} \\ 0 \end{pmatrix}$$

$\text{print}([\text{D}(\text{X})])$

$$\begin{pmatrix} \text{iL}(t) \\ \text{uC}(t) \end{pmatrix}'$$

MATLAB: MuPAD

$\text{print}(\text{D}(\text{X}), "=", \text{A}, ".", \text{X}, "+", \text{F})$

$$\begin{pmatrix} \text{iL}(t) \\ \text{uC}(t) \end{pmatrix}', "=", \begin{pmatrix} -\frac{1}{CR} & -\frac{1}{CR^2} \\ \frac{1}{C} & -\frac{1}{CR} \end{pmatrix}, ".", \begin{pmatrix} \text{iL}(t) \\ \text{uC}(t) \end{pmatrix}, "+", \begin{pmatrix} \frac{\text{ig}}{CR} \\ 0 \end{pmatrix}$$

$\text{Jednako} := \text{newDomain}(\text{"Jednako"}); \text{e1} := \text{new}(\text{Jednako}, 1);$

$\text{Jednako}::\text{print} := \text{x} \rightarrow "=";$

$\text{print}(\text{e1});$

$=$

$\text{Put} := \text{newDomain}(\text{"Put"}); \text{e2} := \text{new}(\text{Put}, 1);$

$\text{Put}::\text{print} := \text{x} \rightarrow ".";$

$\text{print}(\text{e2});$

$.$

$\text{Plus} := \text{newDomain}(\text{"Plus"}); \text{e3} := \text{new}(\text{Plus}, 1);$

$\text{Plus}::\text{print} := \text{x} \rightarrow "+";$

$\text{print}(\text{e3});$

$+$

$\text{myexprseq} := \text{funcenv}(\text{myexprseq}, \text{builtin}(1100, 20, "", \text{"myexprseq"}));$
 $\text{print}(\text{myexprseq}(\text{D}(\text{X}), \text{e1}, \text{A}, \text{e2}, \text{X}, \text{e3}, \text{F}));$

$$\begin{pmatrix} \text{iL}(t) \\ \text{uC}(t) \end{pmatrix}' = \begin{pmatrix} -\frac{1}{CR} & -\frac{1}{CR^2} \\ \frac{1}{C} & -\frac{1}{CR} \end{pmatrix} \cdot \begin{pmatrix} \text{iL}(t) \\ \text{uC}(t) \end{pmatrix} + \begin{pmatrix} \frac{\text{ig}}{CR} \\ 0 \end{pmatrix}$$

Одређивање индиционе функције и импулсног одзива

MATLAB: MuPAD

```
jednacine:={ig = i1 + iL,  
iL = iC + i2,  
u1 = uL + uC,  
uC = u2,  
u1 = R1 * i1,  
u2 = R2 * i2,  
uL = L * DiL,  
iC = C*DuC}
```


```
{u1 = uC + uL, uC = u2, iC = C DuC, uL = DiL L, u1 = R1 i1, u2 = R2 i2, iL = i2 + iC, ig = i1 + iL}
```

```
jednacineIzvoda:=groebner::eliminate(jednacine,{i1, i2, iC, u1, u2, uL})
```

```
[uC + R1 iL - R1 ig + DiL L, R2 iL - uC - C DuC R2, R1 R2 ig - R2 uC - DiL L R2 - R1 uC - C DuC R1 R2]
```

```
assume({R1, R2, C, L, R, t} in R_)
```
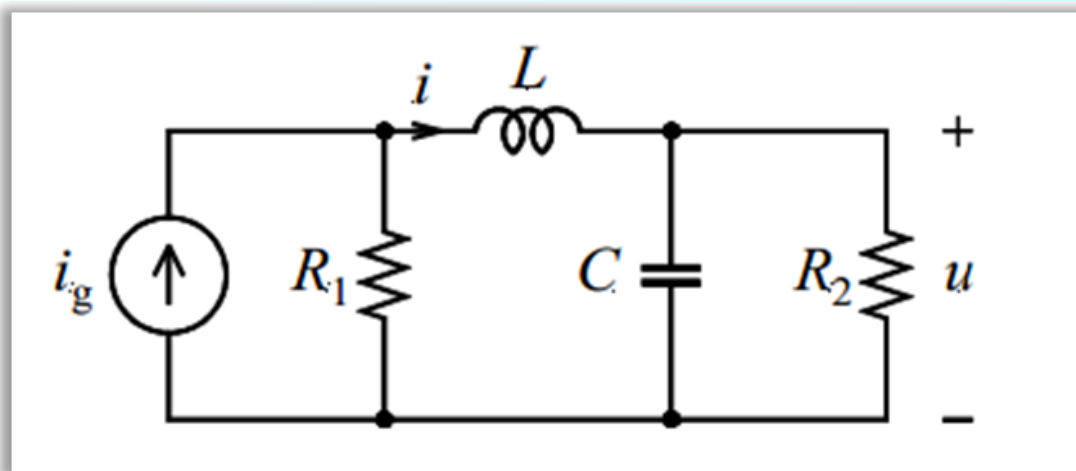
```
assumeAlso( R1>0 and R2>0 and C>0 and L>0 and R>0 )
```



jednacineStanje := solve(jednacineIzvoda, {DiL, DuC})

$$\left\{ \left[\text{DiL} = -\frac{uC + R1 \text{ iL} - R1 \text{ ig}}{L}, \text{DuC} = -\frac{uC - R2 \text{ iL}}{C R2} \right] \right\}$$

PromenljiveStanjaIzvodi := {uC=uC(t), iL=iL(t), DiL=D(iL)(t), DuC=D(uC)(t)}

$$\{ \text{iL} = \text{iL}(t), \text{uC} = \text{uC}(t), \text{DiL} = \text{iL}'(t), \text{DuC} = \text{uC}'(t) \}$$

zamene := {R1=R, R2=R, L=C*R^2, ig=heaviside(t)}

$$\{ R1 = R, R2 = R, \text{ig} = \text{heaviside}(t), L = C R^2 \}$$

JS:=jednacineStanje | PromenljiveStanjaIzvodi | zamene

$$\left\{ \left[\text{iL}'(t) = -\frac{uC(t) - R \text{ heaviside}(t) + R \text{ iL}(t)}{C R^2}, \text{uC}'(t) = -\frac{uC(t) - R \text{ iL}(t)}{C R} \right] \right\}$$

op(op(JS))

$$\text{iL}'(t) = -\frac{uC(t) - R \text{ heaviside}(t) + R \text{ iL}(t)}{C R^2}, \text{uC}'(t) = -\frac{uC(t) - R \text{ iL}(t)}{C R}$$

JSpocetveVrednosti := {op(op(JS)), uC(0)=0, iL(0)=0}

$$\left\{ \text{uC}'(t) = -\frac{uC(t) - R \text{ iL}(t)}{C R}, \text{iL}'(t) = -\frac{uC(t) - R \text{ heaviside}(t) + R \text{ iL}(t)}{C R^2}, \text{iL}(0) = 0, \text{uC}(0) = 0 \right\}$$

`odziv := ode::solve(JSpocetveVrednosti, {uC(t), iL(t)})`

$$\left\{ \left[u_C(t) = \frac{R \operatorname{heaviside}(t)}{2} - \frac{R \sigma_1 \sigma_3 \operatorname{heaviside}(t)}{2} - \frac{R \sigma_1 \sigma_2 \operatorname{heaviside}(t)}{2}, i_L(t) = \frac{\operatorname{heaviside}(t)}{2} - \frac{\sigma_1 \sigma_3 \operatorname{heaviside}(t)}{2} + \frac{\sigma_1 \sigma_2 \operatorname{heaviside}(t)}{2} \right] \right\}$$

where

$$\sigma_1 = e^{-\frac{t}{C R}}$$

$$\sigma_2 = \sin\left(\frac{t}{C R}\right)$$

$$\sigma_3 = \cos\left(\frac{t}{C R}\right)$$

`f(t):=(uC(t) | (odziv))` **Индициона функција**

$$\frac{R \operatorname{heaviside}(t)}{2} - \frac{R e^{-\frac{t}{C R}} \cos\left(\frac{t}{C R}\right) \operatorname{heaviside}(t)}{2} - \frac{R e^{-\frac{t}{C R}} \sin\left(\frac{t}{C R}\right) \operatorname{heaviside}(t)}{2}$$

`g(t):=simplify(diff(f(t),t))` **Импулсни одзив**

$$\frac{e^{-\frac{t}{C R}} \sin\left(\frac{t}{C R}\right) \operatorname{heaviside}(t)}{C}$$

$f(t):=(uC(t) \mid (\text{odziv}))$

$$\frac{R \operatorname{heaviside}(t)}{2} - \frac{R e^{-\frac{t}{CR}} \cos\left(\frac{t}{CR}\right) \operatorname{heaviside}(t)}{2} - \frac{R e^{-\frac{t}{CR}} \sin\left(\frac{t}{CR}\right) \operatorname{heaviside}(t)}{2}$$


$g(t):=\text{simplify}(\text{diff}(f(t),t))$

$$\frac{e^{-\frac{t}{CR}} \sin\left(\frac{t}{CR}\right) \operatorname{heaviside}(t)}{C}$$

$\text{zamena}:=\{R=1e3, C=1e-6\}$

$\{R = 1000.0, C = 0.000001\}$



$\text{plot}(g(t)|\text{zamena}, t=0..0.01)$

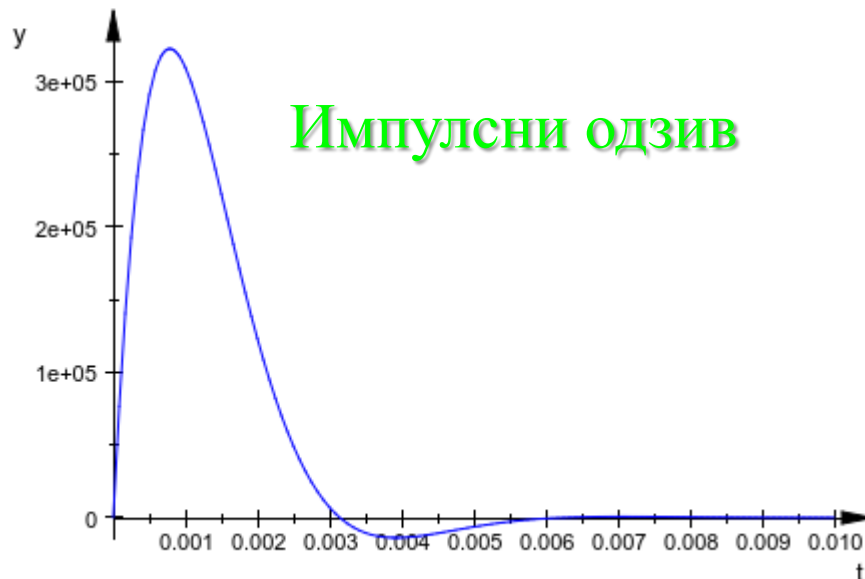


MATLAB: MuPAD

MATLAB: Simulink

Sources

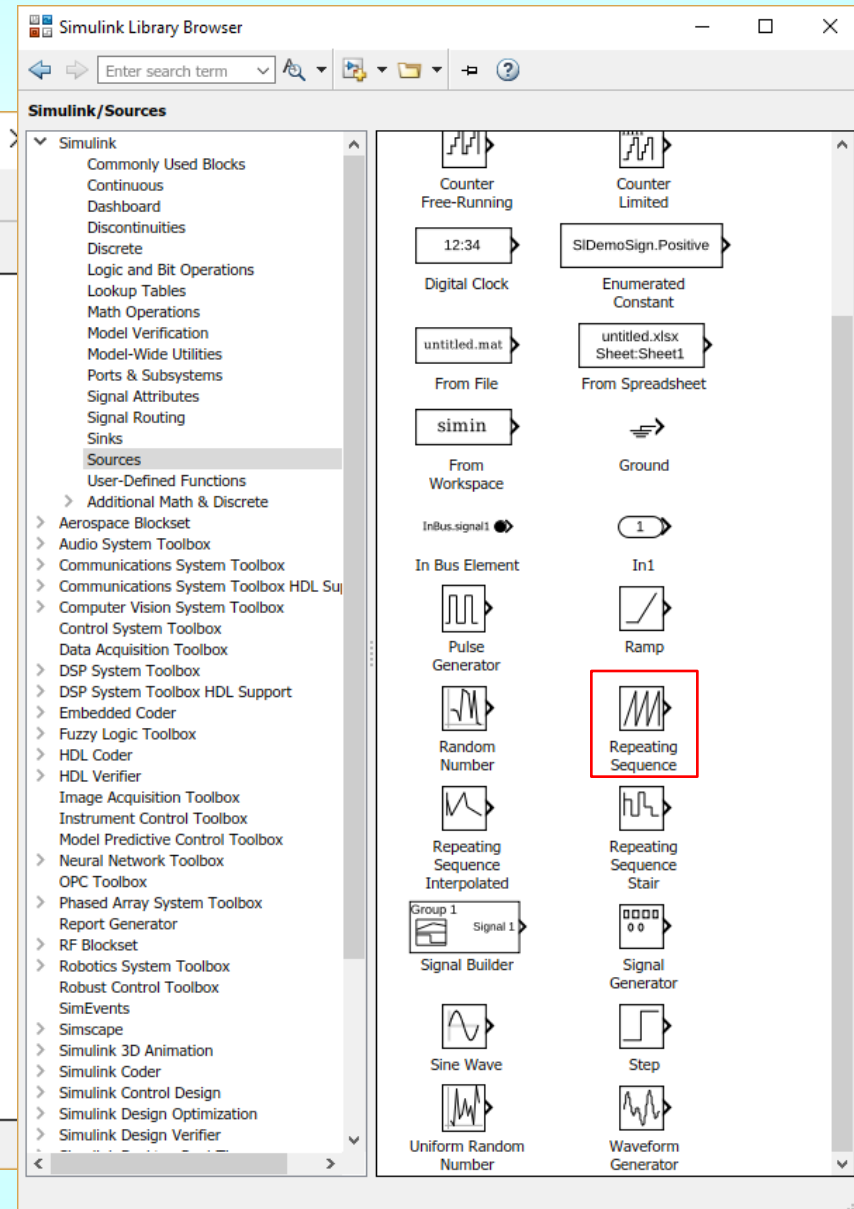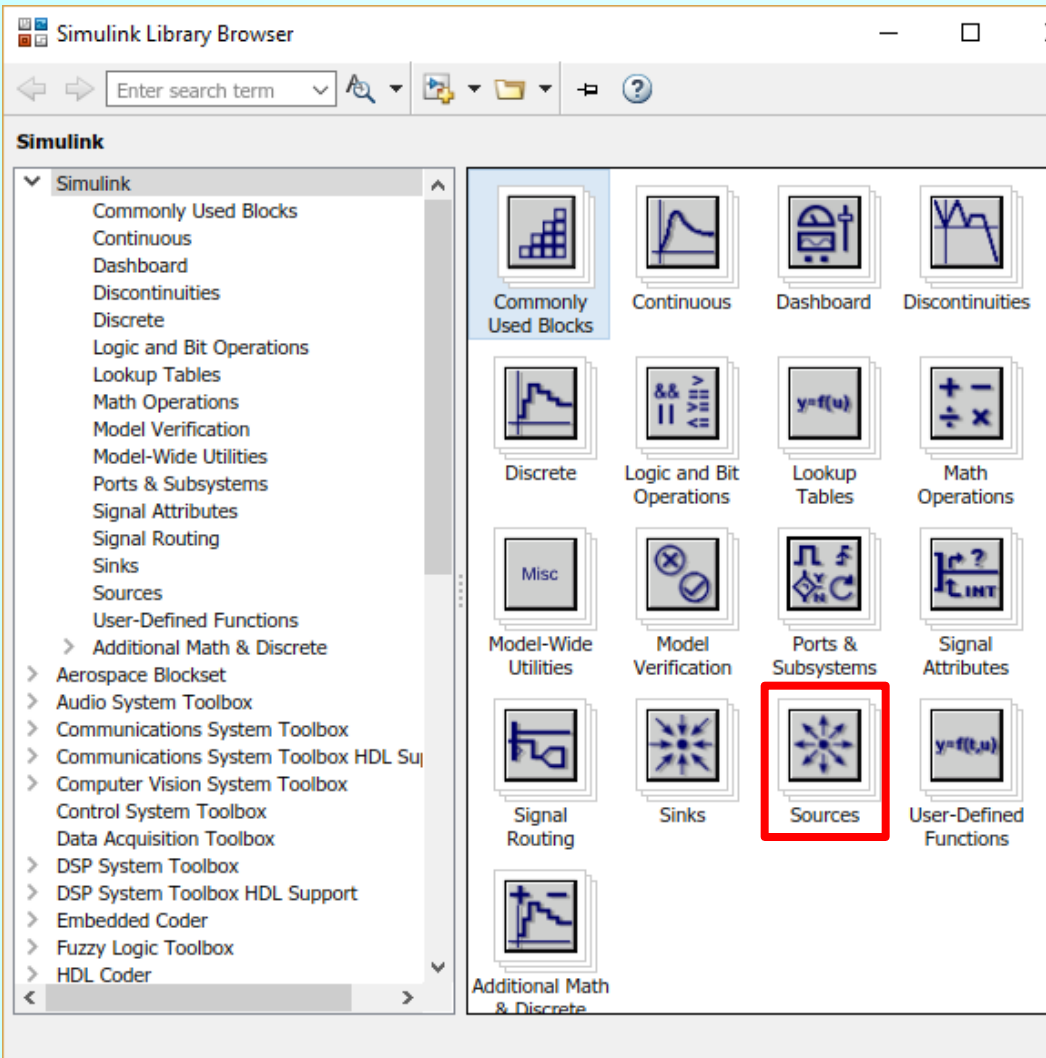

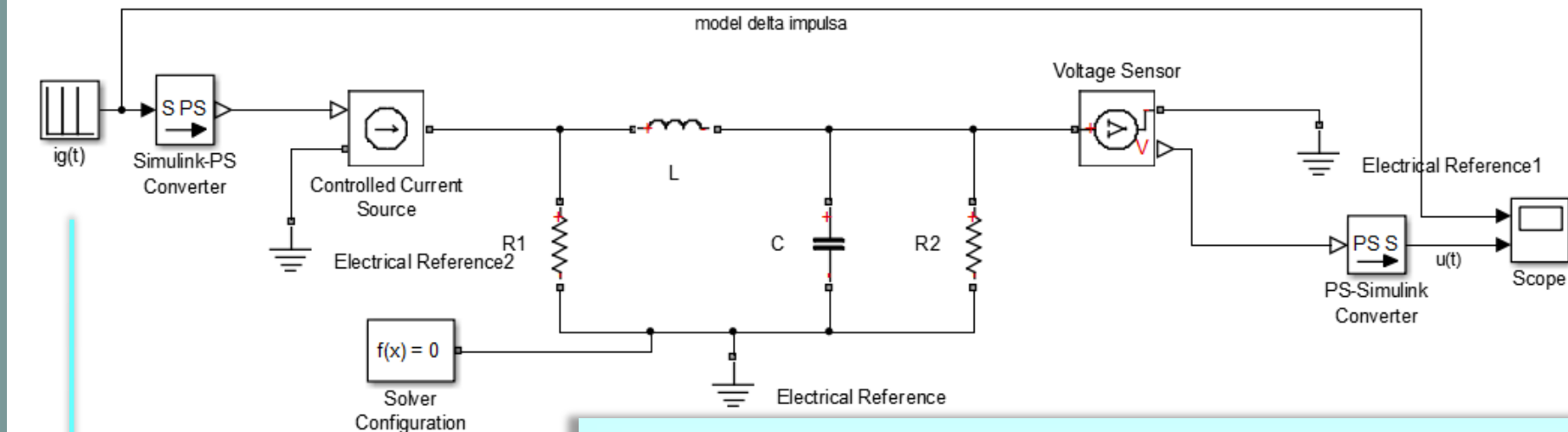




Импулсни одзив за напон кондензатора $u(t)$

$$R_1 = R_2 = R = 1 \text{ k}\Omega$$


$$L = 1 \text{ H}$$


$$C = 1 \text{ }\mu\text{F}$$

$$i_g(t) = \delta(t)$$

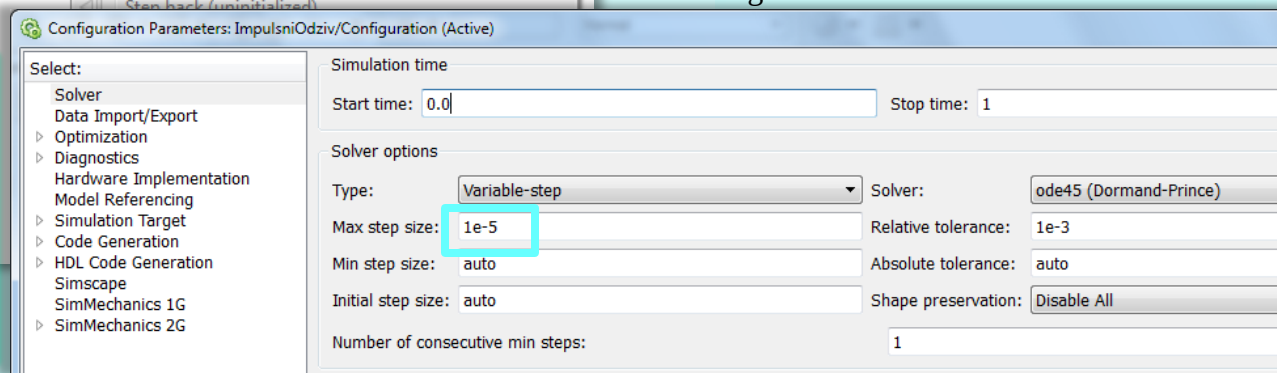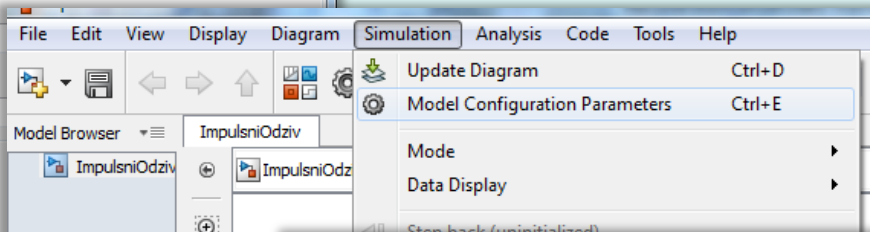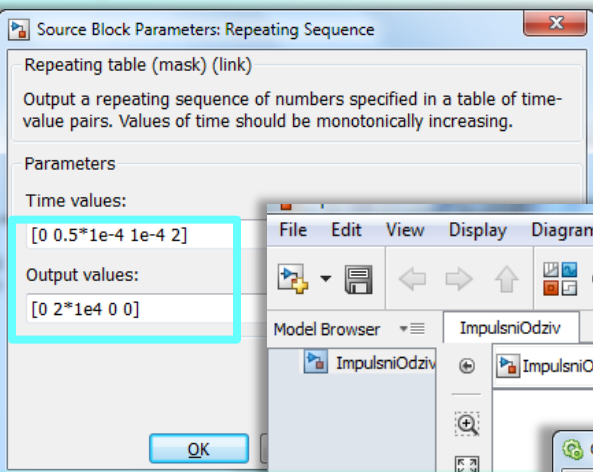

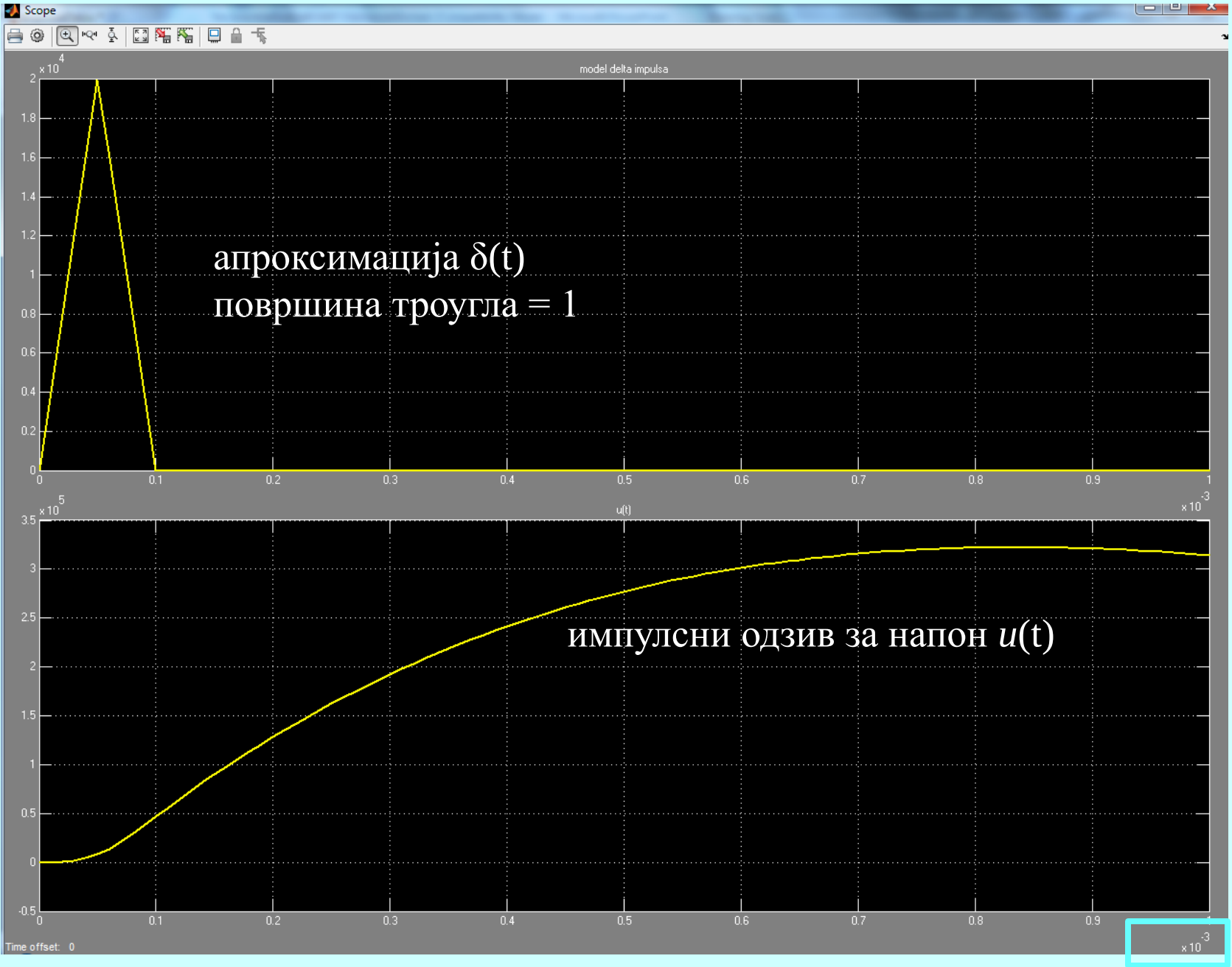
**MATLAB: Simscape
Foundation Library
Utilities
Simulink**



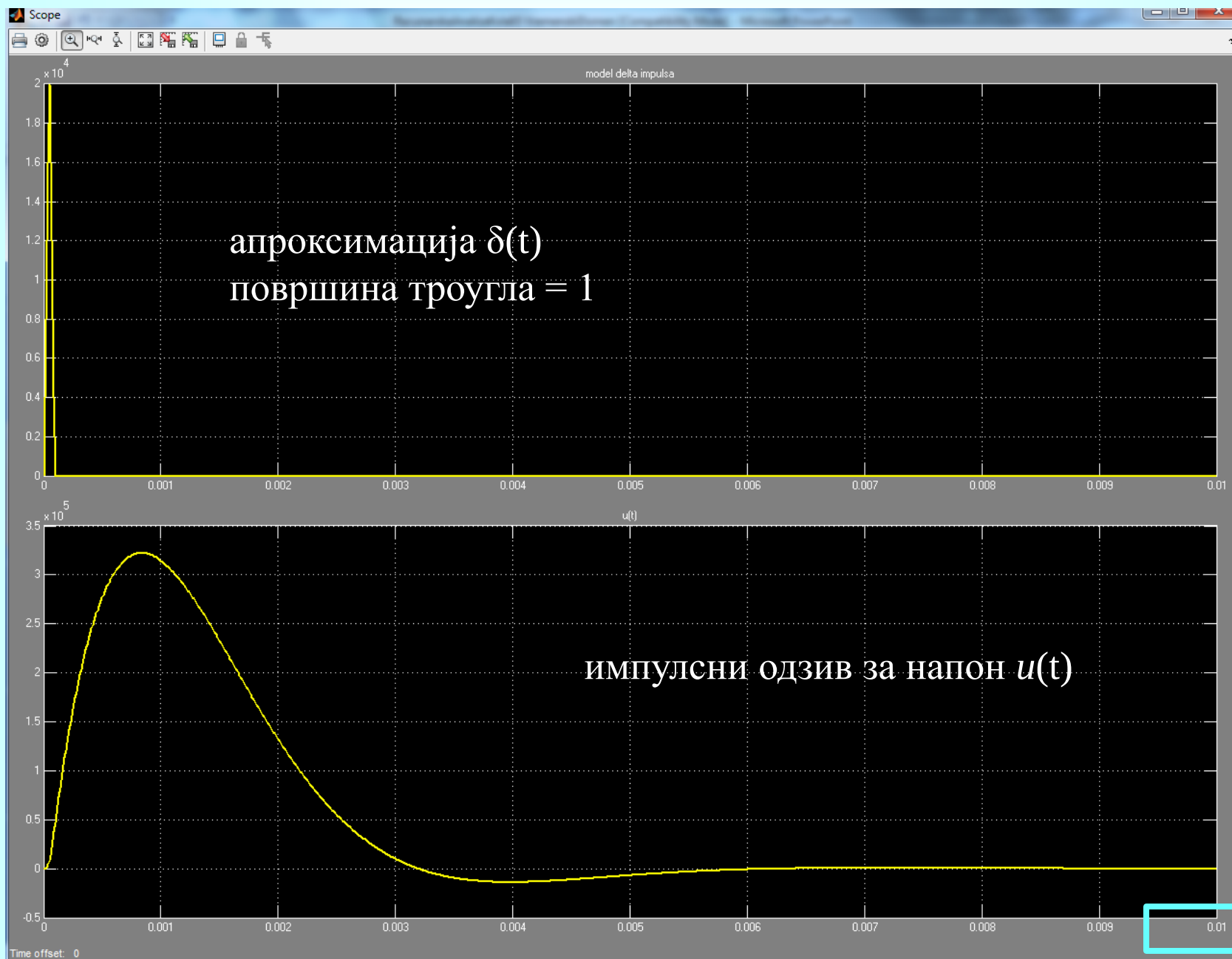


Одзив на сакупљену енергију

$$t_0 = 0$$


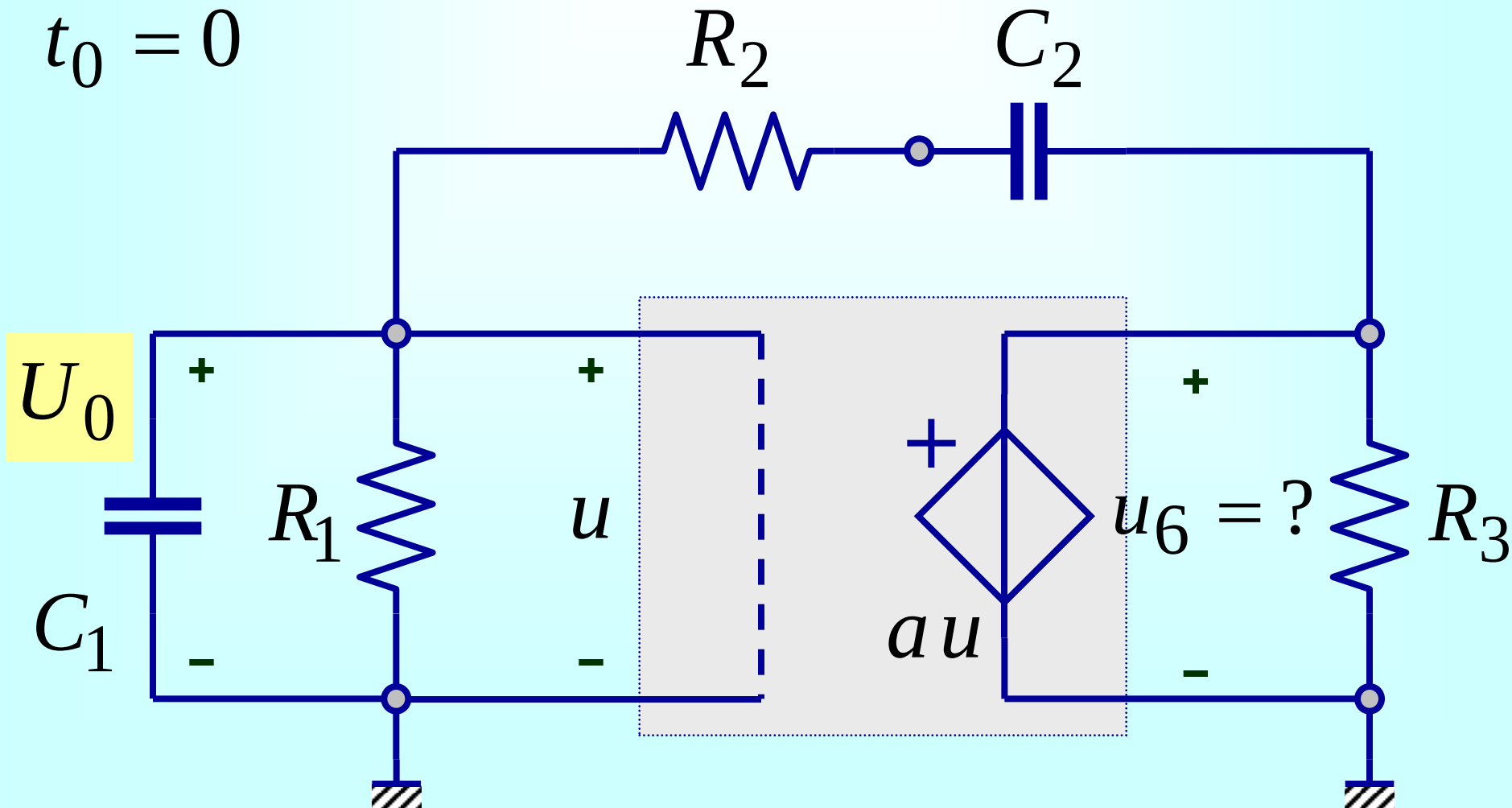


$$t > t_0$$

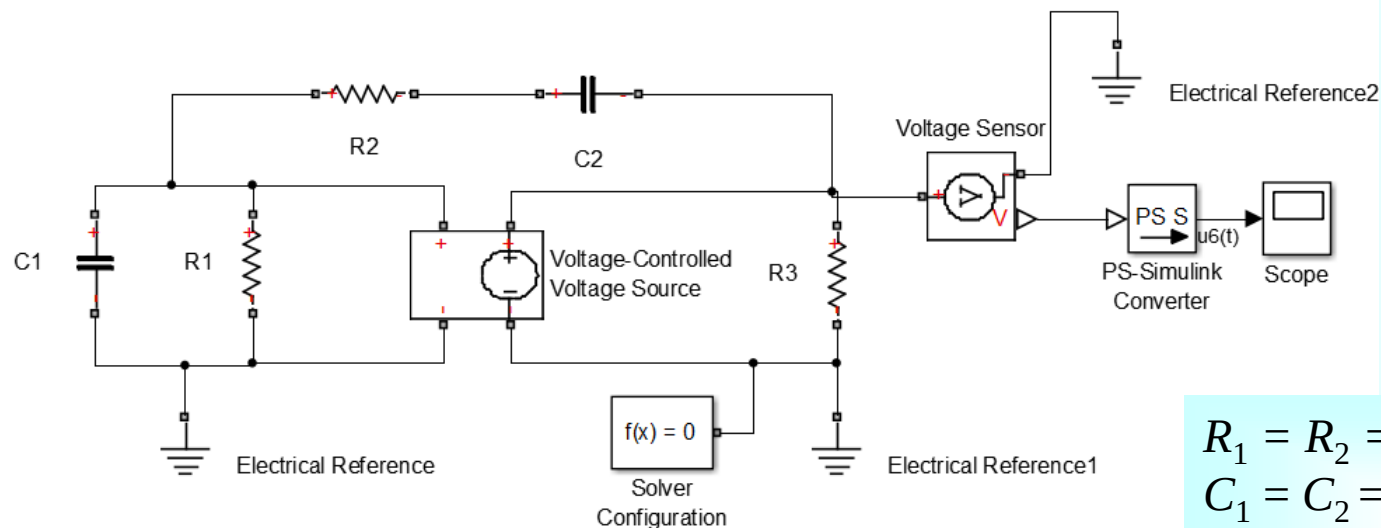
MATLAB: Simscape Foundation Library, Utilities, Simulink



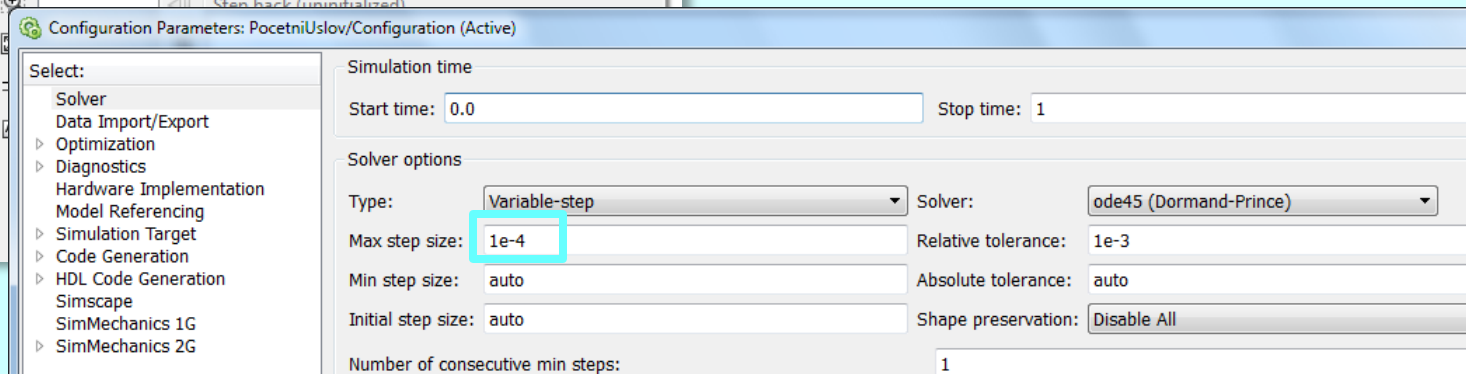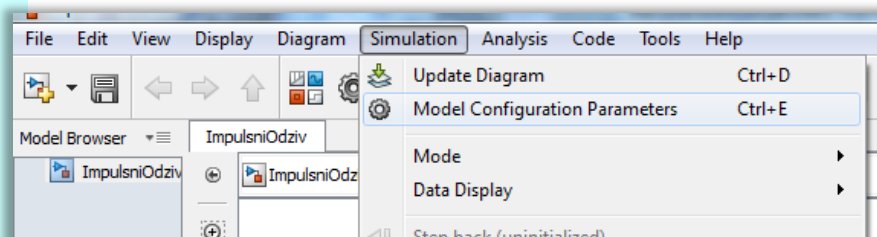
$$\begin{aligned} R_1 &= R_2 = R = 1 \text{ k}\Omega \\ C_1 &= C_2 = 1 \text{ }\mu\text{F} \\ U_0 &= 10 \text{ V} \\ a &= 3 \end{aligned}$$


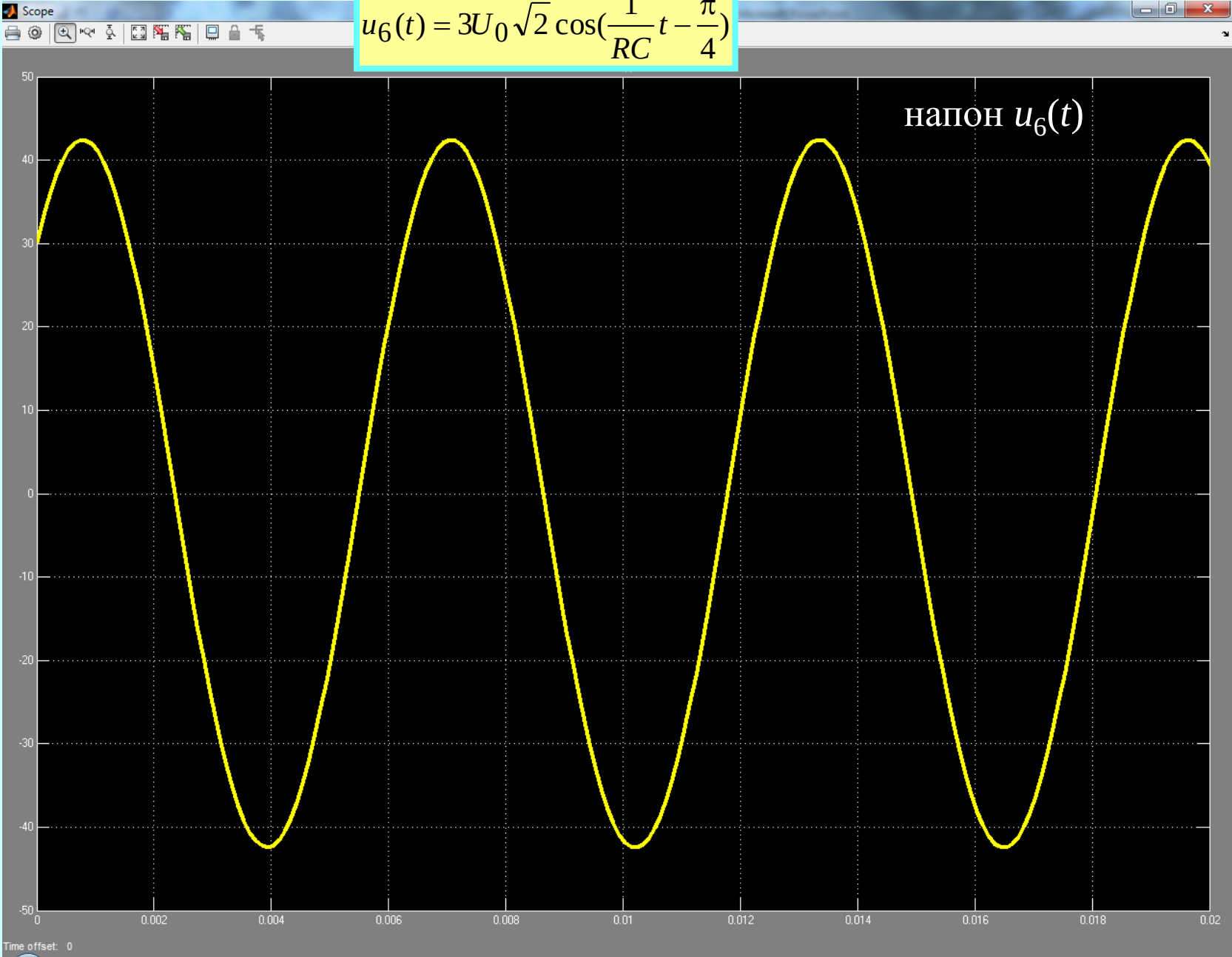
$$u_6(t) = 3U_0\sqrt{2} \cos\left(\frac{1}{RC}t - \frac{\pi}{4}\right)$$



Ознаке чворова и приступа

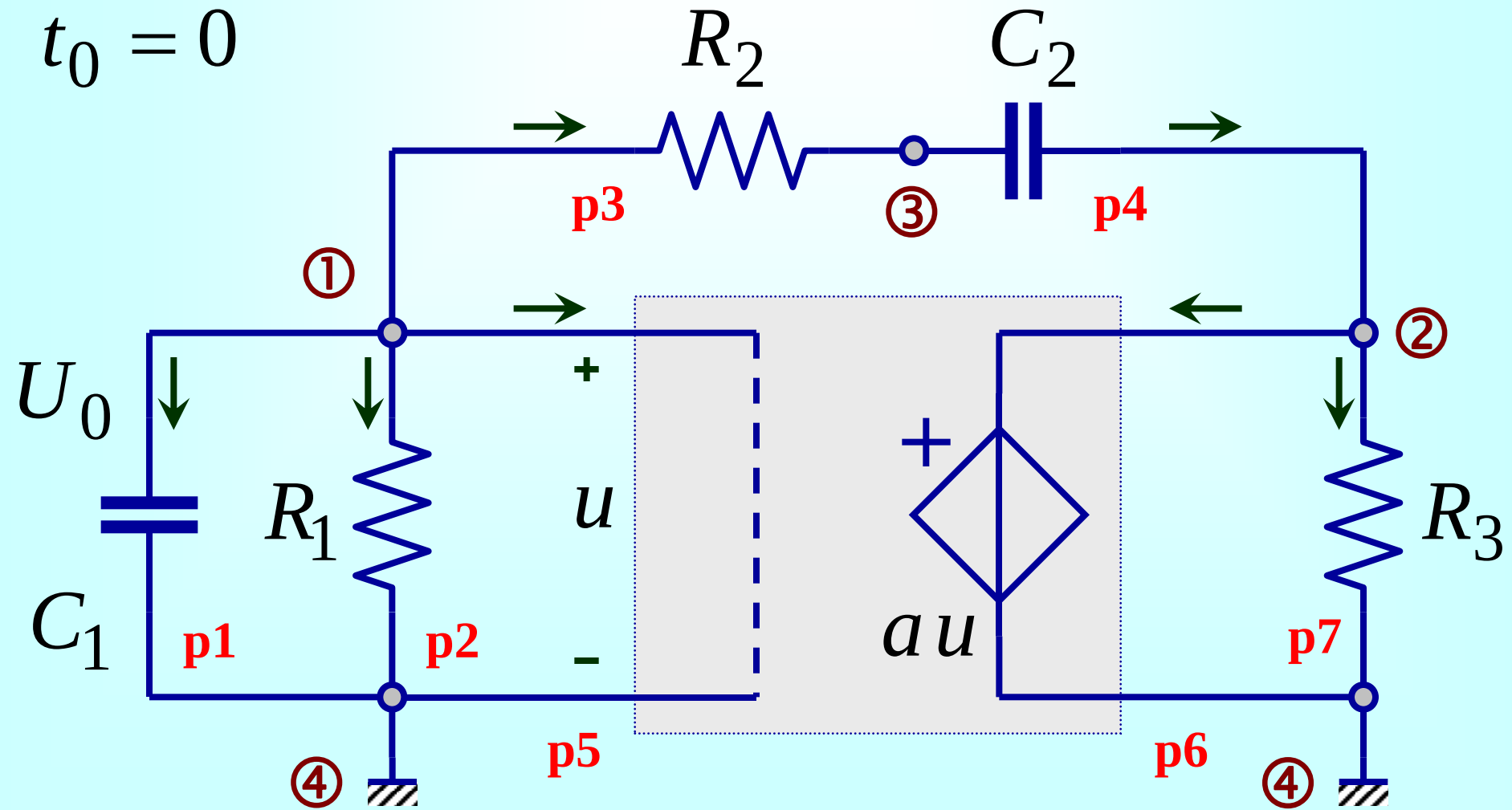

MATLAB: MuPAD


Систем једначина кола

JednacineStanja_VinovOscillator* - MuPAD

File Edit View Navigation Insert Format Notebook Window Help

Generic Serif 18 B I U X2
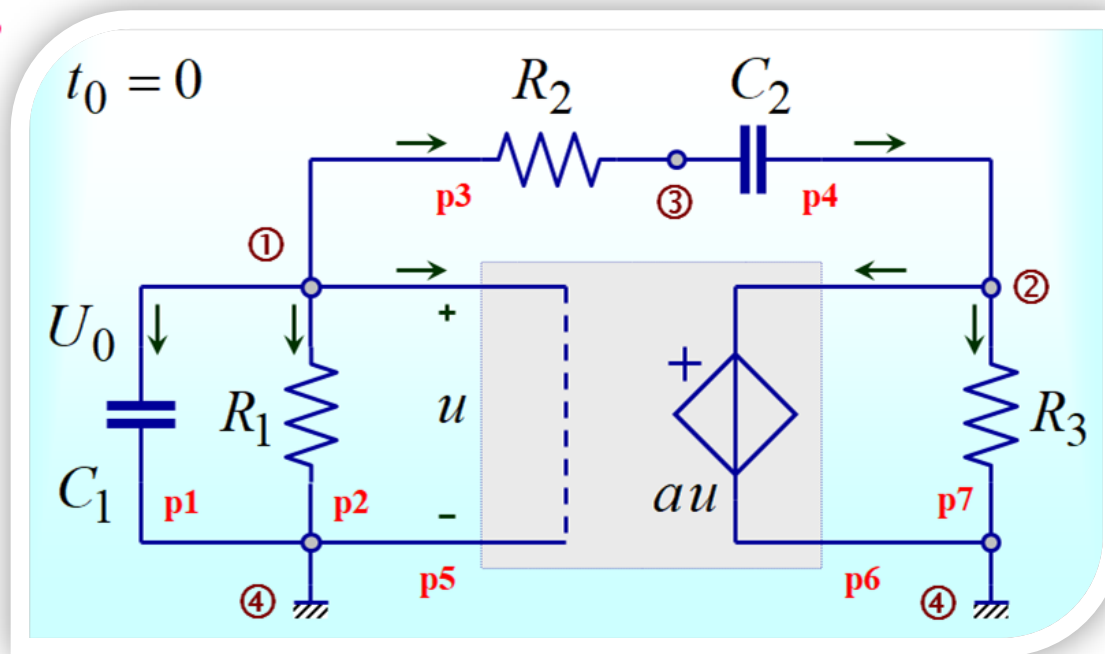
```
jednacine:={i1 + i2 + i3 + i5 = 0,
-i4 + i6 + i7 = 0,
-i3 + i4 = 0,
u1 - u2 = 0,
u2 - u5 = 0,
u5 - u6 - u4 - u3 = 0,
u6 - u7 = 0,
i1 = C1 * Du1,
u2 = R1 * i2,
u3 = R2 * i3,
i4 = C2 * Du4,
i5 = 0,
u6 = a*u5,
u7 = R3*i7}
```



```
{u1 - u2 = 0, u2 - u5 = 0, u6 - u7 = 0, u6 = a u5, i6 - i4 + i7 = 0, i1 + i2 + i3 + i5 = 0,
i1 = C1 Du1, i4 = C2 Du4, u5 - u4 - u3 - u6 = 0, i5 = 0, u2 = R1 i2, u3 = R2 i3,
u7 = R3 i7, i4 - i3 = 0}
```

MATLAB: MuPAD

Једначине стања

```
jednacineIzvoda:=groebner::eliminate(jednacine,{i1, i2, i3, i4, i5, i6, i7, u2, u3, u5, u6, u7})  
[u1 + C1 Du1 R1 + C2 Du4 R1, u4 - u1 + a u1 + C2 Du4 R2]  
  
assume({R1, R2, R3, C1, C2, a, t} in R_)  
assumeAlso( R1>0 and R2>0 and R3>0 and C1>0 and C2>0 and a>0)  
jednacineStanje := solve(jednacineIzvoda, {Du1, Du4})  
  
 $\left\{ \left[ Du1 = - \frac{R1 u1 + R2 u1 - R1 u4 - R1 a u1}{C1 R1 R2}, Du4 = - \frac{u4 - u1 + a u1}{C2 R2} \right] \right\}$ 
```

PromenljiveStanjaIzvodi:={u1=u1(t), u4=u4(t), Du1=D(u1)(t), Du4=D(u4)(t)}

$$\{u1 = u1(t), u4 = u4(t), Du1 = u1'(t), Du4 = u4'(t)\}$$

zamene := {R1=R, R2=R, R3=R, C1=C, C2=C, a=3}

$$\{R1 = R, R2 = R, R3 = R, a = 3, C1 = C, C2 = C\}$$

JS:=jednacineStanje | PromenljiveStanjaIzvodi | zamene

$$\left\{ \left[u1'(t) = \frac{R u1(t) + R u4(t)}{C R^2}, u4'(t) = - \frac{2 u1(t) + u4(t)}{C R} \right] \right\}$$

op(JS)

$$\left[u1'(t) = \frac{R u1(t) + R u4(t)}{C R^2}, u4'(t) = - \frac{2 u1(t) + u4(t)}{C R} \right]$$

op(op(JS))

$$u1'(t) = \frac{R u1(t) + R u4(t)}{C R^2}, u4'(t) = - \frac{2 u1(t) + u4(t)}{C R} \quad \Bigg|$$

JS pocetneVrednosti:={op(op(JS)), u1(0)=10, u4(0)=0}

$$\left\{ u4'(t) = - \frac{2 u1(t) + u4(t)}{C R}, u1'(t) = \frac{R u1(t) + R u4(t)}{C R^2}, u4(0) = 0, u1(0) = 10 \right\}$$

MATLAB: MuPAD

Одзив – напон $u_6(t)$

```
odziv := ode::solve(JSpocetveVrednosti, {u1(t), u4(t)})
```

$$\left\{ \left[u_4(t) = -10 e^{-\frac{t i}{C R}} i + 10 e^{\frac{t i}{C R}} i, u_1(t) = e^{-\frac{t i}{C R}} (5 + 5 i) + e^{\frac{t i}{C R}} (5 - 5 i) \right] \right\}$$

```
Simplify(u1(t)|odziv)
```

$$10 \sqrt{2} \sin\left(\frac{\pi}{4} + \frac{t}{C R}\right)$$

```
u6(t):=Simplify(3*u1(t)|odziv)
```

$$30 \sqrt{2} \sin\left(\frac{\pi}{4} + \frac{t}{C R}\right)$$


```
zamena:={R=1000, C=1e-6}
```

$$\{R = 1000, C = 0.000001\}$$

```
u6_zam(t):=Simplify(u6(t) | odziv | zamena)
```

$$42.42640687 \cos(1000.0 t - 0.7853981634)$$

```
plot(u6_zam(t), t=0..0.02)
```

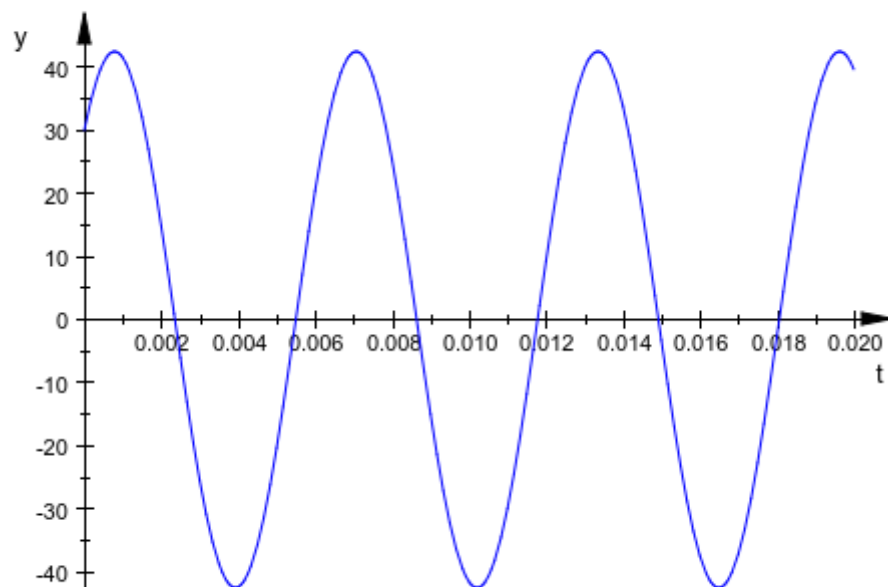


Одзив на побуду и сакупљену енергију

$$t_0 = 0$$

$$R_1 = R_2 = R$$



$$R_3 = 2R$$

$$i_g = I_g e^{-at} h(t)$$

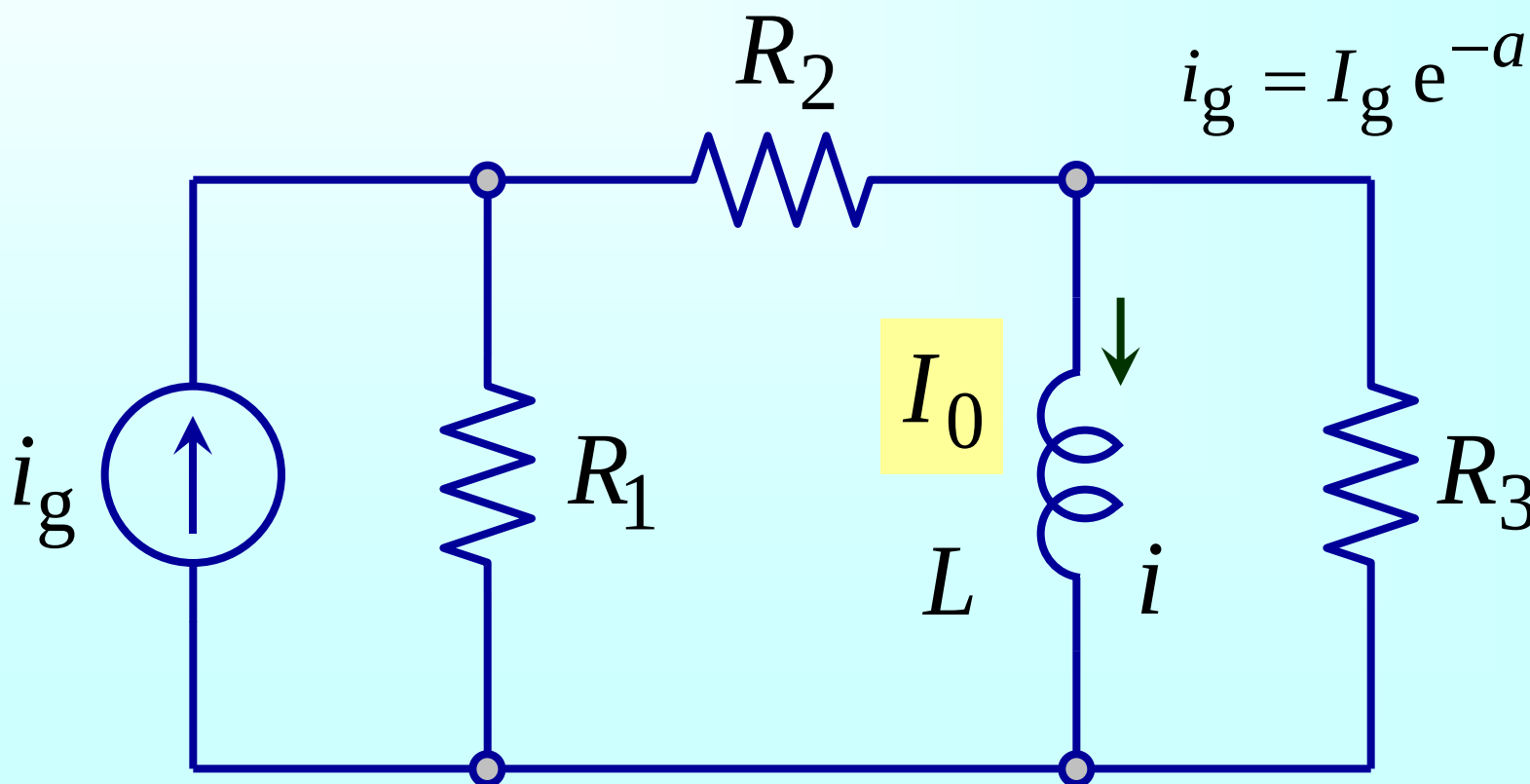


MATLAB: Simulink

Sources

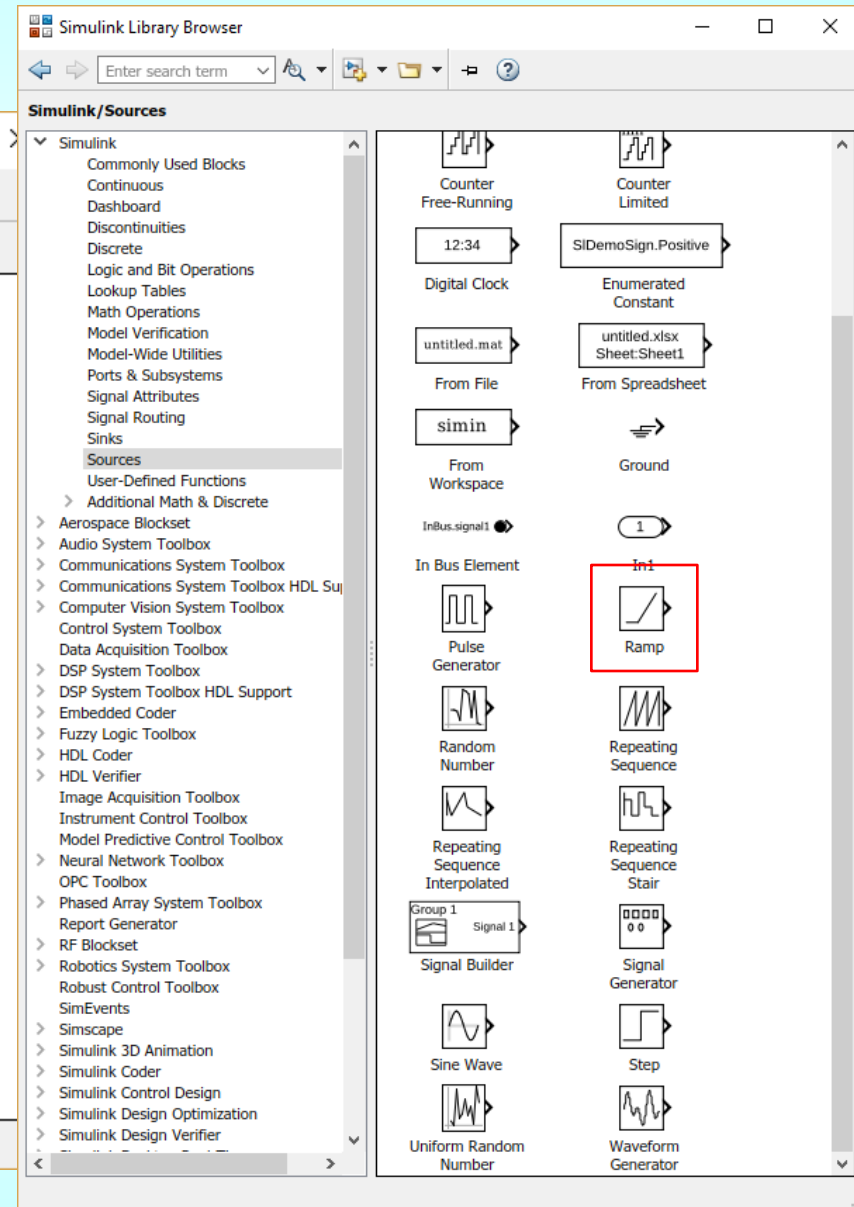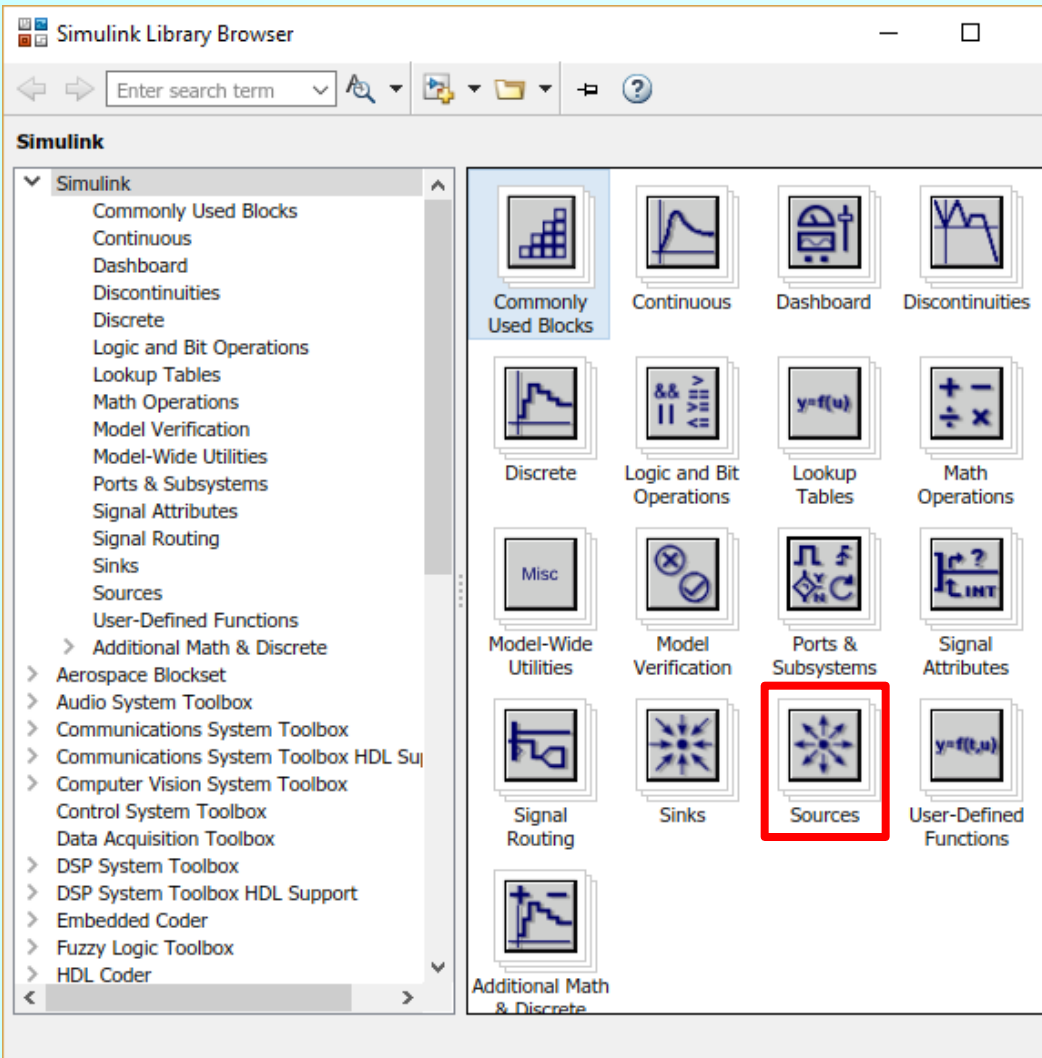


MATLAB: Simulink

Math Operations

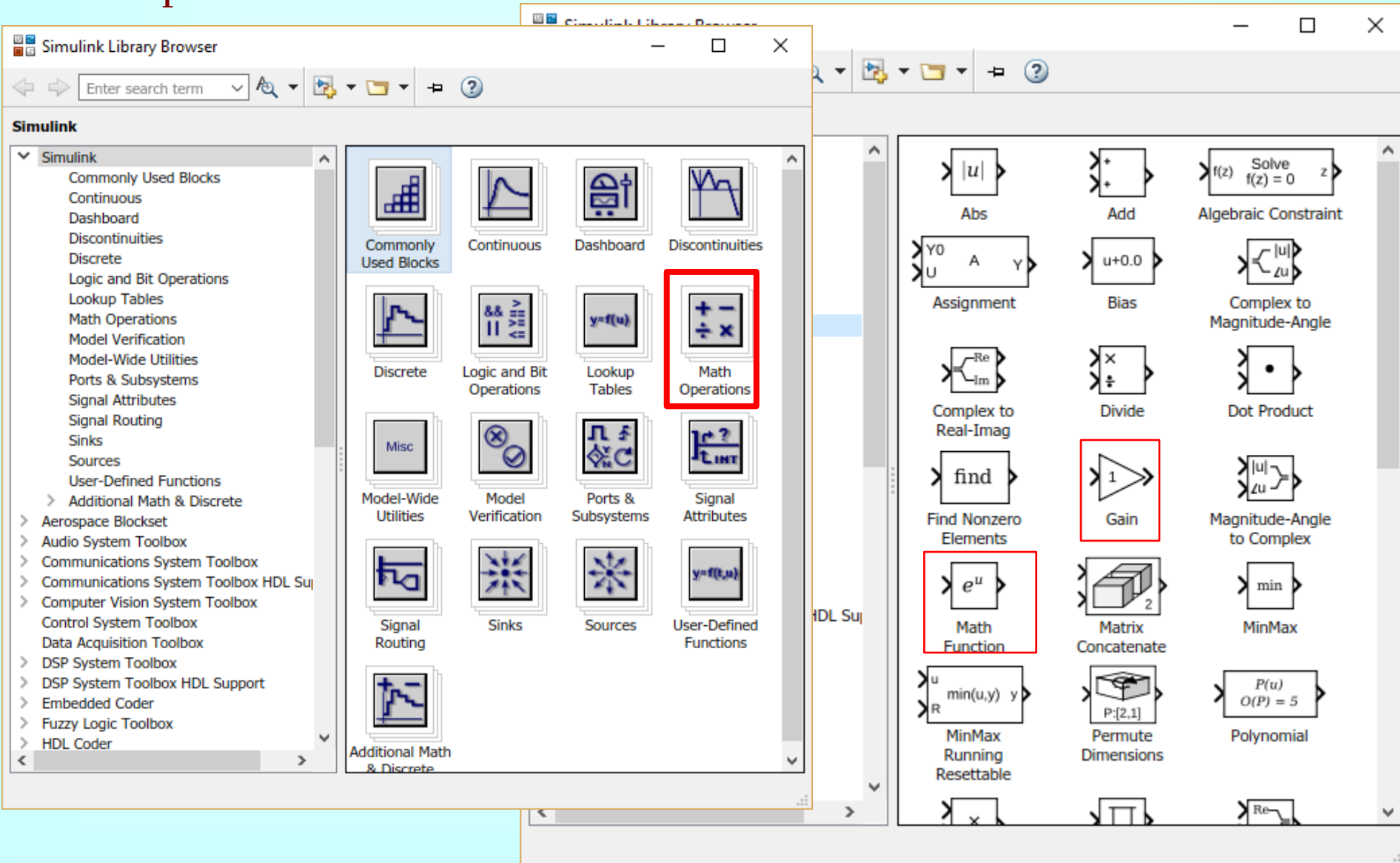

$t > t_0, \quad t_0 = 0$

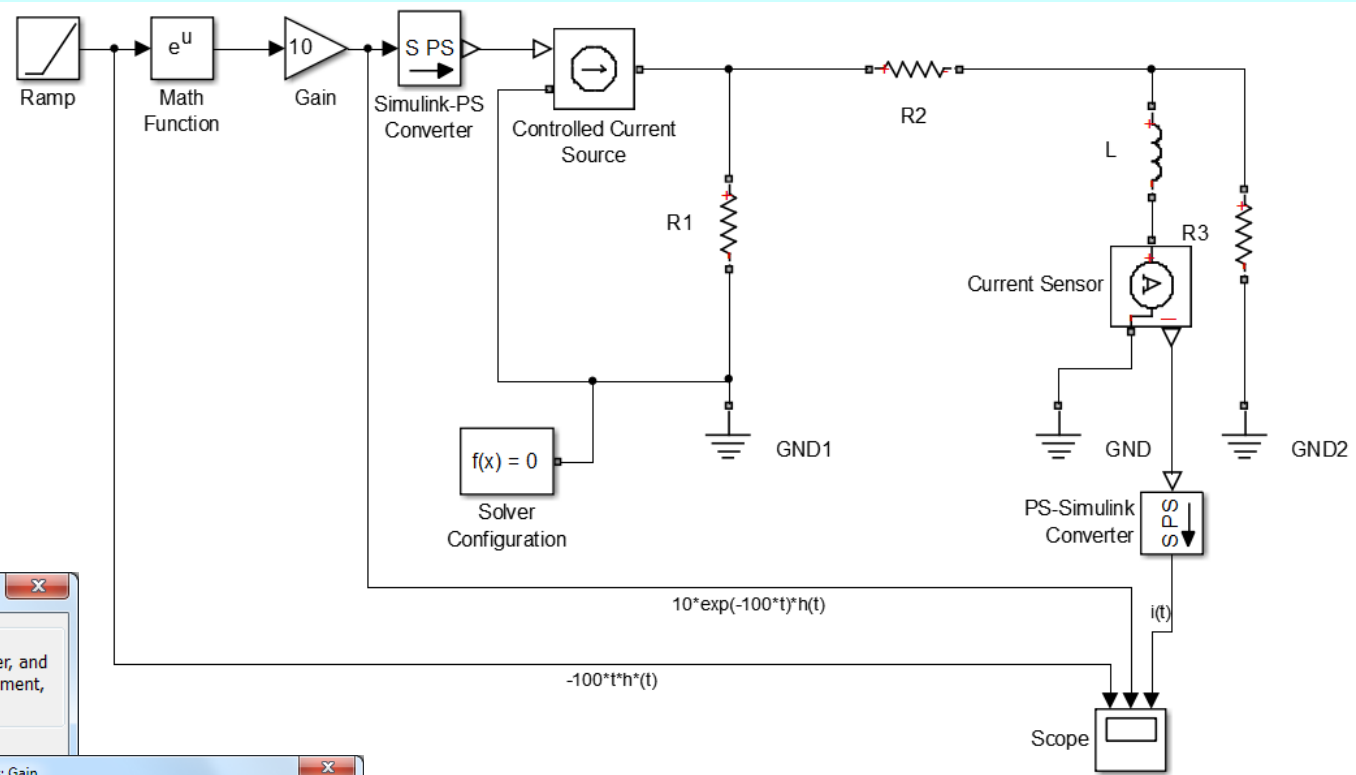

$R_1 = R_2 = R = 1\text{k}\Omega, R_3 = 2R, L = 1\text{mH}$
 $i_g(t) = I_g e^{-at} h(t), I_g = 10\text{ A}, a = 100$
 $i(0^-) = I_0 = -10\text{ A}$

MATLAB: Simscape
Foundation Library
Utilities
Simulink

Source Block Parameters: Ramp

Ramp (mask) (link)

Output a ramp signal starting at the specified time.

Parameters

Slope:

-100

Start time:

0

Initial output:

0

☒ Interpret vector parameters as 1-D

Function Block Parameters: Math Function

Math

Mathematical functions including logarithmic, exponential, power, and modulus functions. When the function has more than one argument, the first argument corresponds to the top (or left) input port.

Main

Signal Attributes

Function:

exp

Output sig

log

10^u

log10

magnitude^2

square

pow

conj

reciprocal

hypot

rem

mod

Function Block Parameters: Gain

Gain

Element-wise gain (y = K.*u) or matrix gain (y = K*u or y = u*K).

Main

Signal Attributes

Parameter Attributes

Gain:

10

Multiplication:

Element-wise(K.*u)

Sample time (-1 for inherited):

-1

Configuration Parameters: PocetniUslovPobuda/Configuration (Active)

Select:

- Solver
- Data Import/Export
- Optimization
- Diagnostics
- Hardware Implementation
- Model Referencing
- Simulation Target
- Code Generation
- HDL Code Generation
- Simscape
- SimMechanics 1G
- SimMechanics 2G

Simulation time

Start time: 0.0

Stop time: 0.1

Solver options

Type: Variable-step

Solver: ode45 (Dormand-Prince)

Max step size: 1e-7


Relative tolerance: 1e-3

Min step size: auto


Absolute tolerance: auto

Initial step size: auto

Shape preservation: Disable All

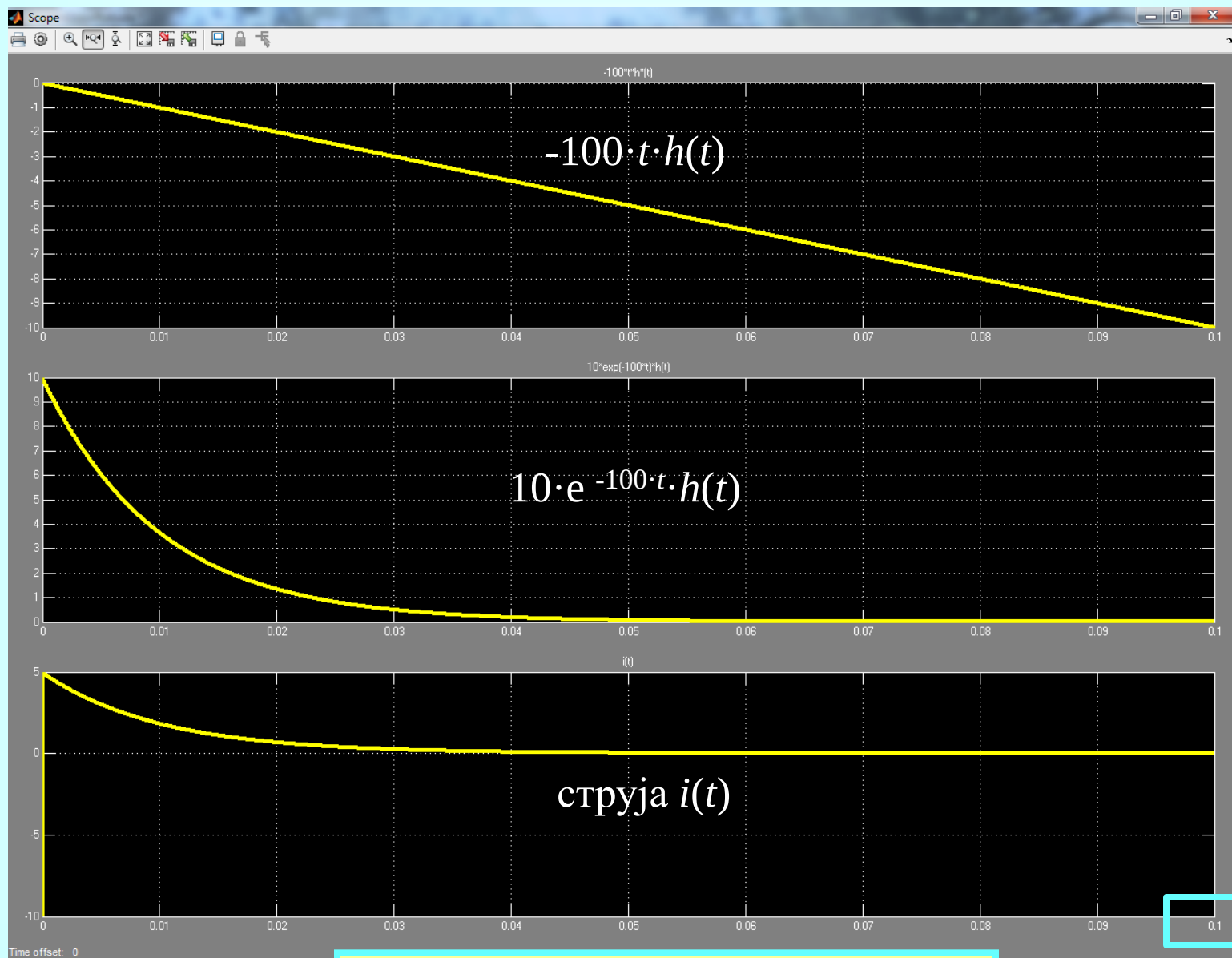
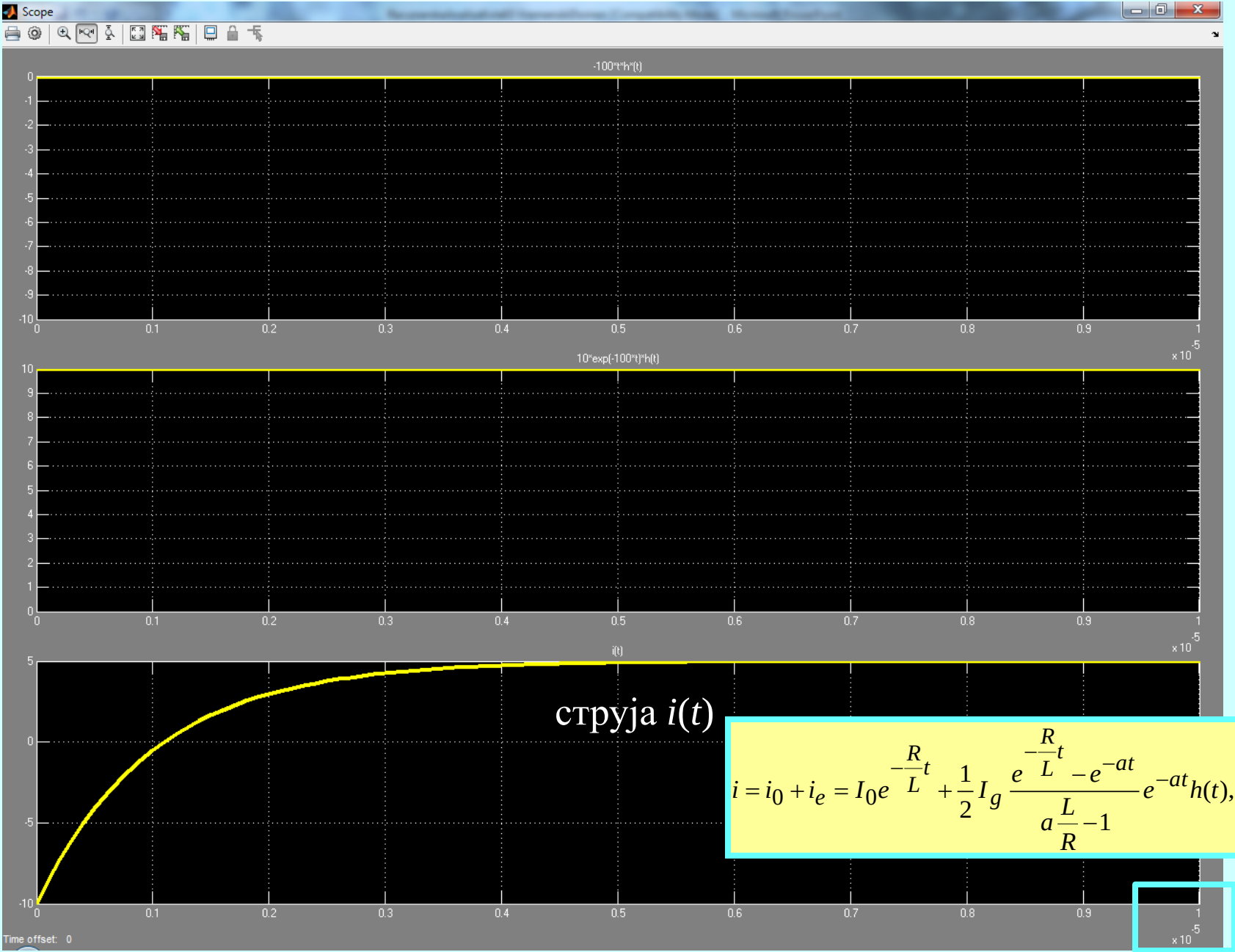
$$i(t) = i_0 + i_e = I_0 e^{-\frac{R}{L}t} + \frac{1}{2} I_g \frac{e^{-\frac{R}{L}t} - e^{-at}}{a \frac{L}{R} - 1} e^{-at} h(t), a \neq \frac{R}{L}$$




Коло са побудом и почет. енер.

$$t_0 = 0$$

$$i_g = I_g e^{-at} \mathfrak{V}(t)$$

$$R_1 = R_2 = R$$

$$R_3 = 2R$$

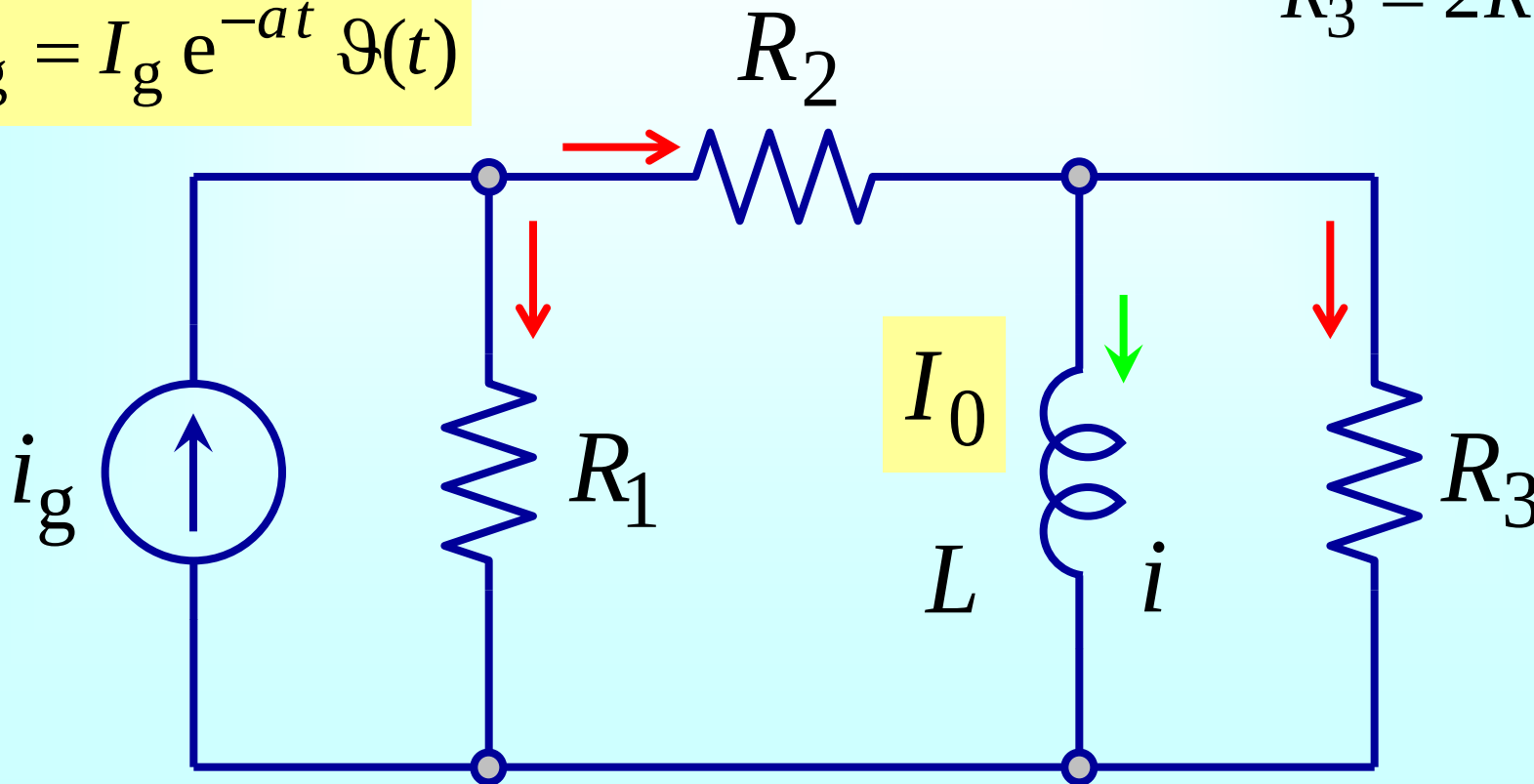

Систем једначина кола

```
jednacine:={iR1 + iR2 - ig = 0,
-iR2 + i + iR3 = 0,
uR1 - uL - uR2= 0,
uL - uR3 = 0,
uL = L *Di,
uR1 = R1 * iR1,
uR2 = R2 * iR2,
uR3 = R3 * iR3}
```

```
{uL - uR3 = 0, i - iR2 + iR3 = 0, iR1 + iR2 - ig = 0, uL = Di L, uR1 - uL - uR2 = 0,
uR1 = R1 iR1, uR2 = R2 iR2, uR3 = R3 iR3}
```

```
jednacineIzvoda:=groebner::eliminate(jednacine,{iR1, iR2, iR3, uR1, uR2, uR3, uL})
```

```
[R1 R3 ig - Di L R2 - Di L R3 - R1 R3 i - R2 R3 i - Di L R1]
```

```
assume({R1, R2, R3, L, t} in R_)
```

```
assumeAlso( R1>0 and R2>0 and R3>0 and L>0)
```

```
jednacineStanje := solve(jednacineIzvoda, {Di})
```


```
{ [Di = - (R1 R3 i + R2 R3 i - R1 R3 ig) / (L R1 + L R2 + L R3) ] }
```

$t_0 = 0$

$$i_g = I_g e^{-at} \mathfrak{I}(t)$$

$$R_1 = R_2 = R$$

$$R_3 = 2R$$

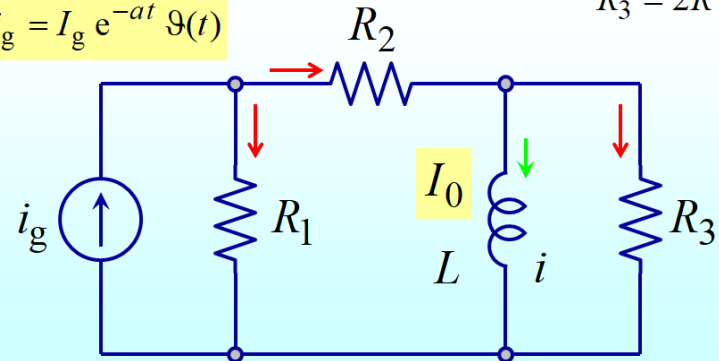

MATLAB: MuPAD

PromenljiveStanjaIzvodi:={i=i(t), Di=D(i)(t)}

$$\{i = i(t), Di = i'(t)\}$$

zamene := {R1=R, R2=R, R3=2*R, ig=Ig*exp(-a*t)*heaviside(t)}

$$\{R1 = R, R2 = R, R3 = 2 R, ig = Ig e^{-a t} \text{heaviside}(t)\}$$

JS:=jednacineStanje | PromenljiveStanjaIzvodi | zamene

$$\left\{ \left[i'(t) = - \frac{4 R^2 i(t) - 2 Ig R^2 e^{-a t} \text{heaviside}(t)}{4 L R} \right] \right\}$$

op(JS)

$$\left[i'(t) = - \frac{4 R^2 i(t) - 2 Ig R^2 e^{-a t} \text{heaviside}(t)}{4 L R} \right]$$

op(op(JS))

$$i'(t) = - \frac{4 R^2 i(t) - 2 Ig R^2 e^{-a t} \text{heaviside}(t)}{4 L R}$$

JSpocetveVrednosti:={op(op(JS)), i(0)=I0}

$$\left\{ i(0) = I0, i'(t) = - \frac{4 R^2 i(t) - 2 Ig R^2 e^{-a t} \text{heaviside}(t)}{4 L R} \right\}$$

Одзив – струја $i(t)$

$\text{JSpocetveVrednosti} := \{\text{op}(\text{op}(\text{JS})), i(0)=I_0\}$

$$\left\{ i(0) = I_0, i'(t) = - \frac{4 R^2 i(t) - 2 I_g R^2 e^{-a t} \text{heaviside}(t)}{4 L R} \right\}$$

$\text{odziv} := \text{ode}::\text{solve}(\text{JSpocetveVrednosti}, \{i(t)\})$

$$\left\{ I_0 e^{-\frac{R t}{L}} - e^{-\frac{R t}{L}} \left(\frac{I_g R \text{heaviside}(t)}{2 (R - L a)} - \frac{I_g R e^{\frac{R t}{L}} e^{-a t} \text{heaviside}(t)}{2 (R - L a)} \right) \right\}$$

$iL(t) := \text{Simplify}(\text{op}(\text{odziv}))$

$$I_0 e^{-\frac{R t}{L}} - \frac{I_g R e^{-\frac{R t}{L}} \text{heaviside}(t)}{2} - \frac{I_g R e^{-a t} \text{heaviside}(t)}{2}$$

$$R - L a$$


$\text{zamena} := \{R=1000, L=1e-3, a=100, I_g=10, I_0=-10\}$

$\{I_0 = -10, I_g = 10, R = 1000, a = 100, L = 0.001\}$


$\text{uL_zam}(t) := \text{Simplify}(iL(t) \mid \text{zamena})$

$$5.00050005 e^{-100.0 t} \text{heaviside}(t) - 10 e^{-1000000.0 t} - 5.00050005 e^{-1000000.0 t} \text{heaviside}(t)$$

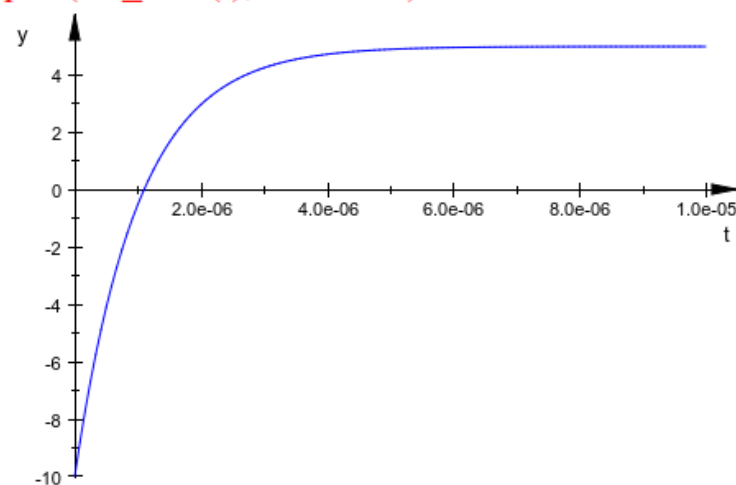
$\text{plot}(\text{uL_zam}(t), t=0..1e-5)$



plot(uL_zam(t), t=0..1e-5)

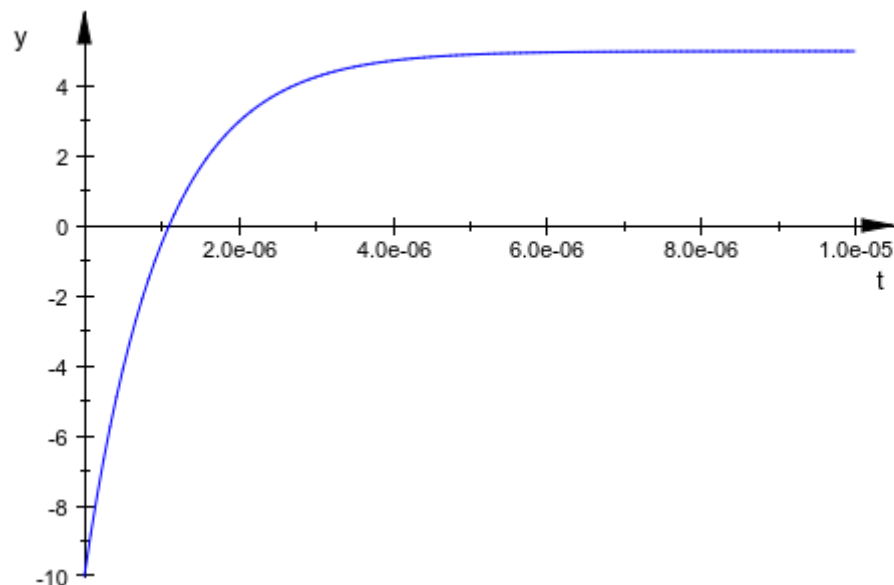

plot(uL_zam(t), t=0..0.1)

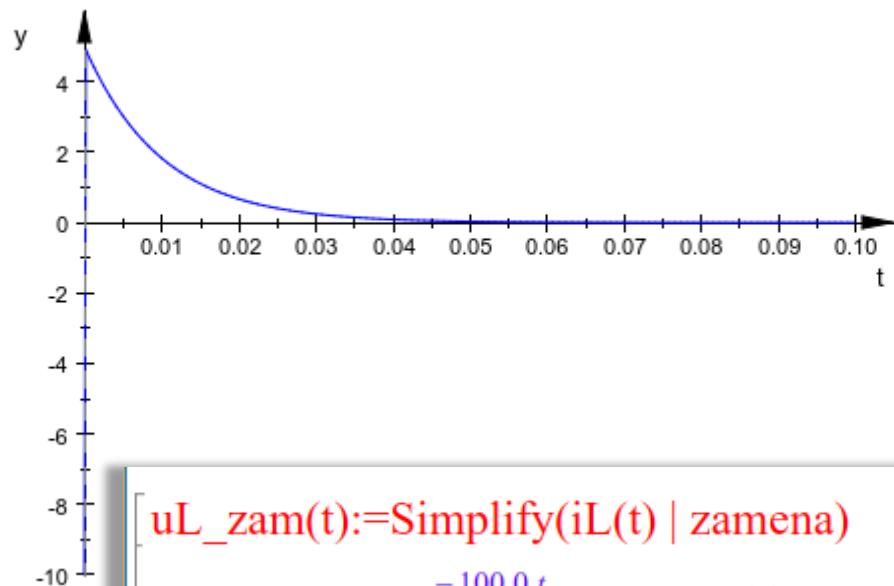

uL_zam(t):=Simplify(iL(t) | zamena)

$$5.00050005 e^{-100.0 t} \text{heaviside}(t) - 10 e^{-1000000.0 t} - 5.00050005 e^{-1000000.0 t} \text{heaviside}(t)$$

$t_0 = 0$

$$i_g = I_g e^{-at} \mathcal{H}(t)$$

$R_1 = R_2 = R$

$R_3 = 2R$

