
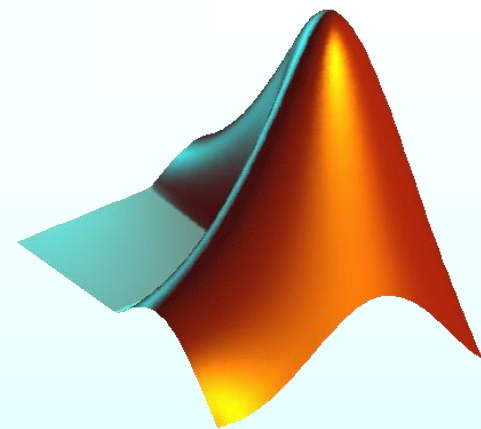


Практикум из рачунарске анализе кола

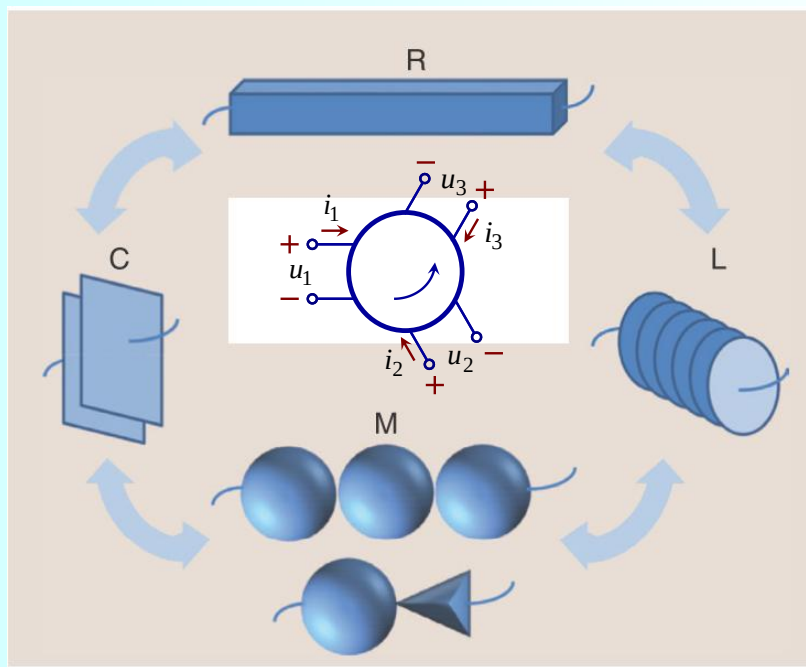


Милка Потребих



Прекидач, диода, трансформатор...

Модел прекидача (нелинеарни елемент)

MATLAB: Simscape
SimPowerSystems

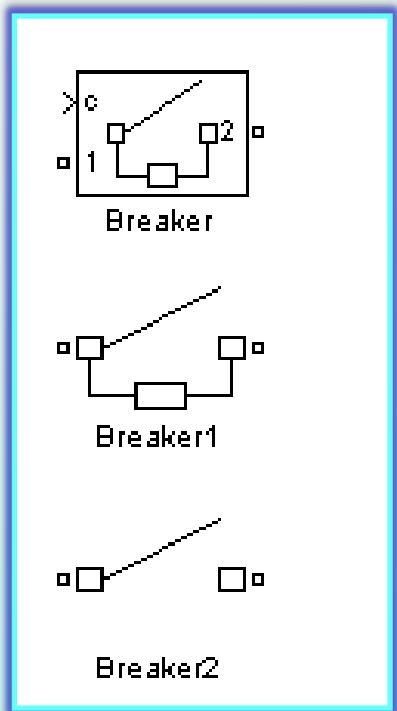

Block Parameters: Breaker

Breaker (mask) (link)

Implements a circuit breaker with internal resistance R_{on} . R_{on} is required by the model and cannot be set to zero.

When the external control mode is selected, a Simulink logical signal is used to control the breaker operation. When the signal becomes greater than zero the breaker closes instantaneously. When it becomes zero, the breaker opens at the next current zero-crossing.

Parameters

Breaker resistance R_{on} (Ohm):
0.01

Initial state (0 for 'open' , 1 for 'closed'):
0

Snubber resistance R_s (Ohms):
1e6

Snubber capacitance C_s (F):
inf

Switching times (s):
[1/60 5/60]


☐ External control of switching times

Measurements None

OK Cancel Help Apply

A series R_s - C_s snubber circuit is included in the model. It can be connected to the circuit breaker. If the Breaker block happens to be in series with an inductive circuit, an open circuit or a current source, you must use a snubber.

Пример ел. кола са прекидачем

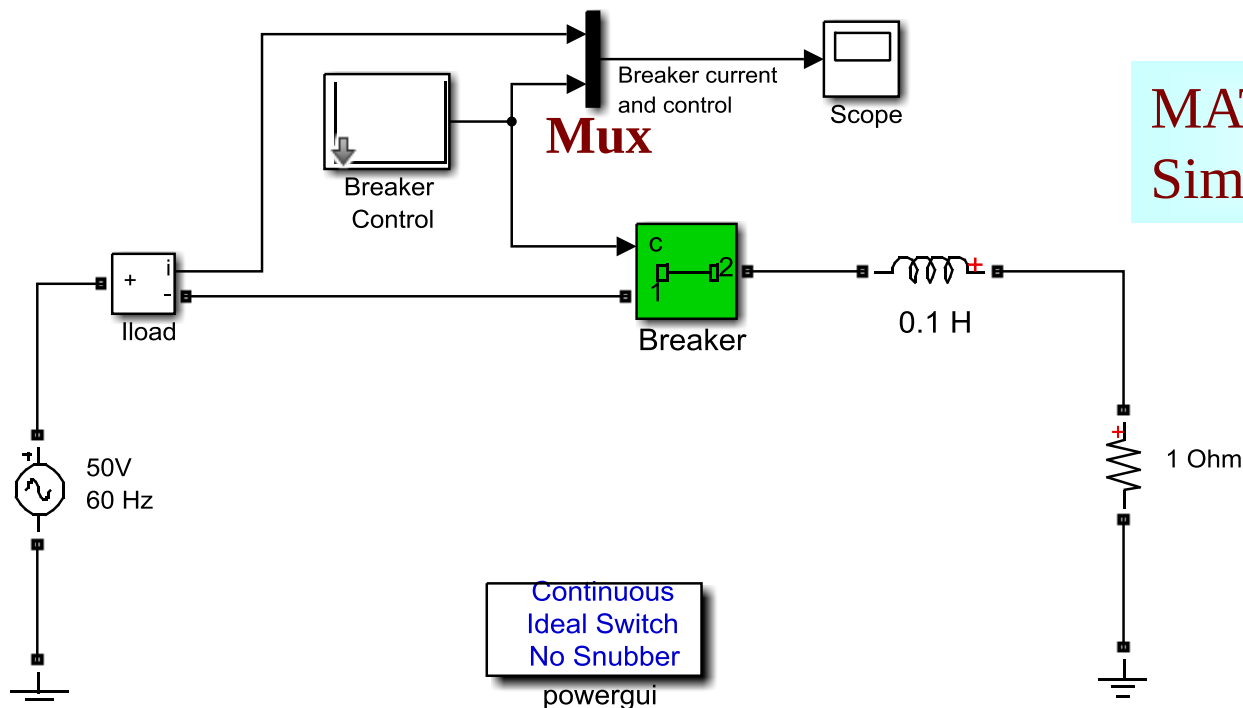

MATLAB: Simscape
SimPowerSystems


ode23tb
ode15s

This example illustrates use of the " Ideal Switching device " solution method for a circuit breaker without snubber and connected in series with an inductive load.

Zoom on breaker current and note the "exact" zero current when the breaker opens.





This solution technique introduced in R2008b is available with continuous time solvers. To enable this option, check the "Enable use of ideal switching devices" checkbox in the powergui block.

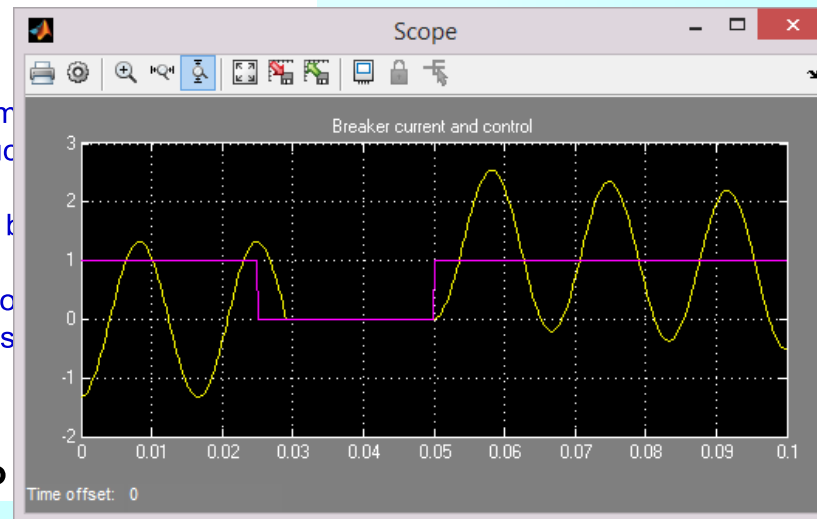Switching an Inductive Circuit Using a Breaker With no




Мултиплексер/демултиплексер

Mux

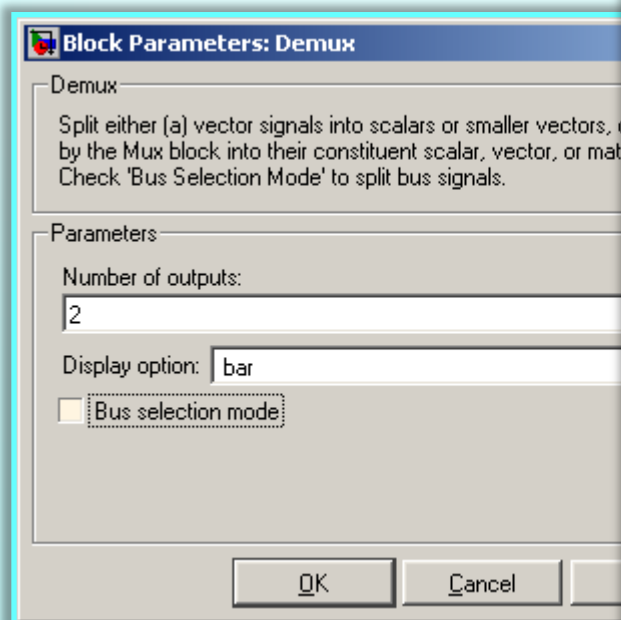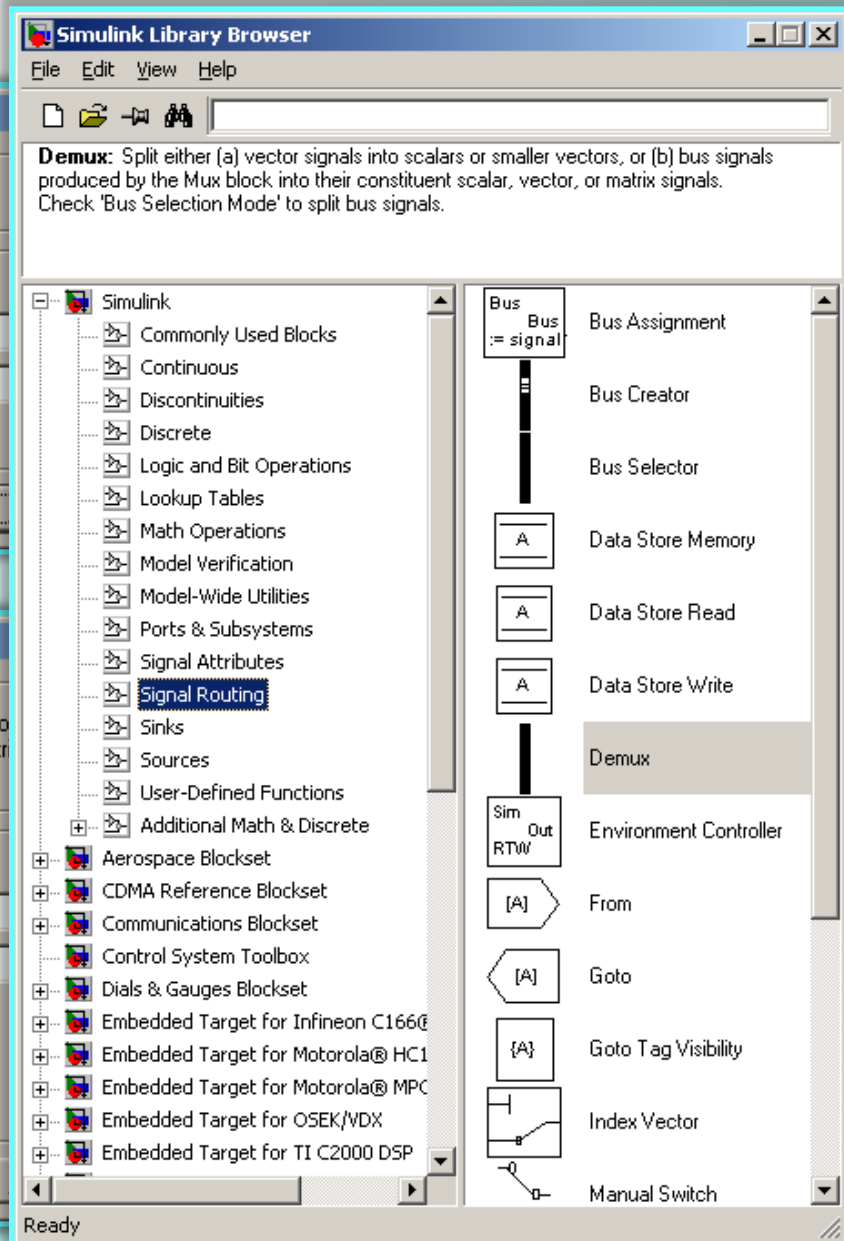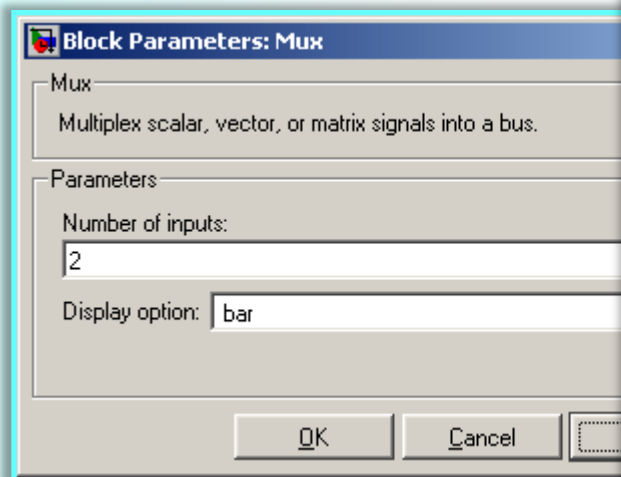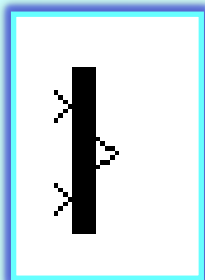

Demux

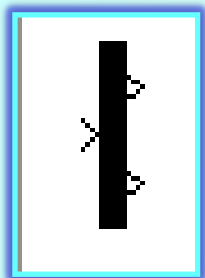

Block Parameters: Breaker

Breaker (mask) (link)

Implements a circuit breaker with internal resistance Ron. Ron is required by the model and cannot be set to zero.

When the external control mode is selected, a Simulink logical signal is used to control the breaker operation. When the signal becomes greater than zero the breaker closes instantaneously. When it becomes zero, the breaker opens at the next current zero-crossing.

Parameters

Breaker resistance Ron (Ohm):

Initial state (0 for 'open' , 1 for 'closed'):

Snubber resistance Rs (Ohms):

Snubber capacitance Cs (F):

☒ External control of switching times


Measurements

OK

Cancel

Help

Apply

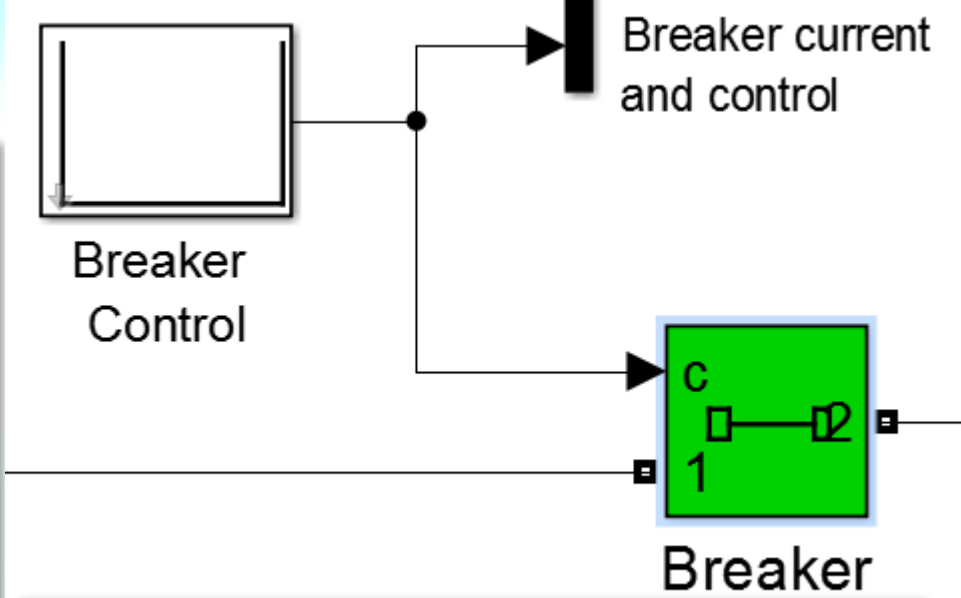

Source Block Parameters: Breaker Control

Stair Generator (mask) (link)

Generate a signal changing at specified times. Output is kept at 0 until the first specified transition time.

Parameters

Time (s):

Amplitude:

Sample time:




OK

Cancel

Help

Apply

Модел диоде (нелинеарни елемент)

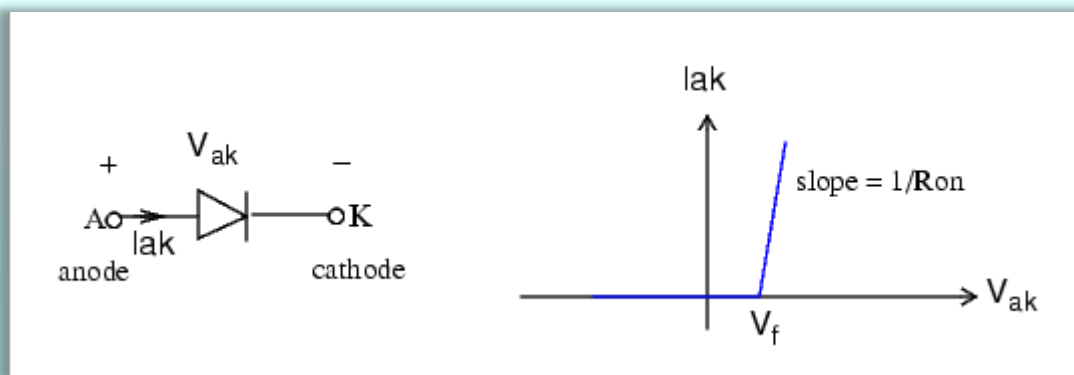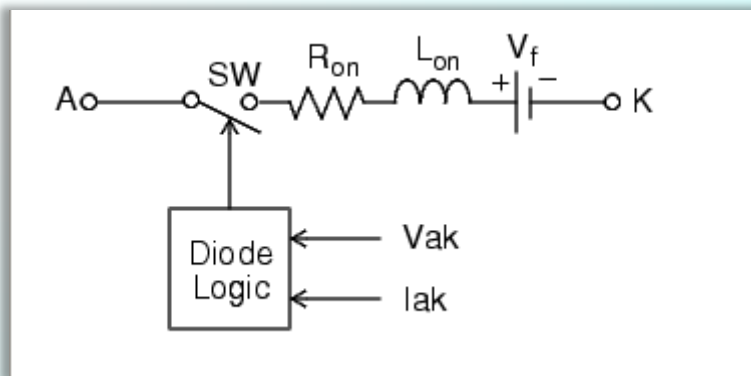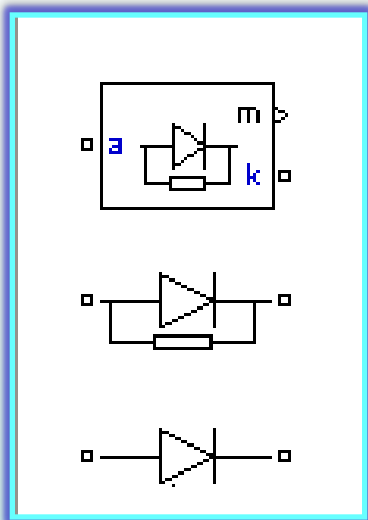

MATLAB: Simscape
SimPowerSystems

Block Parameters: Diode

Diode (mask) (link)

Implements a diode in parallel with a series RC snubber circuit. In on-state the Diode model has an internal resistance (R_{on}) and inductance (L_{on}). For most applications the internal inductance should be set to zero. The Diode impedance is infinite in off-state mode.

Parameters

Resistance R_{on} (Ohms) :
0.001

Inductance L_{on} (H) :
0

Forward voltage V_f (V) :
0.8

Initial current I_c (A) :
0


Snubber resistance R_s (Ohms) :
500

Snubber capacitance C_s (F) :
250e-9

☒ Show measurement port


OK Cancel Help Apply

Пример ел. кола са диодом

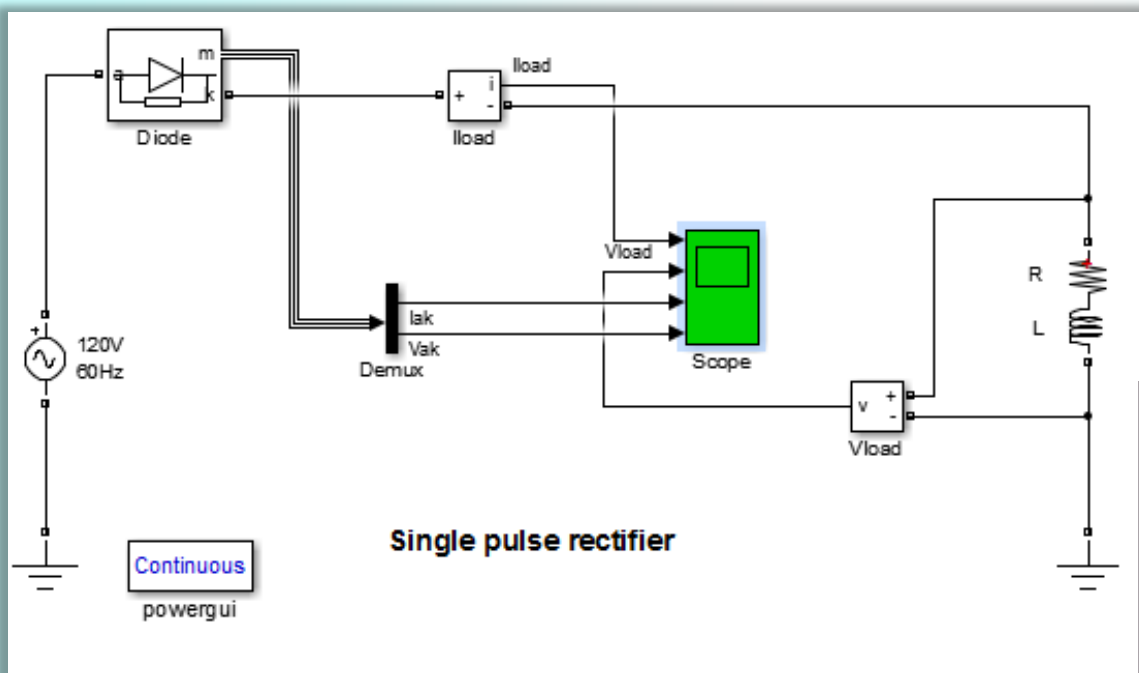

MATLAB: Simscape
SimPowerSystems

ode23tb
ode15s

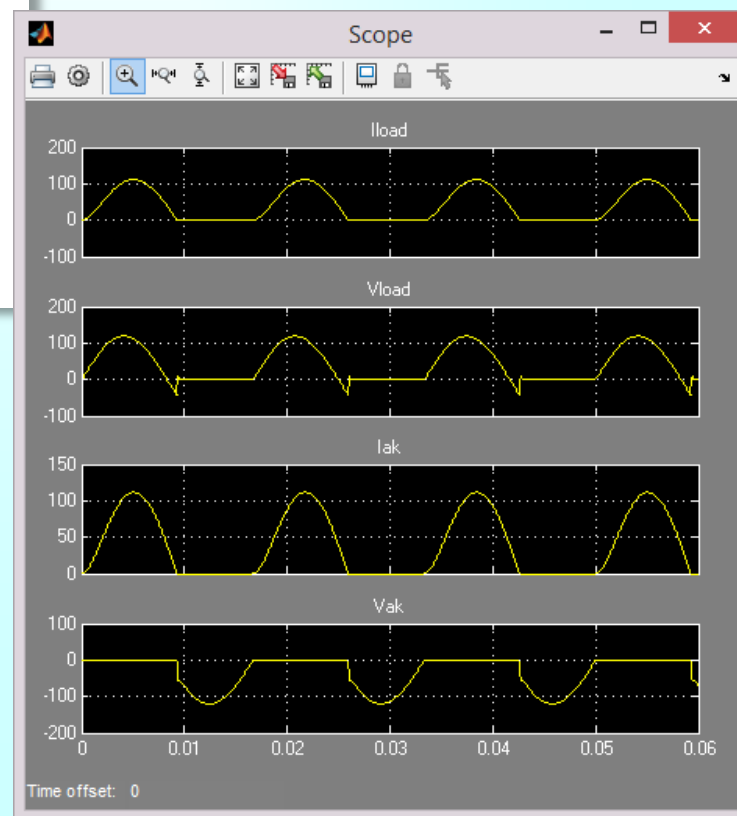



Block Parameters: Diode



Diode (mask) (link)

Implements a diode in parallel with a series RC snubber circuit. In on-state the Diode model has an internal resistance (R_{on}) and inductance (L_{on}). For most applications the internal inductance should be set to zero. The Diode impedance is infinite in off-state mode.

Parameters

Resistance R_{on} (Ohms) :

Inductance L_{on} (H) :

Forward voltage V_f (V) :

Initial current I_c (A) :

Snubber resistance R_s (Ohms) :

Snubber capacitance C_s (F) :

☒ Show measurement port

OK

Cancel

Help

Apply



Block Parameters: R L



Series RLC Branch (mask) (link)

Implements a series branch of RLC elements. Use the 'Branch type' parameter to add or remove elements from the branch.

Parameters

Branch type: RL

Resistance (Ohms):

Inductance (H):

☐ Set the initial inductor current

Measurements None

OK



Cancel

Help

Apply

Линеарни индуктивни трансформатор

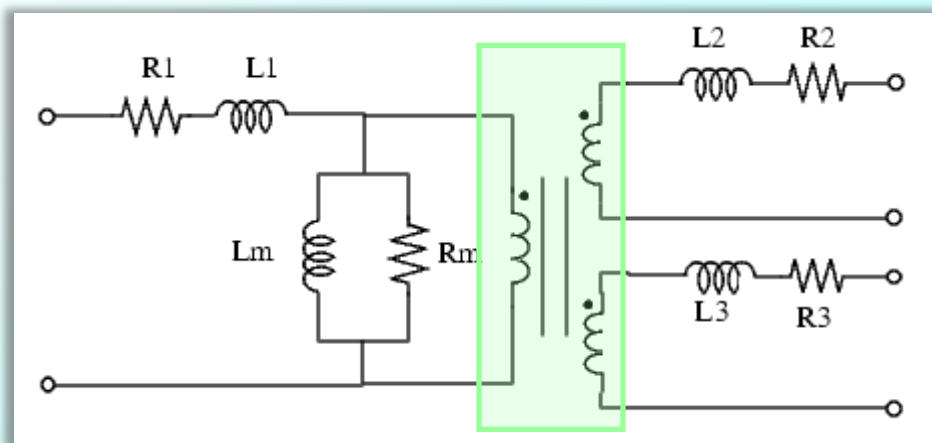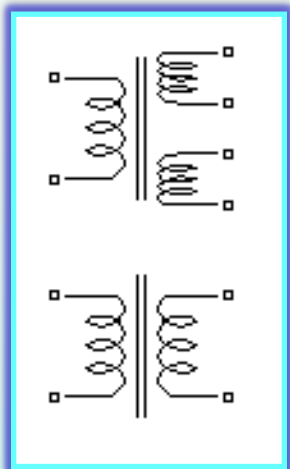- Модел ЛИТ за Енергетику са нормализованим вредностима



Идеални трансформатор

MATLAB: Simscape
SimPowerSystems




$$R_{base} = \frac{(V_n)^2}{P_n}$$
$$L_{base} = \frac{R_{base}}{2\pi f_n}$$

$$R(\text{p.u.}) = \frac{R(\Omega)}{R_{base}}$$
$$L(\text{p.u.}) = \frac{L(H)}{L_{base}}$$

Modeling an Ideal Transformer

To implement an ideal transformer model, set the winding resistances and inductances to 0, and the magnetization resistance and inductance (R_m L_m) to ∞ .

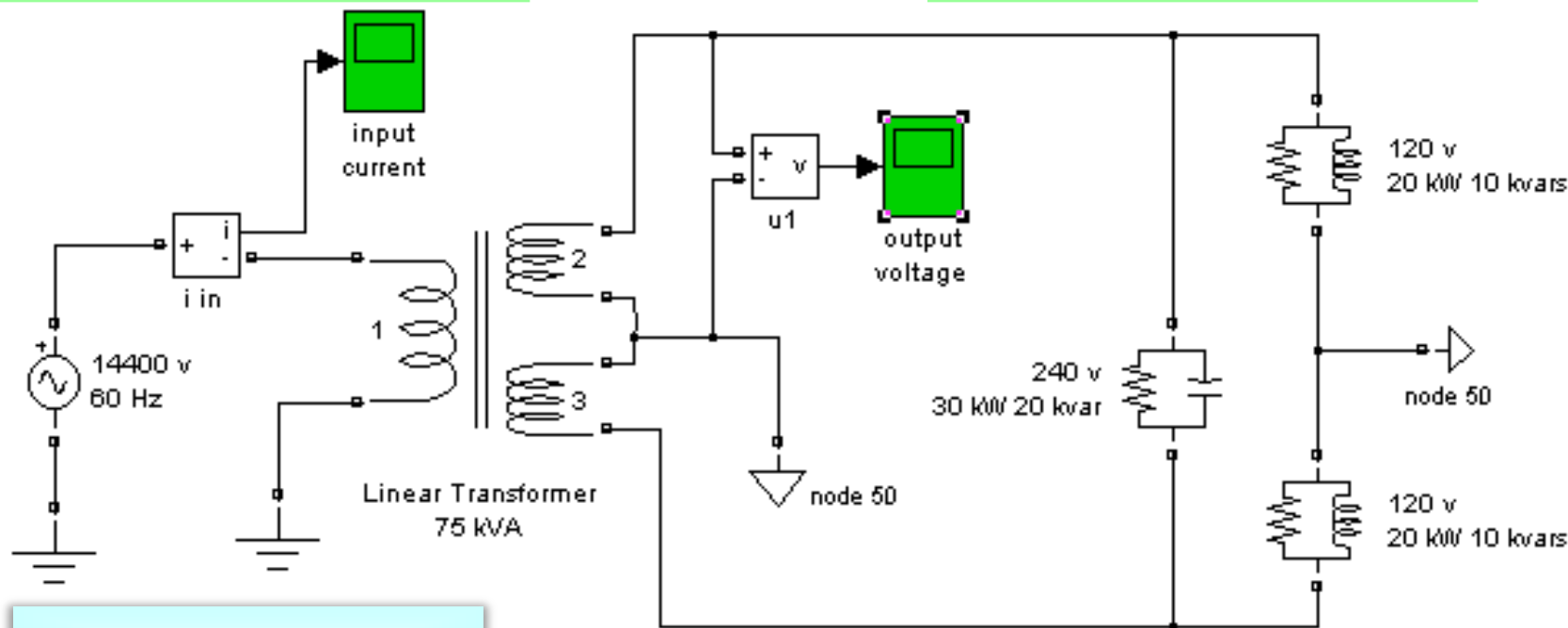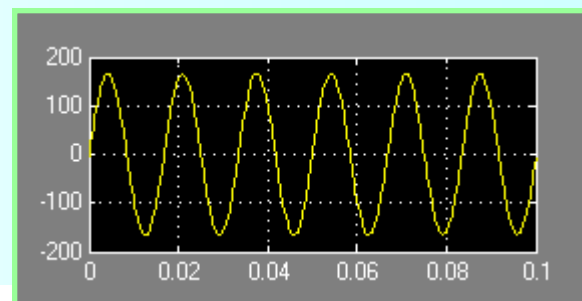
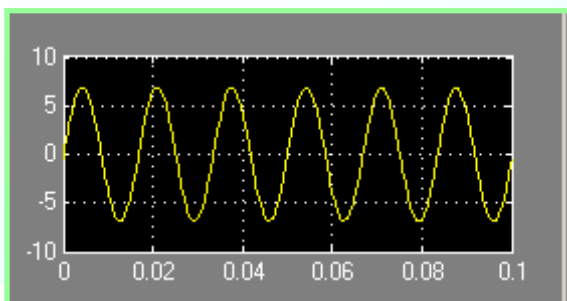
Пример ел. кола са линеарним индуктивним трансформатором



**MATLAB: Simscape
SimPowerSystems**


Mutual Inductance

- Основни модел ЛИТ за Енергетику

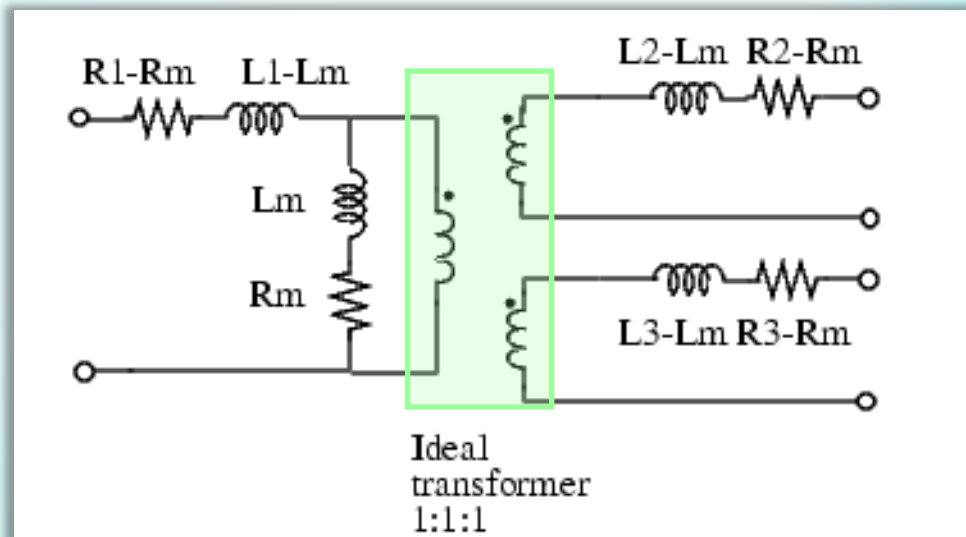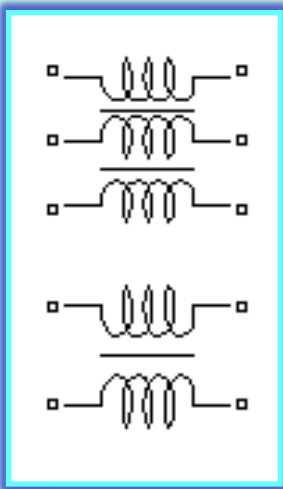

$$R_1, R_2, R_3 \neq R_m$$


$$L_1, L_2, L_3 \neq L_m$$

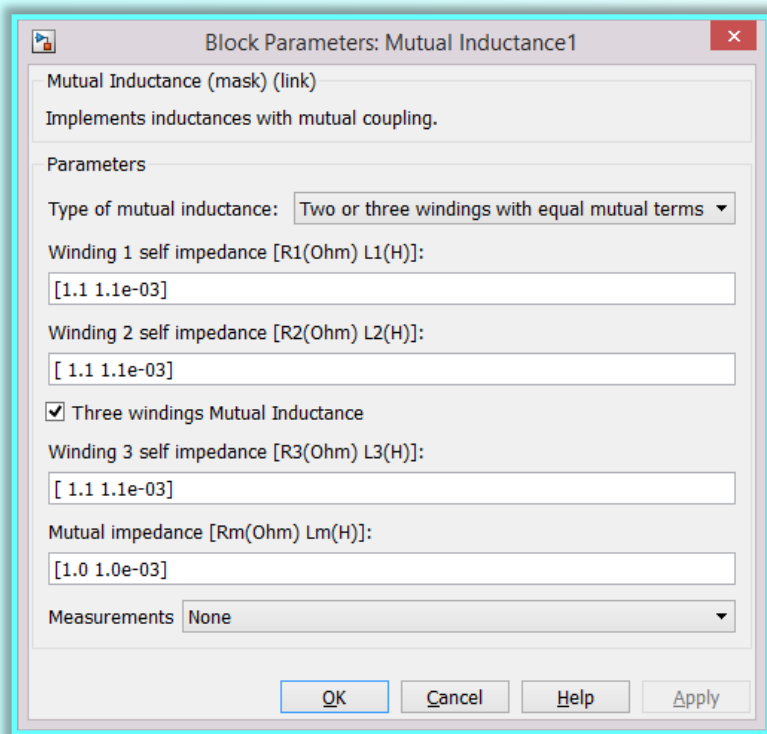


MATLAB: Simscape
SimPowerSystems

Пример ел. кола са моделом ЛИТ

Mutual Inductance

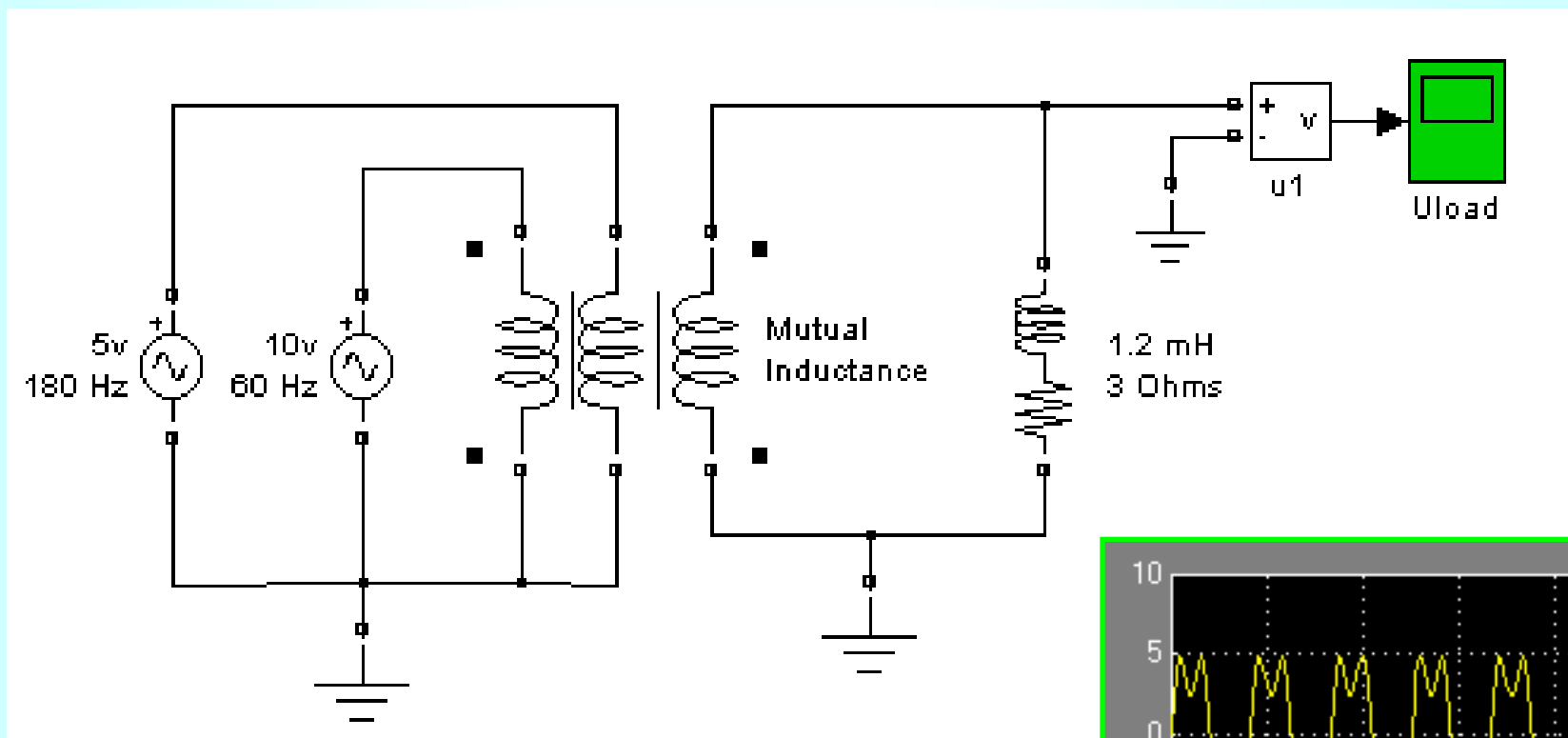


MATLAB: Simscape
SimPowerSystems

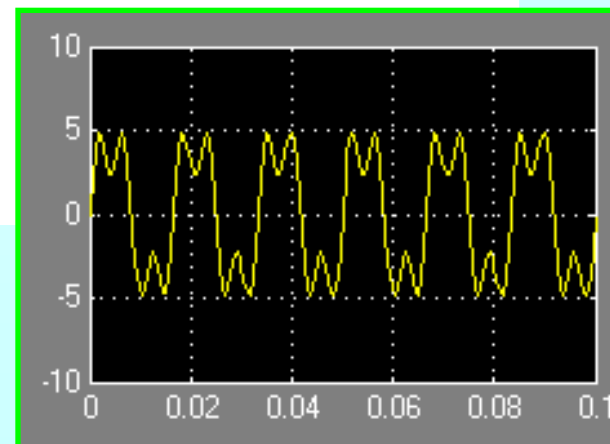

Mutual Inductance

- Основни модел ЛИТ без губитака

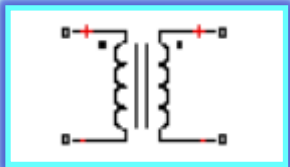

$$V_1 = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$
$$V_2 = L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt}$$
$$M = k\sqrt{L_1 \cdot L_2}$$

V1	Voltage across winding 1
V2	Voltage across winding 2
I1	Current flowing into the + terminal of winding 1
I2	Current flowing into the + terminal of winding 2
L1, L2	Winding self-inductances
M	Mutual inductance
k	Coefficient of coupling, 0 < k < 1
t	Time

Block Parameters: Mutual Inductor

Mutual Inductor

Models a mutual inductor. If winding 1 has voltage V1 across it and current I1 flowing into its + terminal, and winding 2 has voltage V2 across it and current I2 flowing into its + terminal, then

$$V_1 = L_1 \cdot dI_1/dt + M \cdot dI_2/dt$$
$$V_2 = L_2 \cdot dI_2/dt + M \cdot dI_1/dt$$

where parameters L1 and L2 are the winding self-inductances, and M is the mutual inductance. M is defined in terms of the Coefficient of coupling k by $M = k \cdot \sqrt{L_1 \cdot L_2}$. Hence k should be greater than zero and less than one.

The parameters Winding 1 initial current and Winding 2 initial current set the initial current through windings 1 and 2. Note that this value is not used if the solver configuration is set to Start simulation from steady state.

[View source for Mutual Inductor](#)

Parameters

Inductance L1: 1 mH

Inductance L2: 1 mH


Coefficient of coupling: 0.9999

Winding 1 initial current: 0 A

Winding 2 initial current: 0 A

OK Cancel Help Apply

MATLAB: Simscape
Foundation Library

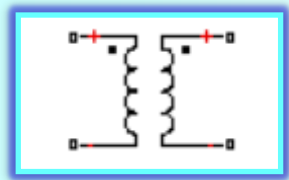

Ideal Transformer

- Модел идеалног трансформатора

$$V_1 = N \cdot V_2$$
$$I_2 = N \cdot I_1$$

Block Parameters: Ideal Transformer

Ideal Transformer

Models an ideal power-conserving transformer satisfying $V_1 = N \cdot V_2$ and $I_2 = N \cdot I_1$ where N is the Winding ratio, V_1 and V_2 are the primary and secondary voltages, I_1 is the current flowing into the primary + terminal, and I_2 is the current flowing out of the secondary + terminal.

This block can be used to represent either an AC transformer or a solid-state DC to DC converter. To model a transformer with inductance and mutual inductance terms, use the Mutual Inductor block.

Note that the two electrical networks connected to the primary and secondary windings must each have their own Electrical Reference block.

[View source for Ideal Transformer](#)

Parameters

Winding ratio:

OK

Cancel


Help

Apply

V_1	Primary voltage
V_2	Secondary voltage
I_1	Current flowing into the primary + terminal
I_2	Current flowing out of the secondary + terminal
N	Winding ratio

MATLAB: Simscape
Foundation Library

Одзив на простопериодичну побуду

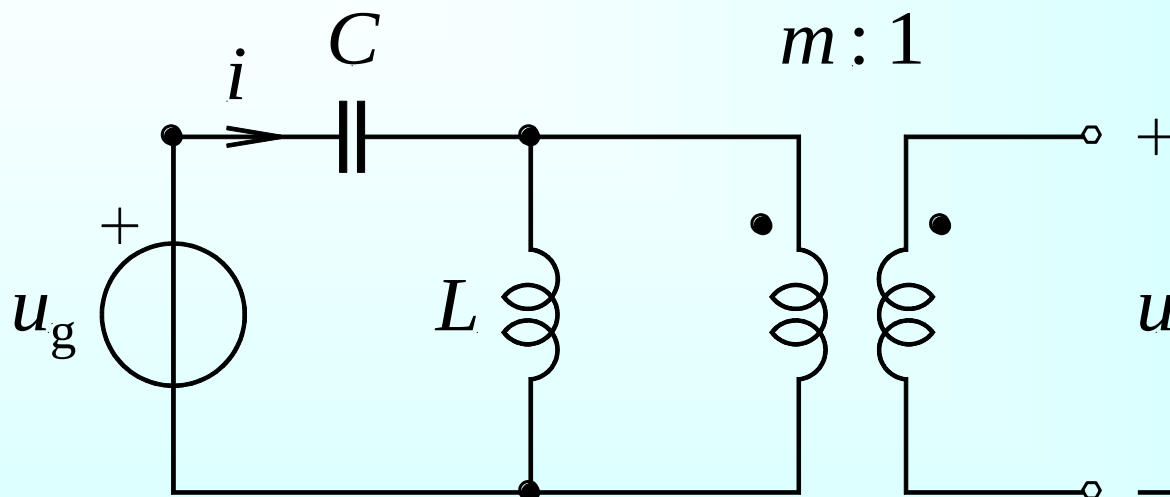

$$U_m = 1\text{ V}$$

$$\omega = 10^5 \text{ rad/s}$$

$$L = 0.1 \text{ mH}$$

$$C = 1 \mu\text{F}$$

$$m = 1$$

$$u_g(t) = U_m \sin\left(\frac{1}{\sqrt{CL}} t\right) h(t)$$

Задатак - простопериодична побуда


(5) Одредити једначину одзива за напон u електричног кола са слике. Вредности елемената и параметри побуде су познати,

$$u_g(t) = U_m \sin\left(\frac{1}{\sqrt{CL}}t\right) h(t).$$

Нема сакупљене енергије.



(5) Одредити струју извора, i , и нацртати график струје извора.




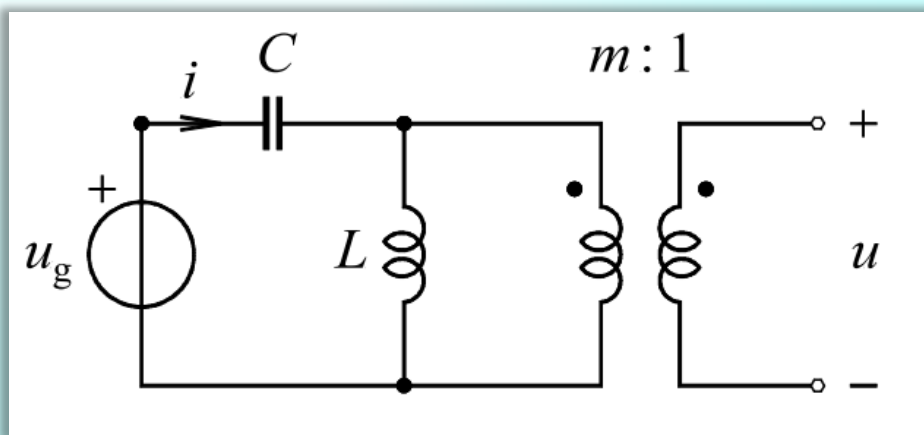
(5) Како гласе једначине стања кола? Написати их у матричном облику.




MATLAB: Simulink

Sources

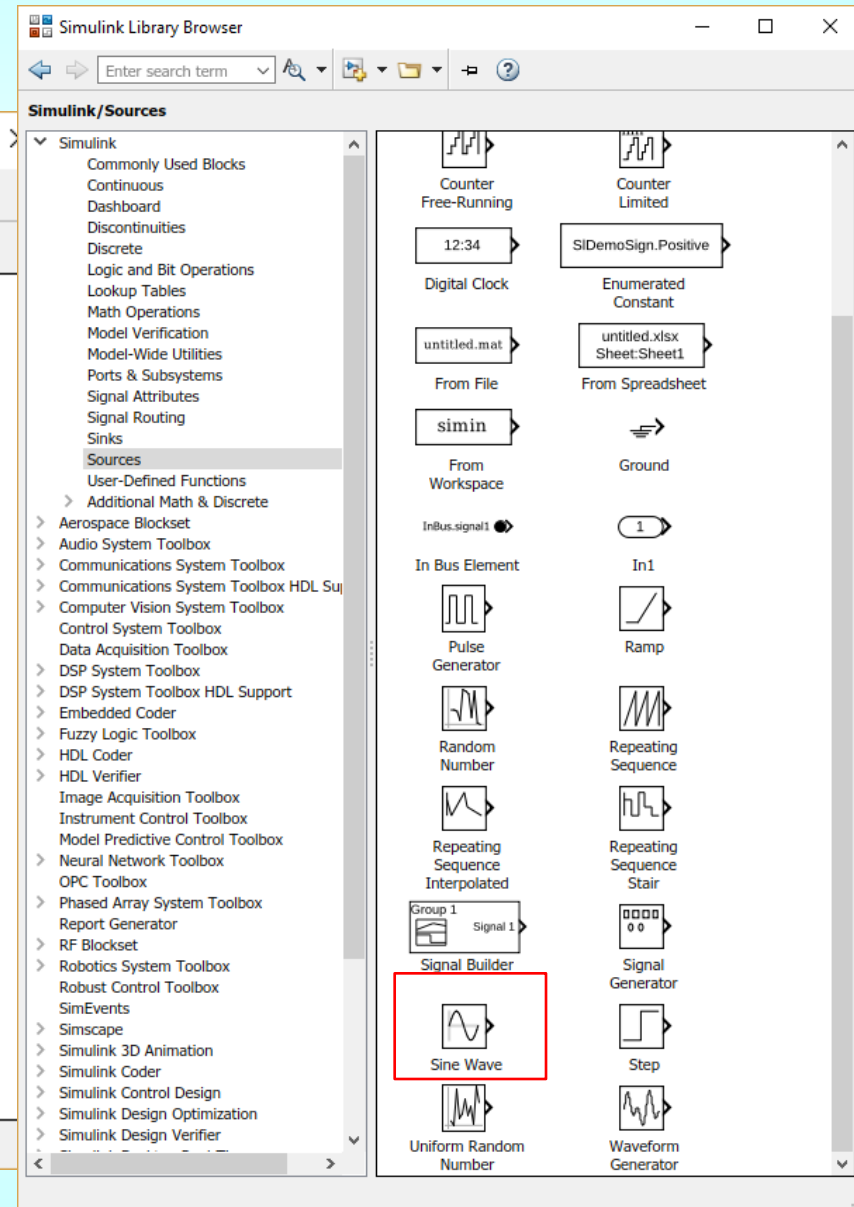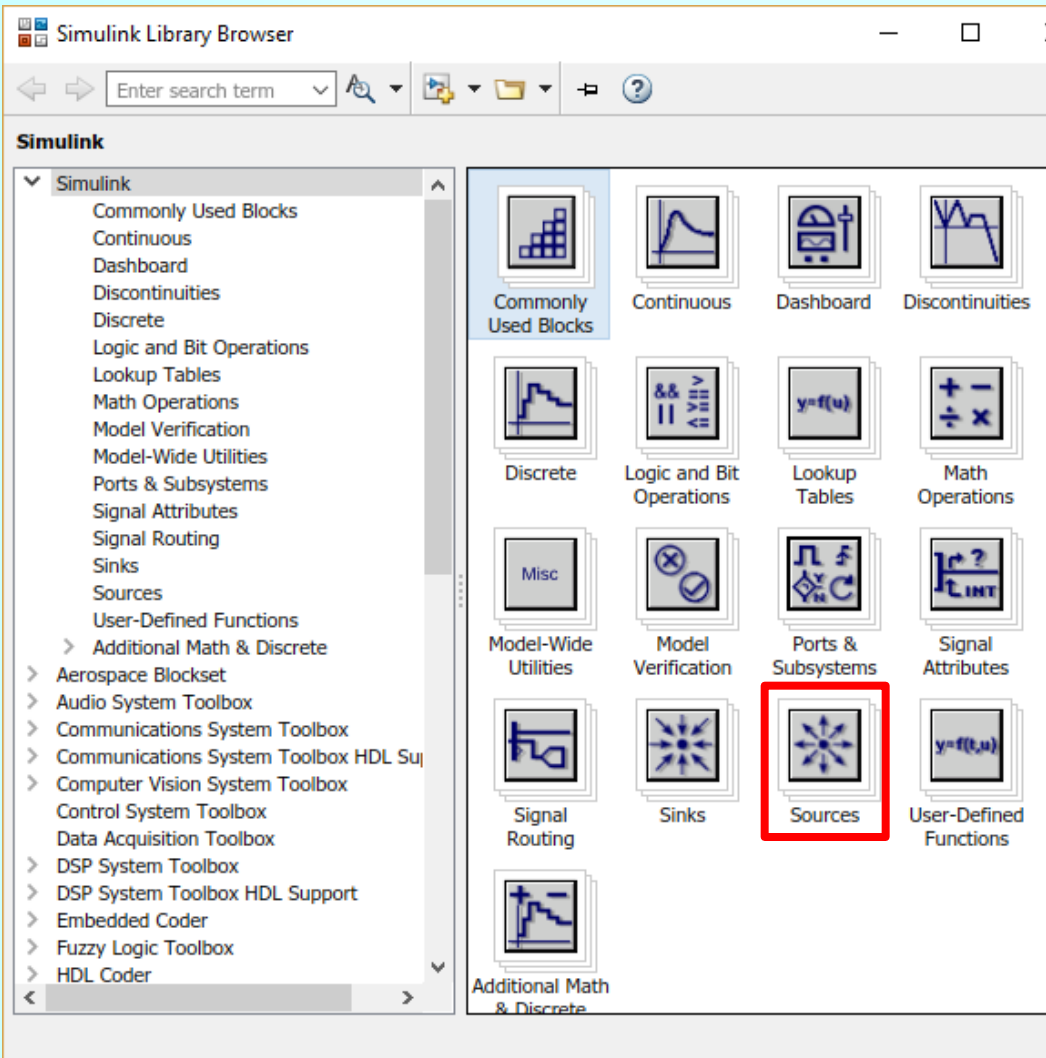

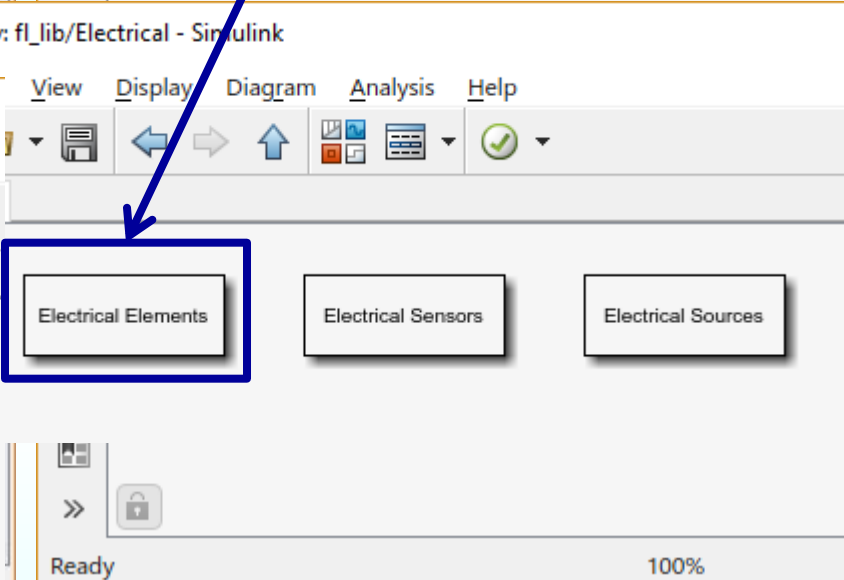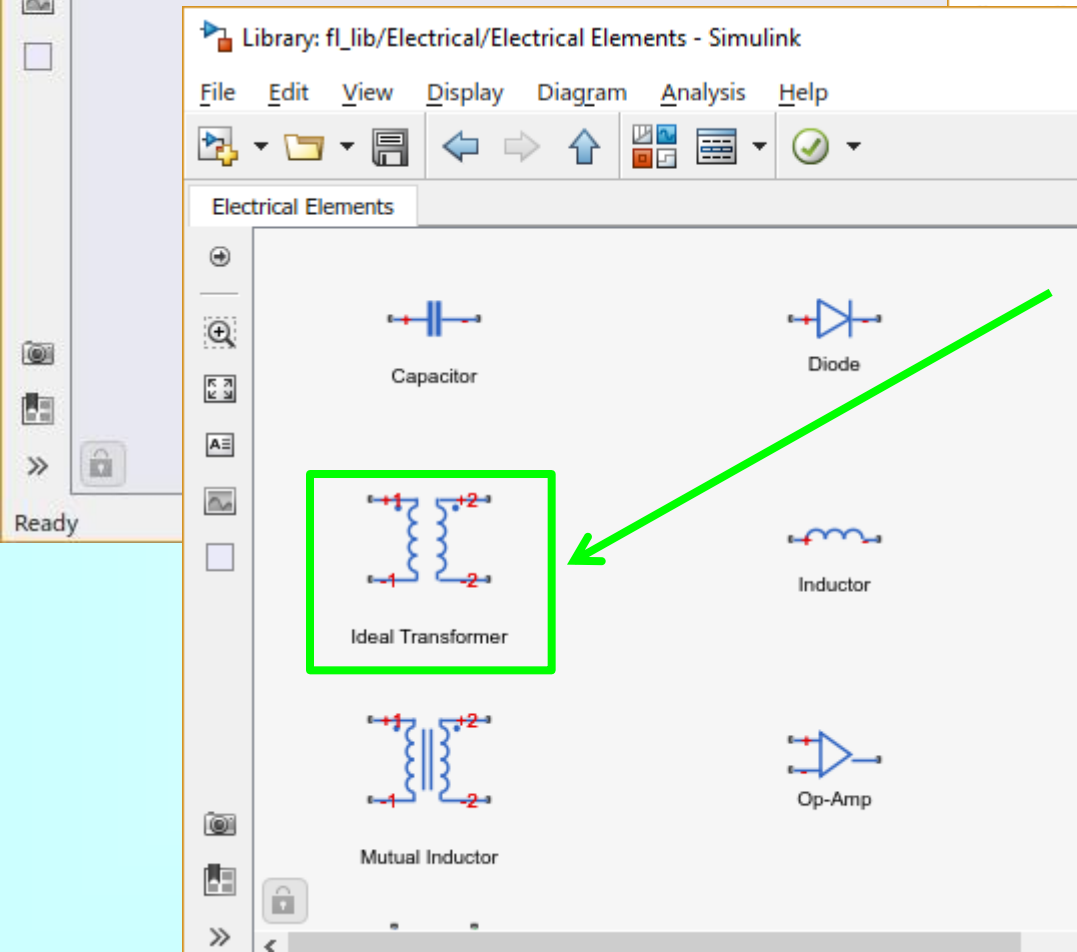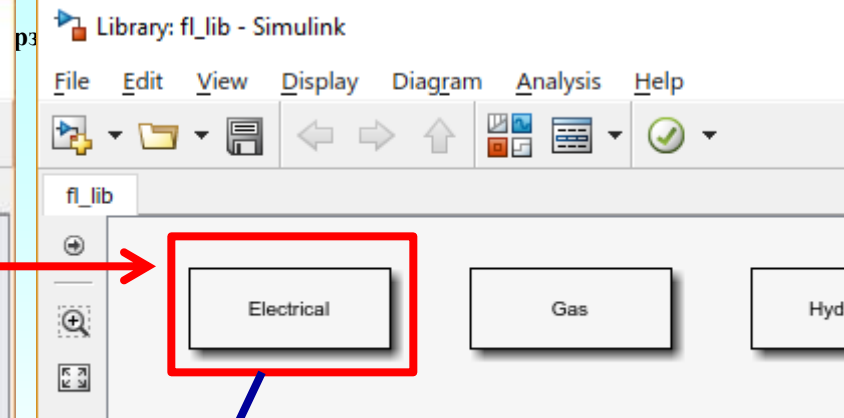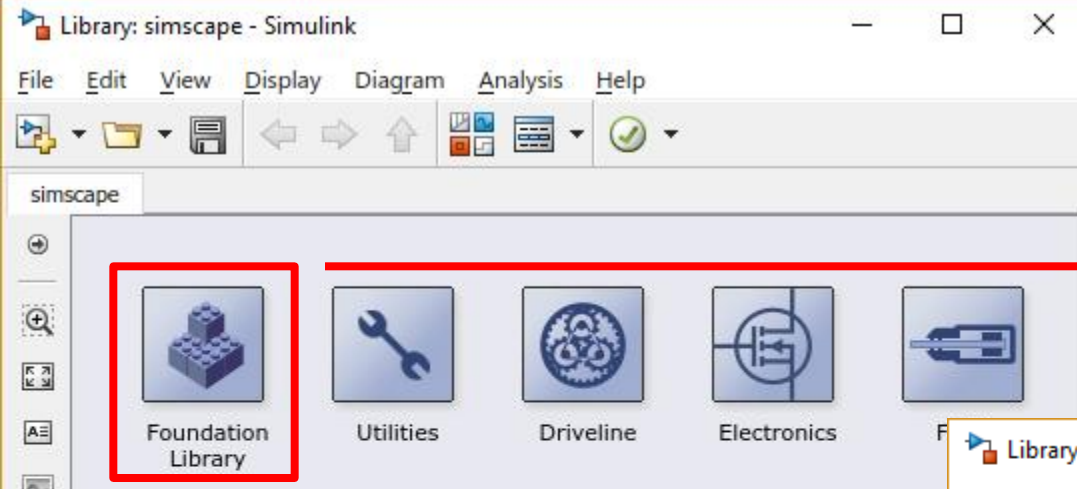

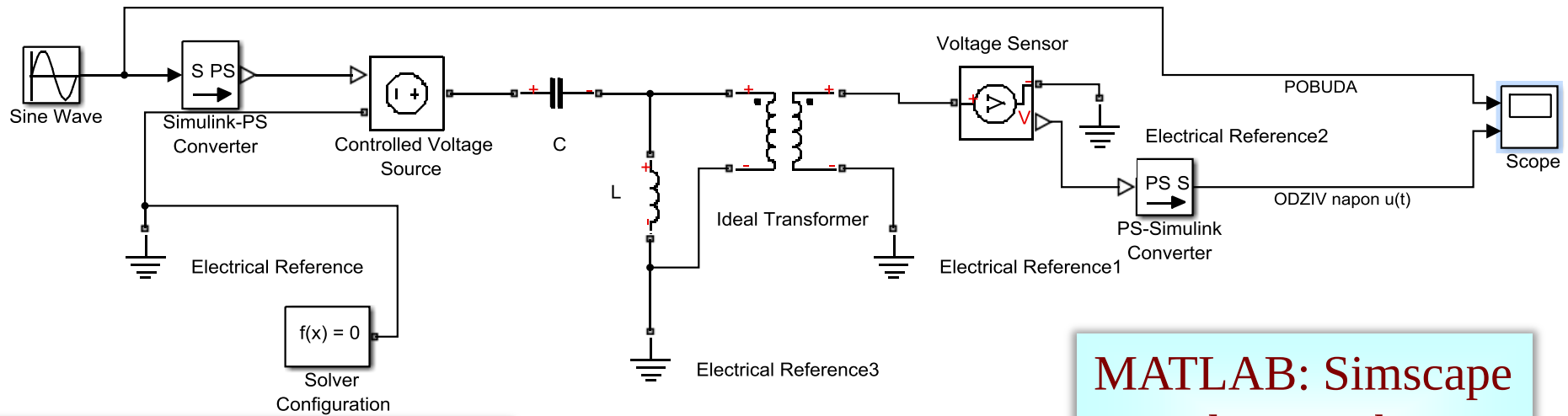

MATLAB: Simscape Foundation Library Utilities Simulink

Source Block Parameters: Sine Wave

Sine Wave

Output a sine wave:

$$O(t) = \text{Amp} \cdot \sin(\text{Freq} \cdot t + \text{Phase}) + \text{Bias}$$

Sine type determines the computational technique used. The parameters in the two types are related through:

Samples per period = $2 \cdot \pi / (\text{Frequency} \cdot \text{Sample time})$

Number of offset samples = $\text{Phase} \cdot \text{Samples per period} / (2 \cdot \pi)$

Use the sample-based sine type if numerical problems due to running for large times (e.g. overflow in absolute time) occur.

Parameters

Sine type: **Time based**

Time (t): **Use simulation time**

Amplitude:

1

Bias:

0

Frequency (rad/sec):

100000

Phase (rad):

0

Sample time:

0

☒ Interpret vector parameters as 1-D

OK Cancel Help Apply

Block Parameters: Ideal Transformer

Ideal Transformer

Models an ideal power-conserving transformer satisfying $V_1 = N \cdot V_2$ and $I_2 = N \cdot I_1$ where N is the Winding ratio, V_1 and V_2 are the primary and secondary voltages, I_1 is the current flowing into the primary + terminal, and I_2 is the current flowing out of the secondary + terminal.

This block can be used to represent either an AC transformer or a solid-state DC to DC converter. To model a transformer with inductance and mutual inductance terms, use the Mutual Inductor block.

Note that the two electrical networks connected to the primary and secondary windings must each have their own Electrical Reference block.


[View source for Ideal Transformer](#)

Parameters

Winding ratio:

1

OK Cancel Help Apply

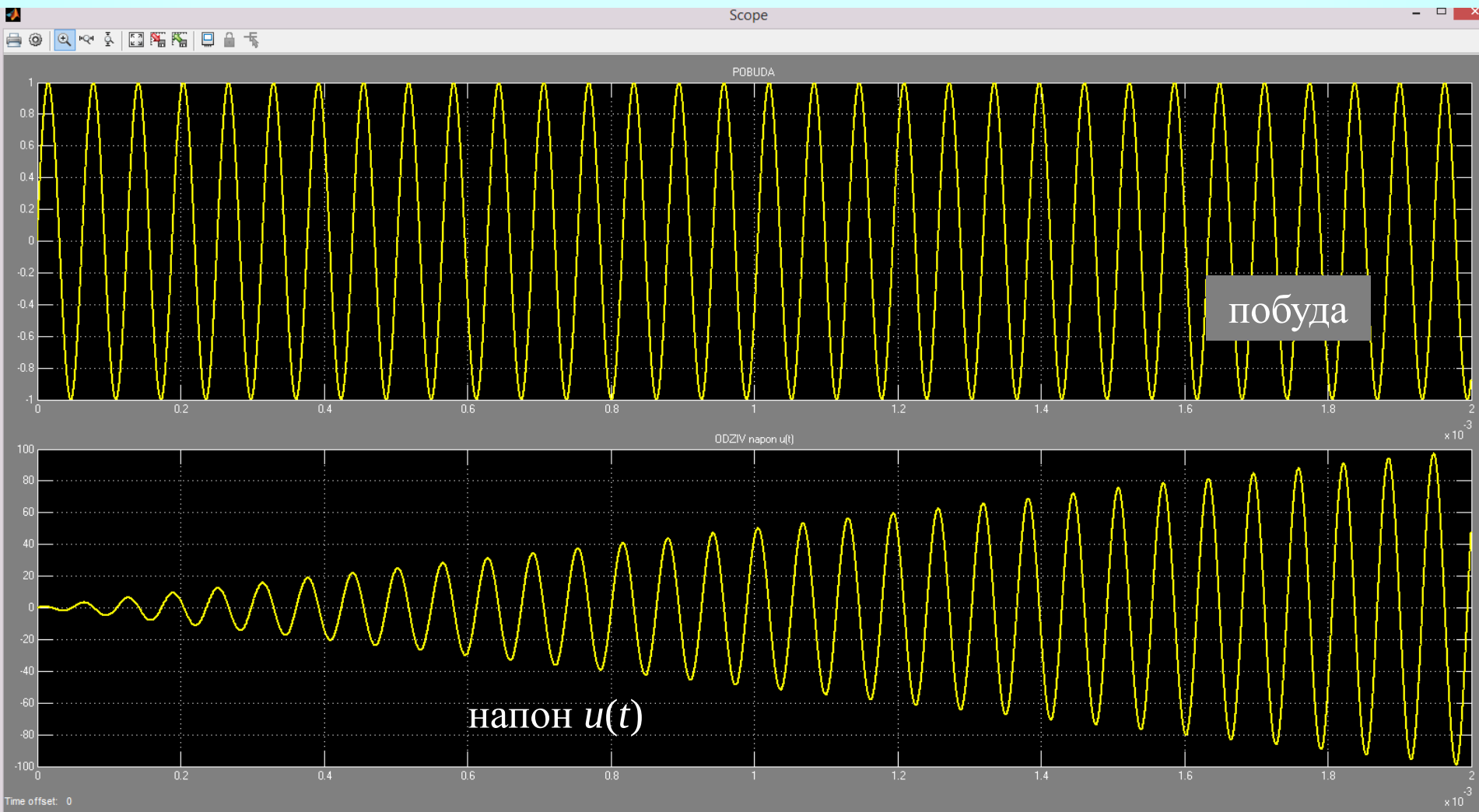

MATLAB: MuPAD

```
jednacine:={ug = uC + uL,  
uL = L * Di,  
i = C*DuC,  
uL=m*u}
```

```
{uL = m u, ug = uC + uL, i = C DuC, uL = Di L}
```

```
jednacineIzvoda:=groebner::eliminate(jednacine,{uL, u})  
[uC - ug + Di L, i - C DuC]
```

```
assume(C>0 and L>0 and m>0 and Um>0 and t>=0)
```

```
jednacineStanja := solve(jednacineIzvoda, {Di, DuC})
```

```
{ [Di = - (uC - ug) / L, DuC = i / C] }
```

```
PromenljiveStanjaIzvodi:={uC=uC(t), i=i(t), Di=D(i)(t), DuC=D(uC)(t)}
```

```
{i = i(t), uC = uC(t), Di = i'(t), DuC = uC'(t)}
```

```
pobuda := {ug=Um*sin(t/sqrt(L*C))*heaviside(t)}
```

```
{ug = Um sin( (t / (sqrt(C) * sqrt(L))) ) heaviside(t) }
```

JS:=jednacineStanja | PromenljiveStanjaIzvodi | pobuda

$$\left\{ \left[i'(t) = - \frac{uC(t) - Um \sin\left(\frac{t}{\sqrt{C}\sqrt{L}}\right) \text{heaviside}(t)}{L}, uC'(t) = \frac{i(t)}{C} \right] \right\}$$

op(op(JS))

$$i'(t) = - \frac{uC(t) - Um \sin\left(\frac{t}{\sqrt{C}\sqrt{L}}\right) \text{heaviside}(t)}{L}, uC'(t) = \frac{i(t)}{C}$$

JSpocetveVrednosti:={op(op(JS)), uC(0)=0, i(0)=0}

$$\left\{ uC'(t) = \frac{i(t)}{C}, i(0) = 0, uC(0) = 0, i'(t) = - \frac{uC(t) - Um \sin\left(\frac{t}{\sqrt{C}\sqrt{L}}\right) \text{heaviside}(t)}{L} \right\}$$

odziv := ode::solve(JSpocetveVrednosti, {uC(t), i(t)})

$$\left\{ \left[uC(t) = \frac{Um \sigma_1}{4} + \frac{Um \sigma_1 \text{sign}(t)}{4} - \frac{Um t \sigma_2}{4 \sqrt{C} \sqrt{L}} - \frac{Um t \sigma_2 \text{sign}(t)}{4 \sqrt{C} \sqrt{L}}, i(t) = \frac{Um t \sigma_1}{4 L} + \frac{Um t \sigma_1 \text{sign}(t)}{4 L} \right] \right\}$$

where

$$\sigma_1 = \sin\left(\frac{t}{\sqrt{C}\sqrt{L}}\right)$$

$$\sigma_2 = \cos\left(\frac{t}{\sqrt{C}\sqrt{L}}\right)$$

MATLAB: MuPAD

MATLAB: MuPAD

assume(t>0):(uC(t) | odziv)

$$\frac{U_m \sin\left(\frac{t}{\sqrt{C} \sqrt{L}}\right)}{2} - \frac{U_m t \cos\left(\frac{t}{\sqrt{C} \sqrt{L}}\right)}{2 \sqrt{C} \sqrt{L}}$$

assume(t>0):(i(t) | odziv)

$$\frac{U_m t \sin\left(\frac{t}{\sqrt{C} \sqrt{L}}\right)}{2 L}$$

iL(t):=i(t) | odziv

$$\frac{U_m t \sin\left(\frac{t}{\sqrt{C} \sqrt{L}}\right)}{2 L}$$

uL(t):=Simplify(L*(diff(iL(t),t)))

$$\frac{U_m \sin\left(\frac{t}{\sqrt{C} \sqrt{L}}\right)}{2} + \frac{U_m t \cos\left(\frac{t}{\sqrt{C} \sqrt{L}}\right)}{2 \sqrt{C} \sqrt{L}}$$


u(t):=m*uL(t)

$$m \left(\frac{U_m \sin\left(\frac{t}{\sqrt{C} \sqrt{L}}\right)}{2} + \frac{U_m t \cos\left(\frac{t}{\sqrt{C} \sqrt{L}}\right)}{2 \sqrt{C} \sqrt{L}} \right)$$


zamena:={L=0.1e-3, C=1e-6, Um=1, m=1}

{L = 0.0001, Um = 1, m = 1, C = 0.000001}

plot(u(t)|zamena, t=0..2e-3, GridVisible = TRUE)

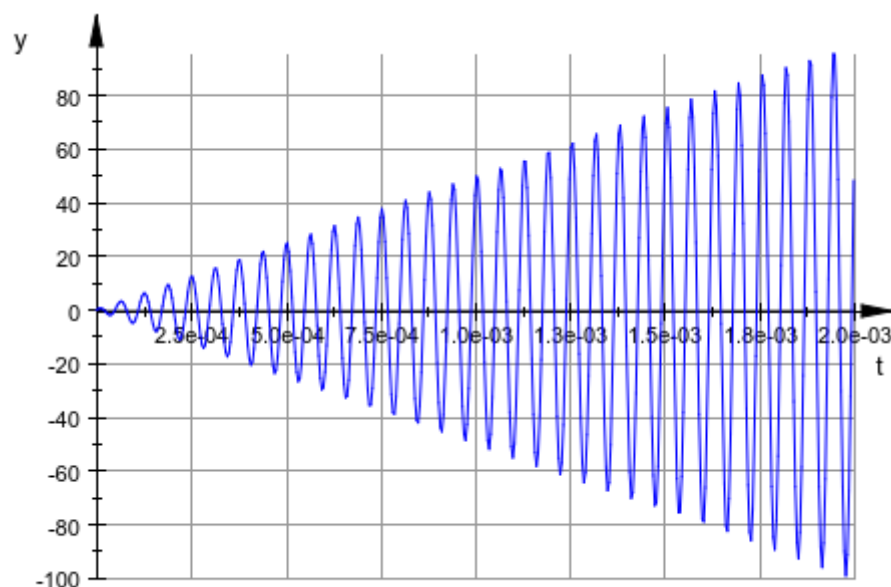


Одзив на експоненцијалну побуду

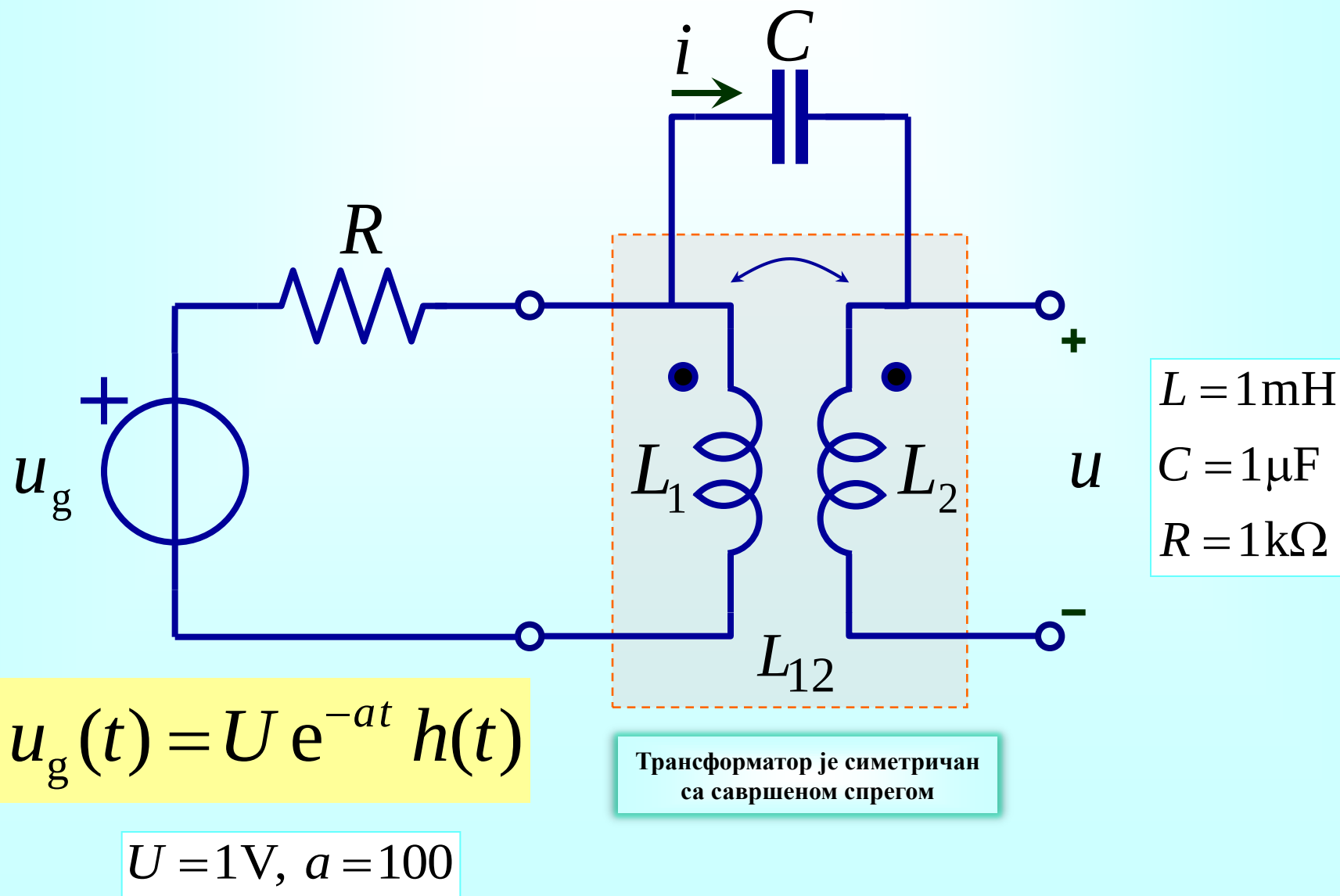

Задатак - експоненцијална побуда

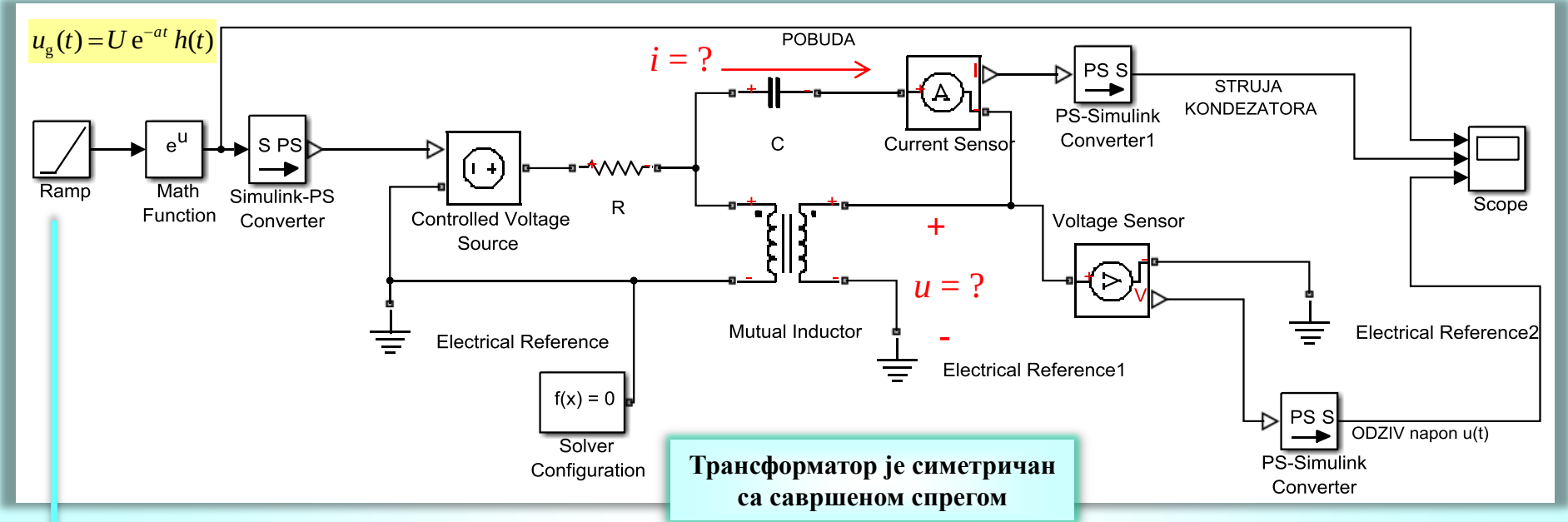- Параметри кола са слике су познати. Линеарни индуктивни трансформатор је симетричан са савршеном спрегом. Нема сакупљене енергије.
- Одредити струју кондензатора $i(t)$ и нацртати њен график.
- Одредити напон секундара $u(t)$ и нацртати његов график.



Source Block Parameters: Ramp

Ramp (mask) (link)

Output a ramp signal starting at the specified time.

Parameters

Slope:

-100

Start time:

0

Initial output:

0

☒ Interpret vector parameters as 1-D

OK Cancel Help Apply

Block Parameters: Mutual Inductor

Mutual Inductor

Models a mutual inductor. If winding 1 has voltage $V1$ across it and current $I1$ flowing into its + terminal, and winding 2 has voltage $V2$ across it and current $I2$ flowing into its + terminal, then

$V1 = L1 \cdot dI1/dt + M \cdot dI2/dt$

$V2 = L2 \cdot dI2/dt + M \cdot dI1/dt$

where parameters $L1$ and $L2$ are the winding self-inductances, and M is the mutual inductance. M is defined in terms of the Coefficient of coupling k by $M = k \cdot \sqrt{L1 \cdot L2}$. Hence k should be greater than zero and less than one.

The parameters Winding 1 initial current and Winding 2 initial current set the initial current through windings 1 and 2. Note that this value is not used if the solver configuration is set to Start simulation from steady state.

[View source for Mutual Inductor](#)

Parameters

Inductance L1: 1 mH

Inductance L2: 1 mH

Coefficient of coupling: 0.9999

Winding 1 initial current: 0 A

Winding 2 initial current: 0 A

OK Cancel Help Apply


$L = 1 \text{ mH}$

$C = 1 \mu\text{F}$

$R = 1 \text{ k}\Omega$

MATLAB: Simscape
Foundation Library
Utilities
Simulink

$U = 1 \text{ V}, a = 100$

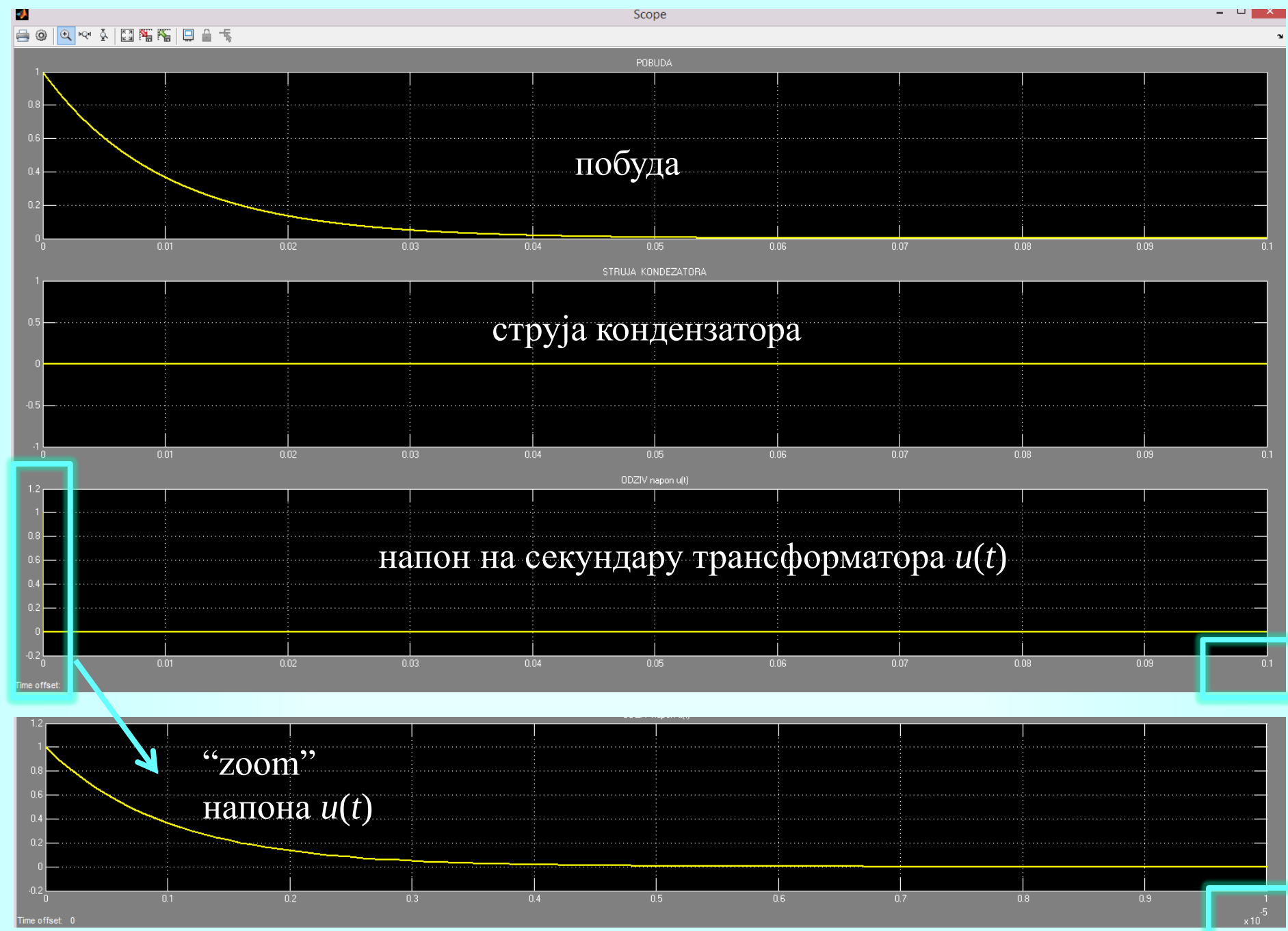

MATLAB: MuPAD

```
assume( R>0 and C>0 and L1>0 and L2>0 and L12>0 and L>0 and U>0 and a>0)
```

```
zamene := {L1=L, L2=L, L12=L}
```

```
{L1 = L, L2 = L, L12 = L}
```

```
pobuda:={ug=U*exp(-a*t)*heaviside(t)}
```

```
{ug = U e-a t heaviside(t)}
```

```
jednacine:={ug = uR + uL1,
```

```
uR = R*iR,
```

```
uL1 = L1*DiL1 + L12*DiL2,
```

```
u = L2*DiL2 + L12*DiL1,
```

```
uC = uL1 - u,
```

```
i = C*DuC,
```

```
iR = i + iL1,
```

```
i = iL2}
```

```
{u = DiL2 L2 + DiL1 L12, uL1 = DiL1 L1 + DiL2 L12, ug = uL1 + uR, i = iL2, uC = uL1 - u, i = C DuC, uR = R iR, iR = i + iL1}
```

```
promenljive := {uL1, u, uR, iR, i}
```

```
{i, iR, u, uL1, uR}
```

```
jednacineIzvoda:=groebner::eliminate(jednacine, promenljive)
```

```
[R iL1 - ug + R iL2 + DiL1 L1 + DiL2 L12, C DuC - iL2, uC - DiL1 L1 + DiL2 L2 + DiL1 L12 - DiL2 L12]
```

```
JednacineIzvodaZamene:=jednacineIzvoda | zamene
```

```
[R iL1 - ug + R iL2 + DiL1 L + DiL2 L, C DuC - iL2, uC]
```

```
PromenljiveStanjaIzvodi:={uC=uC(t), DuC=D(uC)(t), iL1=iL1(t), DiL1=D(iL1)(t), iL2=iL2(t), DiL2=D(iL2)(t)}
```

```
{iL1 = iL1(t), iL2 = iL2(t), uC = uC(t), DiL1 = iL1'(t), DiL2 = iL2'(t), DuC = uC'(t)}
```

JednacinPromenljiveStanja:=JednacinIzvodaZamene | PromenljiveStanjaIzvodi | {pobuda}

$$\left[L iL1'(t) + R iL1(t) + L iL2'(t) + R iL2(t) - U e^{-at} \text{heaviside}(t), C uC'(t) - iL2(t), uC(t) \right]$$

promenljiveStanja:=[iL1(t), iL2(t), uC(t)]

$$[iL1(t), iL2(t), uC(t)]$$

MATLAB: MuPAD

[noveJednacin, novePromenljive,
reseneJednacin,
konstantnePromenljive,
zamenjenePromenljive,
drugeJednacin

] := daetools::reduceRedundancies(JednacinPromenljiveStanja, promenljiveStanja)

$$\left[\left[e^{-at} \left(L e^{at} iL1'(t) + R e^{at} iL1(t) - U \text{heaviside}(t) \right) \right], [iL1(t)], [uC(t), -iL2(t)], [uC(t) = 0, iL2(t) = 0], [], [] \right]$$

noveJednacin

$$\left[e^{-at} \left(L e^{at} iL1'(t) + R e^{at} iL1(t) - U \text{heaviside}(t) \right) \right]$$

novePromenljive

$$[iL1(t)]$$

reseneJednacin

$$[uC(t), -iL2(t)]$$

konstantnePromenljive

$$[uC(t) = 0, iL2(t) = 0]$$

zamenjenePromenljive

$$[]$$

drugeJednacin

$$[]$$

noveJednacinePocetveVrednosti:={op(noveJednacine)), iL1(0)=0}

$$\left\{ e^{-a t} \left(L e^{a t} iL1'(t) + R e^{a t} iL1(t) - U \text{heaviside}(t) \right), iL1(0) = 0 \right\}$$

odziv := ode::solve(noveJednacinePocetveVrednosti, {iL1(t)})

$$\left\{ -e^{-\frac{R t}{L}} \left(\frac{U \text{heaviside}(t)}{R - L a} - \frac{U e^{\frac{R t}{L}} e^{-a t} \text{heaviside}(t)}{R - L a} \right) \right\}$$

iL1:=t--> op(odziv)

$$t \rightarrow -e^{-\frac{R t}{L}} \left(\frac{U \text{heaviside}(t)}{R - L a} - \frac{U e^{\frac{R t}{L}} e^{-a t} \text{heaviside}(t)}{R - L a} \right)$$

u(t):=L12*diff(iL1(t),t) | zamene

$$-L \left(\sigma_2 \left(\frac{U \delta(t)}{R - L a} - \frac{U \sigma_1 e^{-a t} \delta(t)}{R - L a} + \frac{U a \sigma_1 e^{-a t} \text{heaviside}(t)}{R - L a} - \frac{R U \sigma_1 e^{-a t} \text{heaviside}(t)}{L (R - L a)} \right) - \frac{R \sigma_2 \left(\frac{U \text{heaviside}(t)}{R - L a} - \frac{U \sigma_1 e^{-a t} \text{heaviside}(t)}{R - L a} \right)}{L} \right)$$

where

$$\sigma_1 = e^{\frac{R t}{L}}$$

$$\sigma_2 = e^{-\frac{R t}{L}}$$

MATLAB: MuPAD

$u:=t \rightarrow \text{Simplify}(u(t))$


MATLAB: MuPAD

$$t \rightarrow \frac{U \operatorname{heaviside}(t) \left(R e^{-\frac{R t}{L}} - L a e^{-a t} \right)}{R - L a}$$

$\text{vrednosti}:=\{R=1\text{e}3, C=1\text{e}-6, L=1\text{e}-3, U=1, a=100\}$

$\{R = 1000.0, U = 1, a = 100, C = 0.000001, L = 0.001\}$

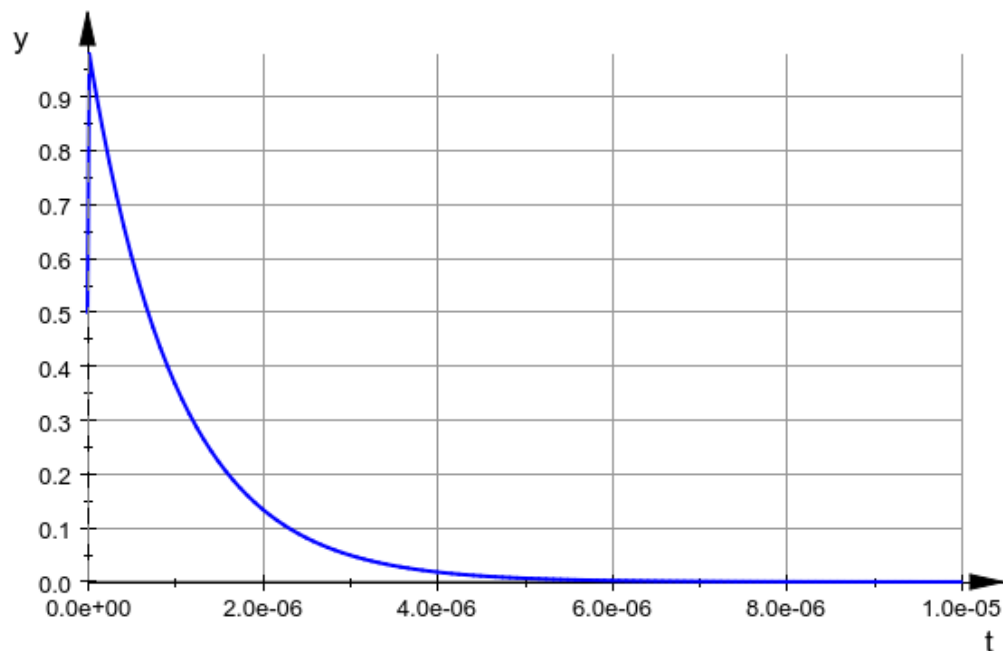$\text{plot}(u(t) \mid \text{vrednosti}, t=0..1\text{e}-5, \text{GridVisible} = \text{TRUE})$



$\text{limit}(u(t) \mid \text{vrednosti}, t = 0, \text{Right})$



1.0

$\text{limit}(u(t) \mid \text{vrednosti}, t = 0, \text{Left})$

0

Гранична вредност за
напон $u(t)$ кад $t \rightarrow 0$

Одзив на сложену побуду

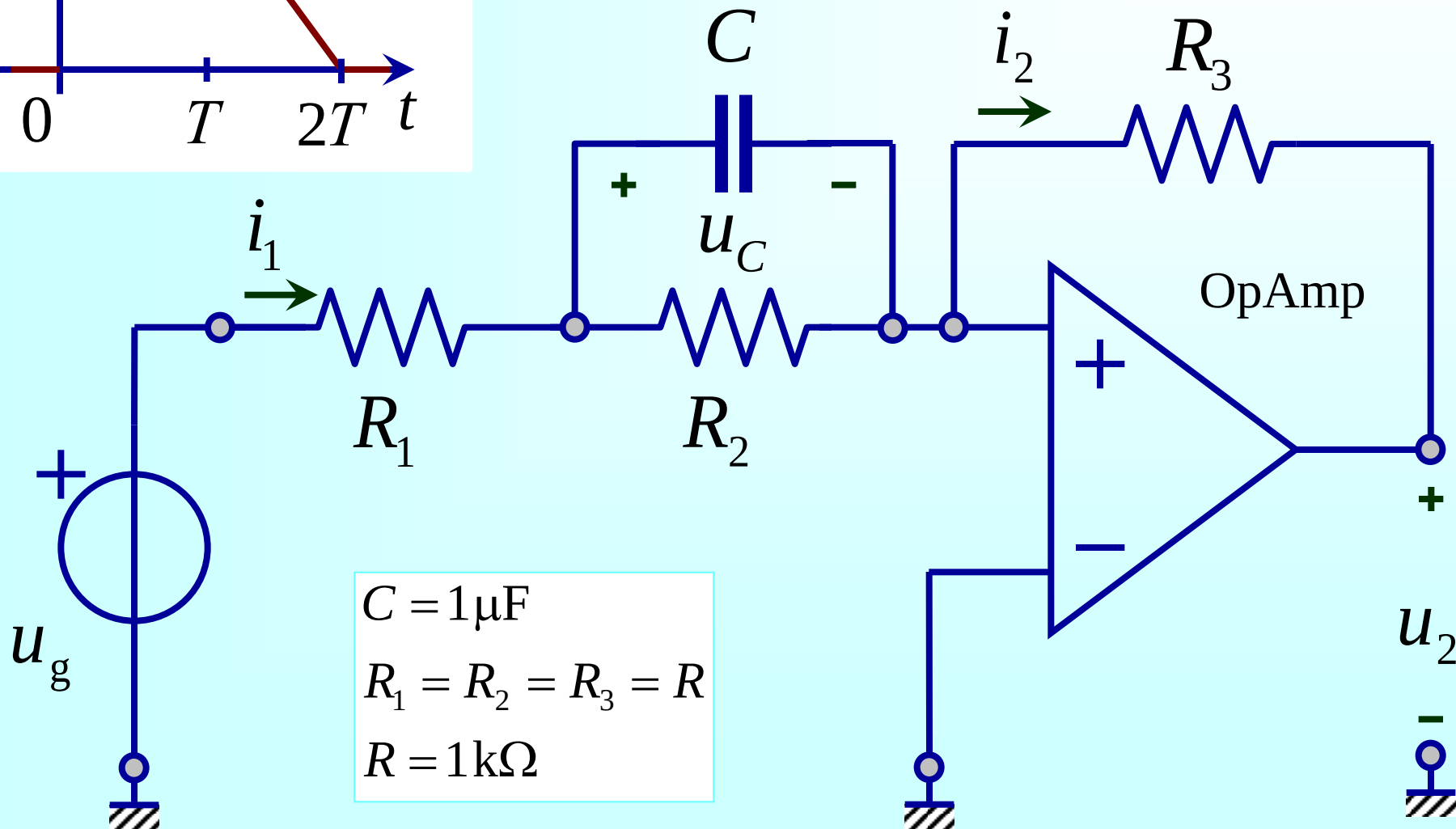
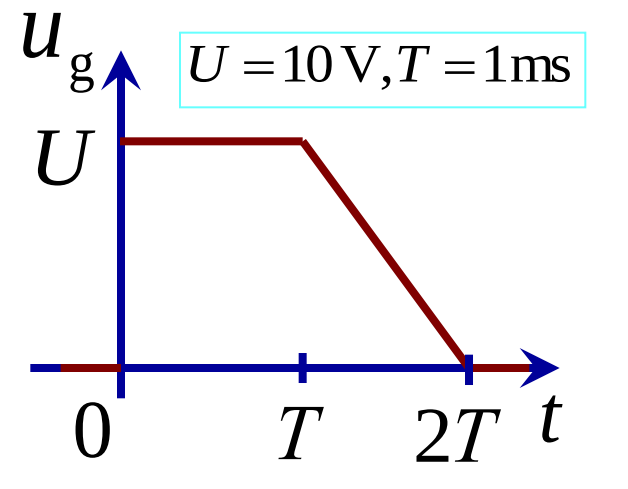




Задатак - сложена побуда

- Параметри кола са слике су познати:
 $R_1 = R_2 = R_3 = R$. Нема сакупљене енергије.
- Применом конволуционог интеграла одредити напон кондензатора $u_C(t)$, а затим и излазни напон $u_2(t)$ и нацртати његов график.
- Напон генератора се мења са временом као на диаграму, при чему је $T = RC$.

MATLAB: Simulink

Sources

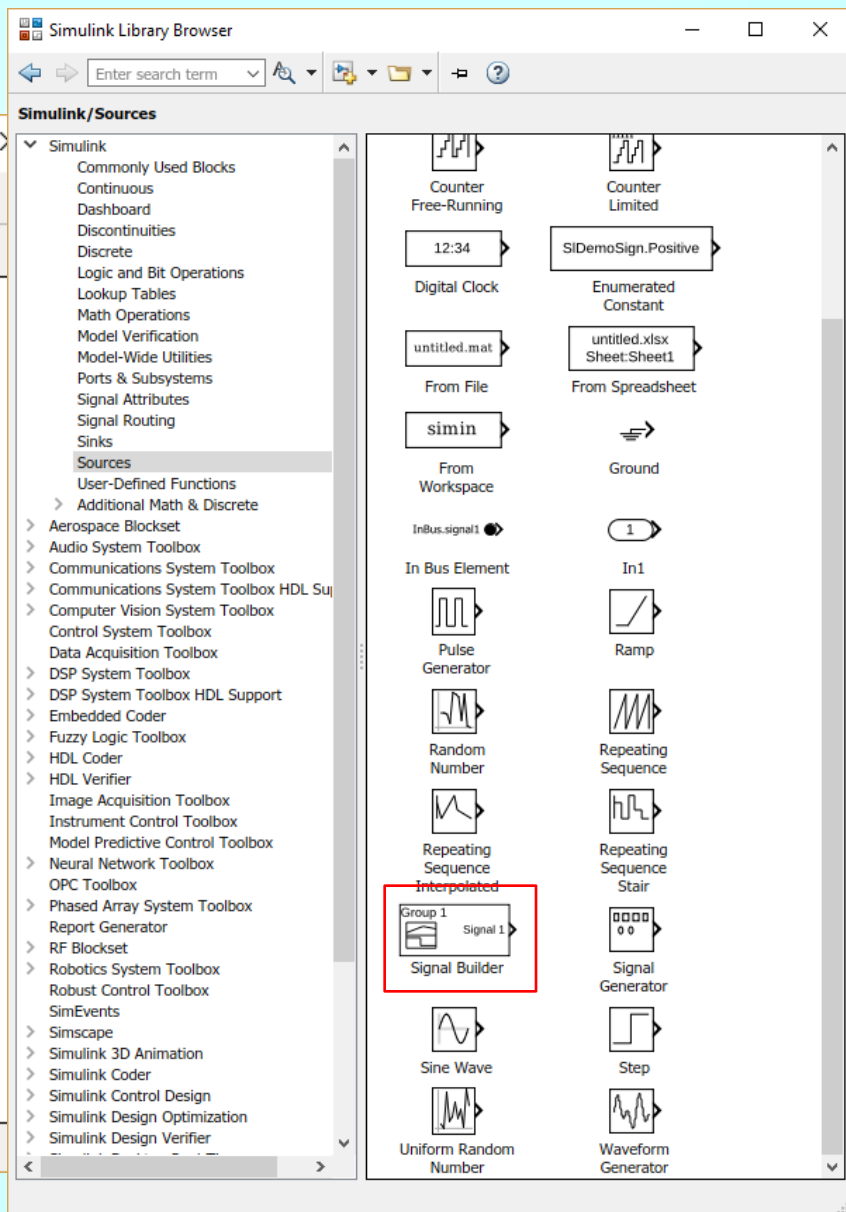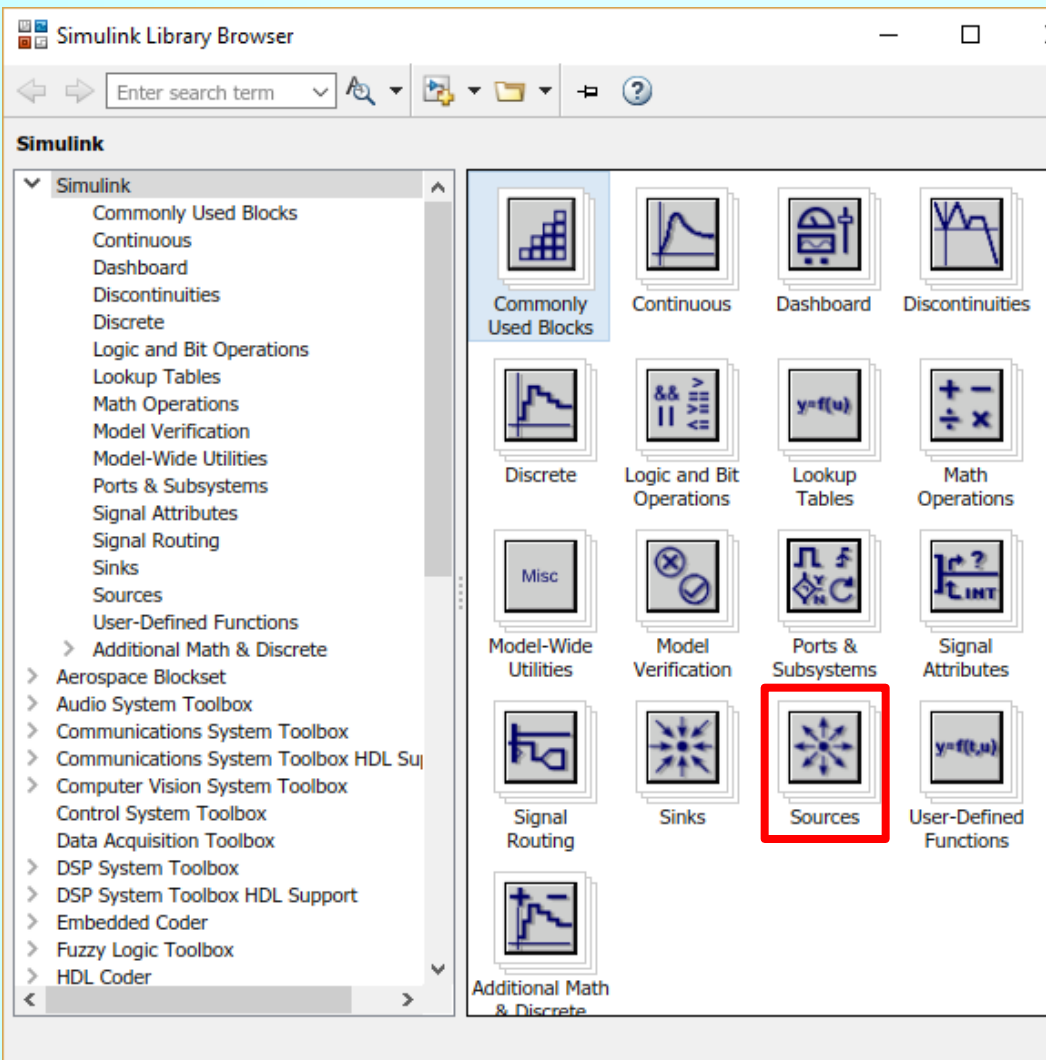


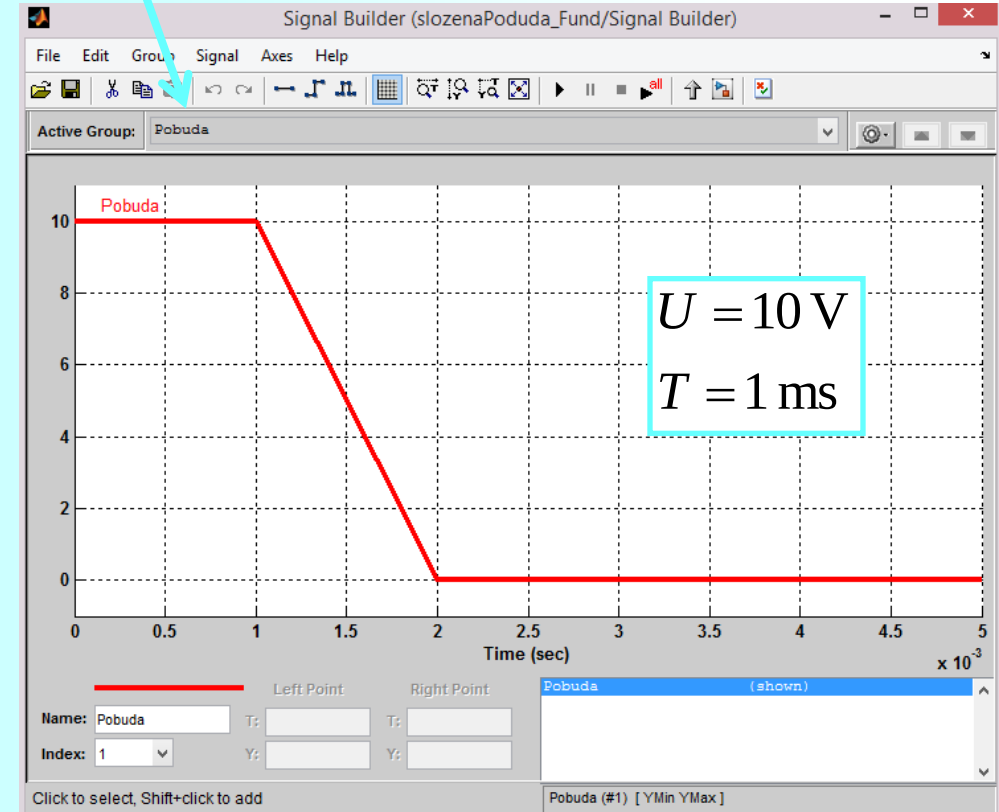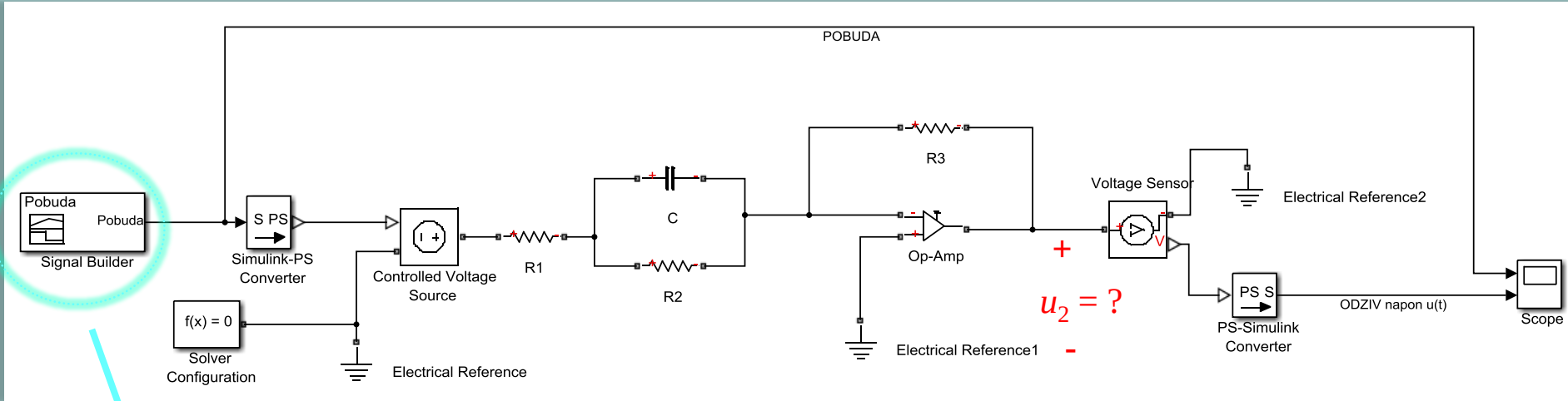

$$u_2 = ?$$

$$R_1 = R_2 = R_3 = 1\text{ k}\Omega$$
$$C_1 = 1\text{ }\mu\text{F}$$

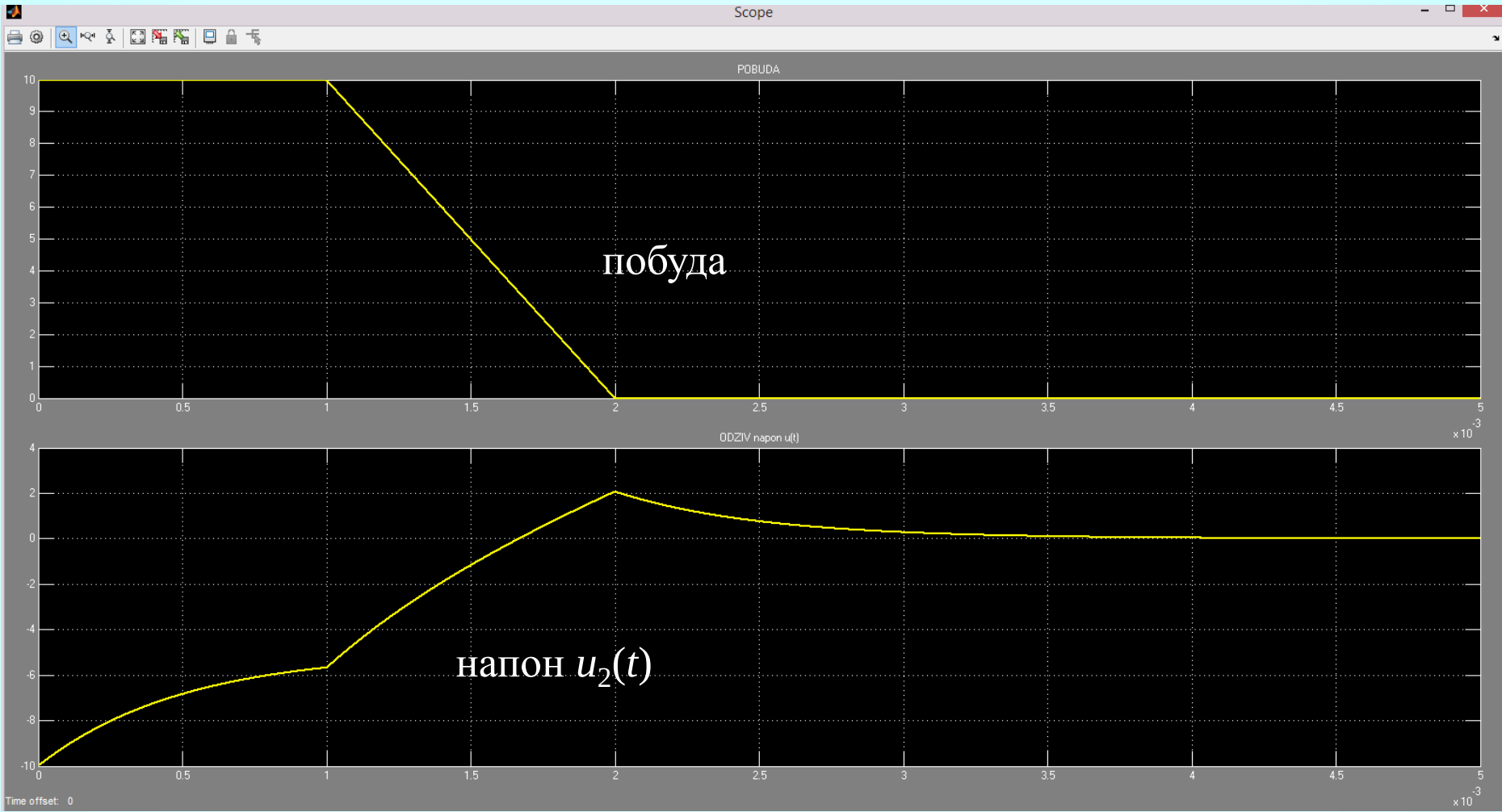MATLAB: Simscape
Foundation Library
Utilities
Simulink



MATLAB: MuPAD

```
assume( R1>0 and R2>0 and R3>0 and R>0 and C>0 and U>0 and T>0)
```

```
jednacine:={ug = uR1 + uC,  
uR1=R1*i1,  
iC=C*DuC,  
uR2=R2*iR2,  
uR2=uC,  
i1 = iR2+iC,  
i2=i1,  
u=-R3*i2}
```

```
{ug = uC + uR1, i2 = i1, uR2 = uC, iC = C DuC, u = - R3 i2, uR1 = R1 i1, uR2 = R2 iR2, i1 = iC + iR2}
```

```
jednacineIzvoda:=groebner::eliminate(jednacine,{ i1, iC, uR1, iR2, uR2, i2, u})
```

```
[R1 uC + R2 uC - R2 ug + C DuC R1 R2]
```

```
jednacineStanje := solve(jednacineIzvoda, {DuC})
```

```

$$\left\{ \left[ DuC = - \frac{R1 uC + R2 uC - R2 ug}{C R1 R2} \right] \right\}$$

```

```
PromenljiveStanjaIzvodi:={uC=uC(t), DuC=D(uC)(t)}
```

```
{uC = uC(t), DuC = uC'(t)}
```

```
zamene := {R1=R, R2=R, R3=R, T=R*C}
```

```
{R1 = R, R2 = R, R3 = R, T = C R}
```

MATLAB: MuPAD

pobuda := {ug=heaviside(t)}

{ug = heaviside(t)}

JS:=jednacineStanje | PromenljiveStanjaIzvodi | {pobuda, zamene}

$$\left\{ \left[u_C'(t) = \frac{R \text{heaviside}(t) - 2 R u_C(t)}{C R^2} \right] \right\}$$

JSpocetveVrednosti:={op(op(JS)), uC(0)=0}

$$\left\{ u_C'(t) = \frac{R \text{heaviside}(t) - 2 R u_C(t)}{C R^2}, u_C(0) = 0 \right\}$$

odziv := ode::solve(JSpocetveVrednosti, {uC(t)})

$$\left\{ \frac{e^{-\frac{2t}{CR}} \text{heaviside}(t) \left(e^{\frac{2t}{CR}} - 1 \right)}{2} \right\}$$

f_uC(t):=(op(odziv))

Индициона функција за $u_C(t)$

$$\frac{e^{-\frac{2t}{CR}} \text{heaviside}(t) \left(e^{\frac{2t}{CR}} - 1 \right)}{2}$$

Импулсни одзив за $u_C(t)$

g_uC:=t --> simplify(diff(f_uC(t),t))

$$t \rightarrow \frac{e^{-\frac{2t}{CR}} \text{heaviside}(t)}{C R}$$

ug_1:=t -> U

$$t \rightarrow U$$

ug_2:= t-> -U*(t-2*T)/T

$$t \rightarrow -\frac{U (t - 2 T)}{T}$$

ug_3:= t-> 0

$$t \rightarrow 0$$

$$0 < t \leq T$$

assume(0 < t <= T and T > 0): uC_1(t):=int(ug_1(Tau) * g_uC(t-Tau), Tau=0..t)

$$- \frac{U \left(e^{-\frac{2t}{CR}} - 1 \right)}{2}$$

Конволуциони интеграл
за напон $u_C(t)$ за $0 < t \leq T$



i1_1(t):=(1/R)*(ug_1(t)-uC_1(t))|zamene:

i2_1(t):=i1_1(t):

u2_1(t):=-R*i2_1(t)

$$-U - \frac{U \left(e^{-\frac{2t}{CR}} - 1 \right)}{2}$$

Simplify(u2_1(t))

$$- \frac{U \left(e^{-\frac{2t}{CR}} + 1 \right)}{2}$$

напон $u_2(t)$ за $0 < t \leq T$

MATLAB: MuPAD

assume(2*T >= t > T and T>0):

uC_2(t):=int(ug_1(Tau) * g_uC(t-Tau), Tau=0..T) + int(ug_2(Tau) * g_uC(t-Tau), Tau=T..t)

$$\frac{U e^{-\frac{2t}{CR}} \left(e^{\frac{2T}{CR}} - 1 \right)}{2} - U \left(e^{\frac{2(T-t)}{CR}} - 1 \right) - \frac{U \left(\frac{CR(2t-CR)}{4} - \frac{CR e^{\frac{2T-2t}{CR}} (2T-CR)}{4} \right)}{CRT}$$

Simplify(uC_2(t)|zamene)

$$\frac{5U}{4} - \frac{U e^{-\frac{2t}{CR}}}{2} - \frac{U e^2 e^{-\frac{2t}{CR}}}{4} - \frac{Ut}{2CR}$$

Конволуциони интеграл
за напон $u_C(t)$ за $T < t \leq 2T$

i1_2(t):=(1/R)*(ug_2(t) - uC_2(t))|zamene:

i2_2(t):=i1_2(t):

u2_2(t):=-R*i2_2(t)

$T < t \leq 2T$

$$\frac{U e^{-\frac{2t}{CR}} (e^2 - 1)}{2} - U \left(e^{-\frac{2(t-CR)}{CR}} - 1 \right) - \frac{U \left(\frac{CR(2t-CR)}{4} - \frac{C^2 R^2 e^{-\frac{2t-2CR}{CR}}}{4} \right)}{C^2 R^2} + \frac{U(t-2CR)}{CR}$$

Simplify(u2_2(t))

$$\frac{Ut}{2CR} - \frac{U e^{-\frac{2t}{CR}}}{2} - \frac{U e^2 e^{-\frac{2t}{CR}}}{4} - \frac{3U}{4}$$

напон $u_2(t)$ за $T < t \leq 2T$

MATLAB: MuPAD

assume(t > 2*T and T > 0):

uC_3(t):=int(ug_1(Tau) * g_uC(t-Tau), Tau=0..T)+int(ug_2(Tau) * g_uC(t-Tau), Tau=T..2*T)

$$\frac{U e^{-\frac{2t}{CR}} \left(e^{\frac{2T}{CR}} - 1 \right)}{2} - \frac{U e^{\frac{2T}{CR}} e^{-\frac{2t}{CR}} \left(2T + CR - CR e^{\frac{2T}{CR}} \right)}{4T}$$



Конволуциони интеграл
за напон $u_C(t)$ за $t > 2T$

Simplify(uC_3(t)|zamene)

$$\frac{U e^{-\frac{2t}{CR}} (e^2 + 1) (e^2 - 2)}{4}$$

$t > 2T$

i1_3(t):=(1/R)*(ug_3(t)-uC_3(t)) | zamene:

i2_3(t):=i1_3(t):

u2_3(t):=-R*i2_3(t)

$$\frac{U e^{-\frac{2t}{CR}} (e^2 - 1)}{2} - \frac{U e^2 e^{-\frac{2t}{CR}} (3CR - CR e^2)}{4CR}$$

Simplify(u2_3(t))

$$\frac{U e^{-\frac{2t}{CR}} (e^2 + 1) (e^2 - 2)}{4}$$

напон $u_2(t)$ за $t > 2T$

MATLAB: MuPAD

$\text{vrednosti} := \{R=1e3, C=1e-6, U=10, T=1e-3\}$


MATLAB: MuPAD

$\{R = 1000.0, U = 10, C = 0.000001, T = 0.001\}$

$u2(t) := \text{piecewise}([0 < t \leq T \mid \text{vrednosti}, u2_1(t)],$
 $[T < t \leq 2*T \mid \text{vrednosti}, u2_2(t)], [t > 2*T \mid \text{vrednosti}, u2_3(t)]) \mid \text{vrednosti}$

$$\begin{cases} 5 e^{-2000.0 t} (e^2 - 1) + 2500.0 e^2 e^{-2000.0 t} (0.001 e^2 - 0.003) & \text{if } 0.002 < t \\ -5 e^{-2000.0 t} - 5 & \text{if } t \leq 0.001 \\ 5000.0 t - 7.5 e^{2.0 - 2000.0 t} + 5 e^{-2000.0 t} (e^2 - 1) - 7.5 & \text{if } t \in (0.001, 0.002] \end{cases}$$

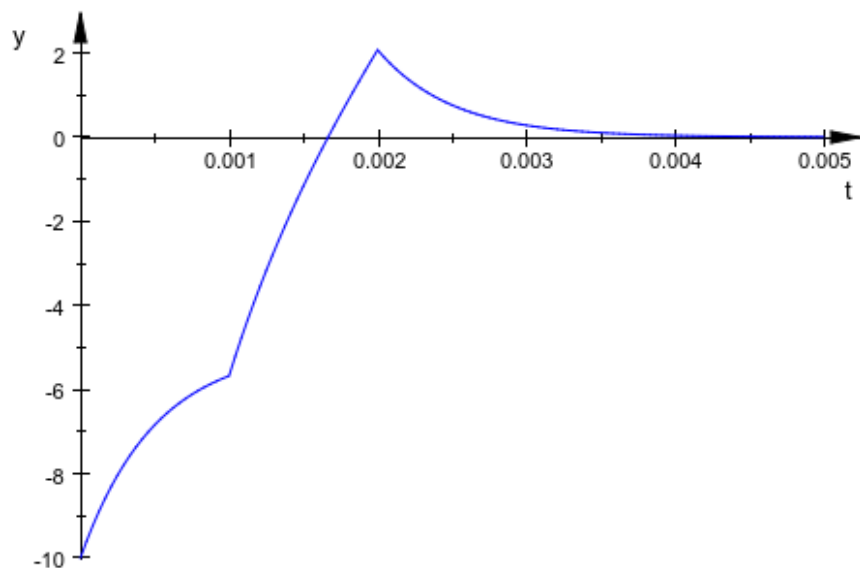$\text{plot}(u2(t) \mid \text{zamene}, \text{tx}=0..5e-3)$





Одзив на троугаони импулс

Параметри електричног кола са слике су познати. Побуда је дата на слици, $T = L/R$, $R_1 = R$, $R_2 = 2R$, $L_1 = L$, $L_2 = 4L$, $k = 1/2$.

(5) Одредити индициону функцију за напон отвореног секундара (одскочни одзив).

(5) Одредити напон отвореног секундара и

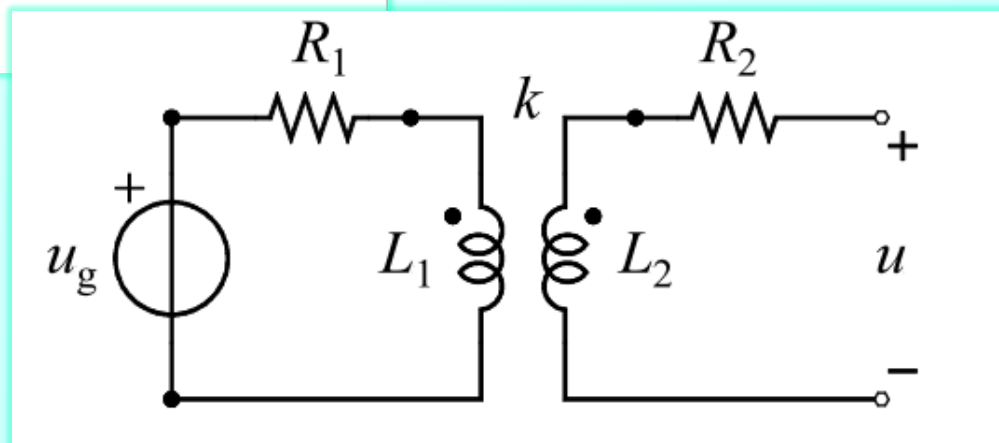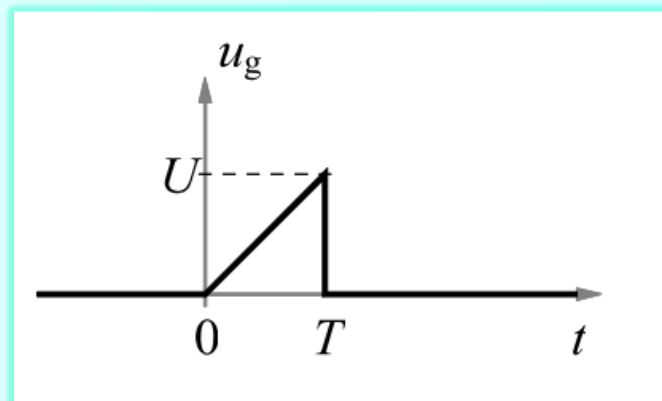(5) нацртати његов график. Обележити осе графика, координатни почетак, пресеке и додире графика са осама, и тачке екстремума.



```
assume( R1>0 and L1>0 and L2>0 and L12>0 and L>0 and U>0 and T>0 and t>=0)
zamene := {L1=L, L2=4*L, L12=(1/2)*sqrt(L*4*L), R1=R, R2=2*R, T=L/R}
{R1 = R, T = \frac{L}{R}, L2 = 4 L, R2 = 2 R, L1 = L, L12 = L}
```

```
jednacine:={ug = uR1 + u1,
u1 = L1 * Di1 ,
u2 = L12 * Di1,
uR1=R1*i1}
```

```
{ug = u1 + uR1, u1 = Di1 L1, u2 = Di1 L12, uR1 = R1 i1}
```

```
Jednacine:=jednacine | zamene
```

```
{ug = u1 + uR1, u1 = Di1 L, u2 = Di1 L, uR1 = R i1}
```

```
jednacineIzvoda:=groebner::eliminate(Jednacine,{u1, u2, uR1})
```

```
[R i1 - ug + Di1 L]
```

```
jednacineStanja := solve(jednacineIzvoda, {Di1})
```

```
{ \left[ Di1 = \frac{ug - R i1}{L} \right]}
```

```
PromenljiveStanjaIzvodi:={i1=i1(t), Di1=D(i1)(t)}
```

```
{i1 = i1(t), Di1 = i1'(t)}
```

MATLAB: MuPAD

pobuda := {ug=heaviside(t)}

{ug = heaviside(t)}

JS:=jednacineStanja | PromenljiveStanjaIzvodi | pobuda

$$\left\{ \left[i_1'(t) = \frac{\text{heaviside}(t) - R i_1(t)}{L} \right] \right\}$$

op(op(JS))

$$i_1'(t) = \frac{\text{heaviside}(t) - R i_1(t)}{L}$$

JSpocetveVrednosti:={op(op(JS)), i1(0)=0}

$$\left\{ i_1'(t) = \frac{\text{heaviside}(t) - R i_1(t)}{L}, i_1(0) = 0 \right\}$$

odziv := ode::solve(JSpocetveVrednosti, {i1(t)})

$$\left\{ \frac{e^{-\frac{Rt}{L}} \text{heaviside}(t) \left(e^{\frac{Rt}{L}} - 1 \right)}{R} \right\}$$

f_i1(t):=(op(odziv))

Индициона функција за струју $i_1(t)$

$$\frac{e^{-\frac{Rt}{L}} \text{heaviside}(t) \left(e^{\frac{Rt}{L}} - 1 \right)}{R}$$

MATLAB: MuPAD

`g_i1:=t --> simplify((diff(f_i1(t),t)))`

Импулсни одзив за струју $i_1(t)$

$$t \rightarrow \frac{e^{-\frac{Rt}{L}} \text{heaviside}(t)}{L}$$

`assume(0<t<=T):i1_1(t):=int((U*Tau/T)*g_i1(t-Tau), Tau=0..t)`

$$\frac{U \left(R t - L + L e^{-\frac{Rt}{L}} \right)}{R^2 T}$$

Конволуциони интеграл
за струју $i_1(t)$ за $0 < t \leq T$

`u2_1(t):=simplify(L12*diff(i1_1(t),t)|zamene)`

$$U - U e^{-\frac{Rt}{L}}$$

напон $u_2(t)$ за $0 < t \leq T$

`assume(t>T): i1_2(t):=int((U*Tau/T)*g_i1(t-Tau), Tau=0..T)`

$$\frac{L U e^{-\frac{Rt}{L}}}{R^2 T} - \frac{U e^{\frac{RT-Rt}{L}} (L - R T)}{R^2 T}$$

Конволуциони интеграл
за струју $i_1(t)$ за $t > T$

`u2_2(t):=simplify(L12*diff(i1_2(t),t)|zamene)`

$$- U e^{-\frac{Rt}{L}}$$

напон $u_2(t)$ за $t > T$

MATLAB: MuPAD

```
vrednosti:={R=1000, L=1e-3, T=1e-6, U=10}
```


```
{R = 1000, U = 10, L = 0.001, T = 0.000001}
```

```
u2(t) := piecewise([0 < t <= T|vrednosti, u2_1(t)], [t > T|vrednosti, u2_2(t)])|vrednosti
```

$$\begin{cases} -10 e^{-1000000.0 t} & \text{if } 0.000001 < t \\ 10 - 10 e^{-1000000.0 t} & \text{if } t \in (0, 0.000001] \end{cases}$$

напон $u_2(t)$ за $t > 0$
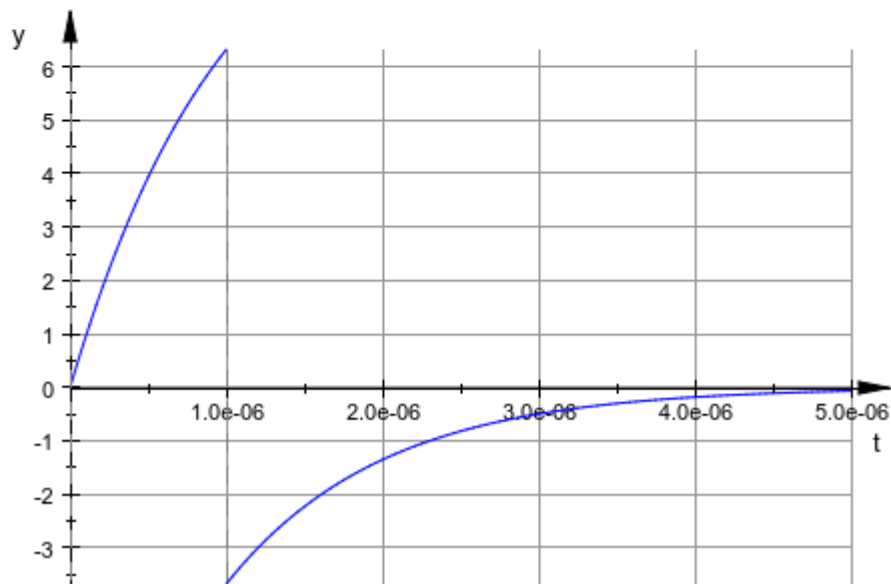
```
plot(u2(t), t=0..5e-6, GridVisible = TRUE)
```



```
limit(u2(t), t = 1e-6, Left)
```

```
6.321205588
```



```
limit(u2(t), t = 1e-6, Right)
```

```
-3.678794412
```


Гранична вредност за
напон $u_2(t)$ кад $t \rightarrow T = 1 \mu\text{s}$





MATLAB: Simulink


Sources

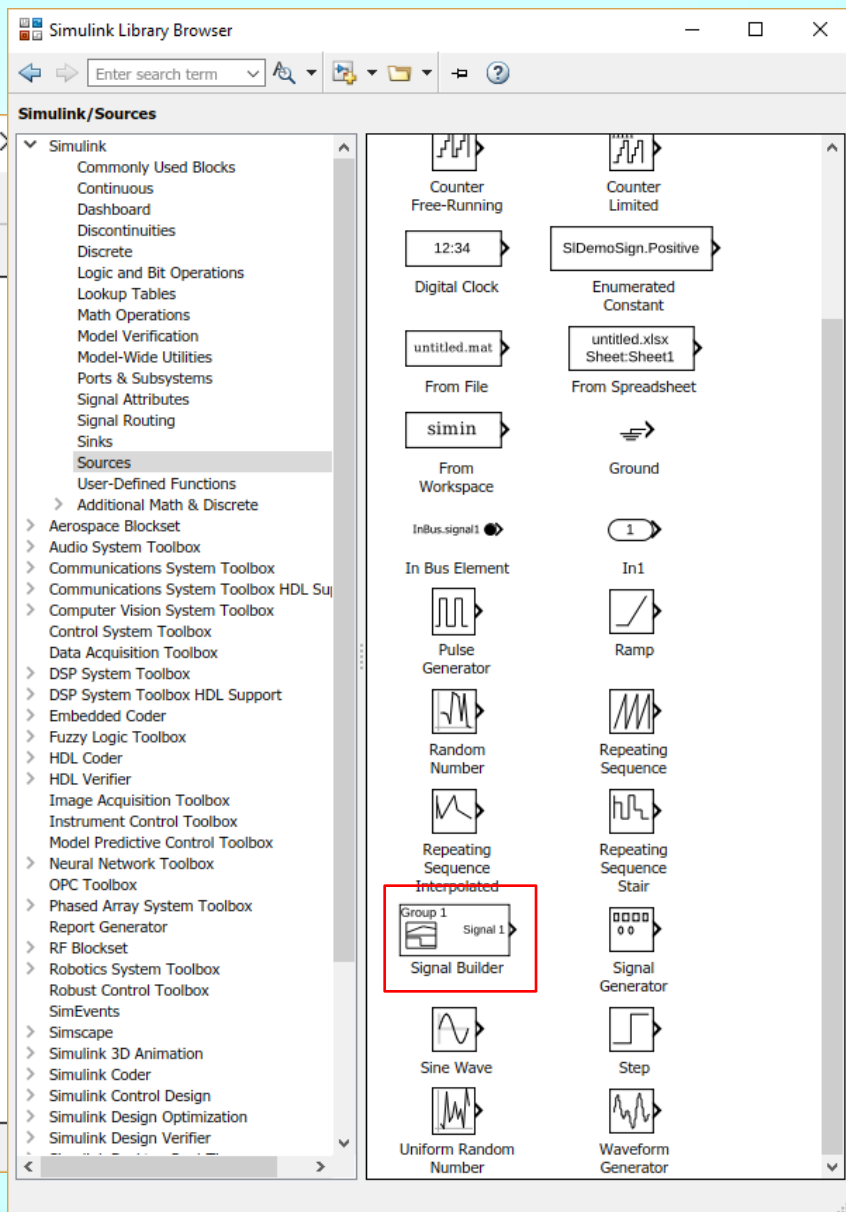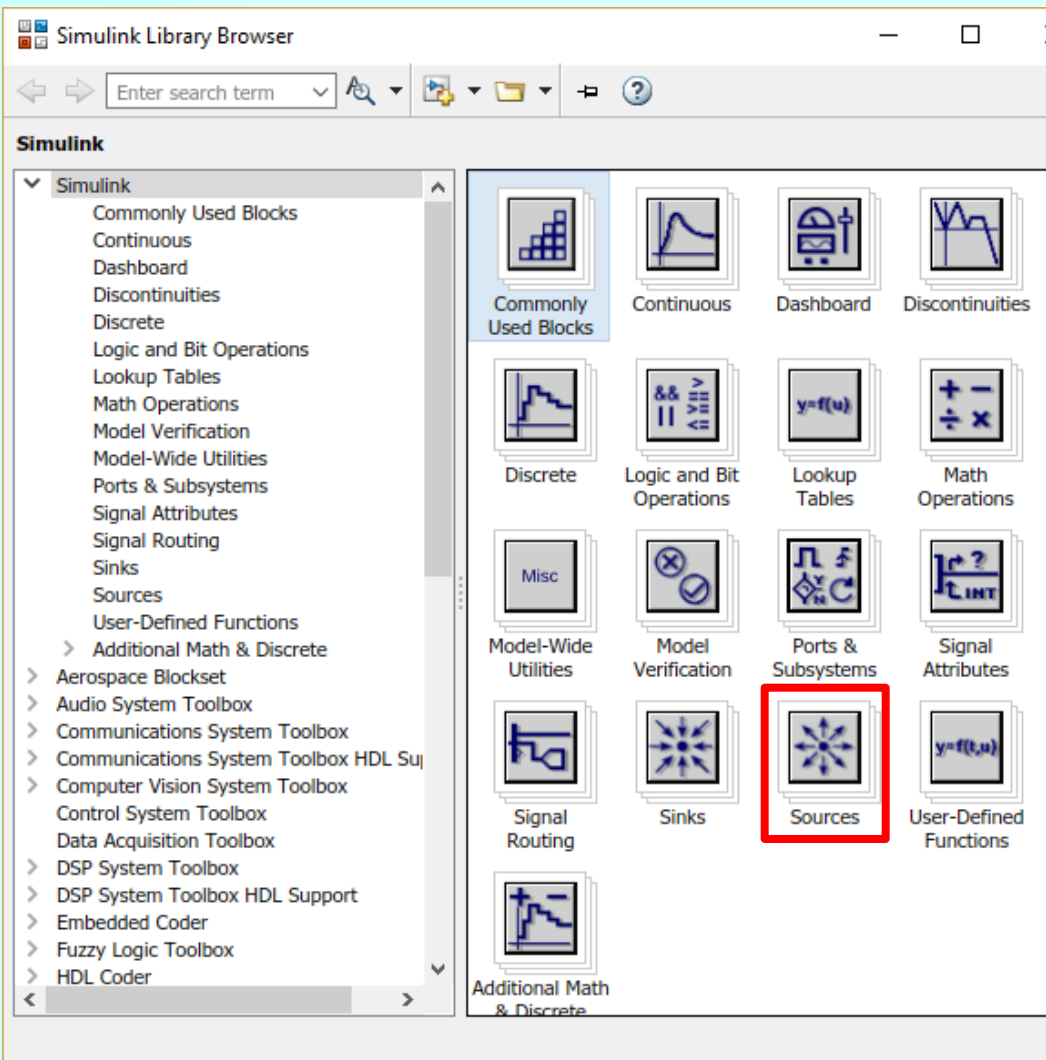

Signal Builder

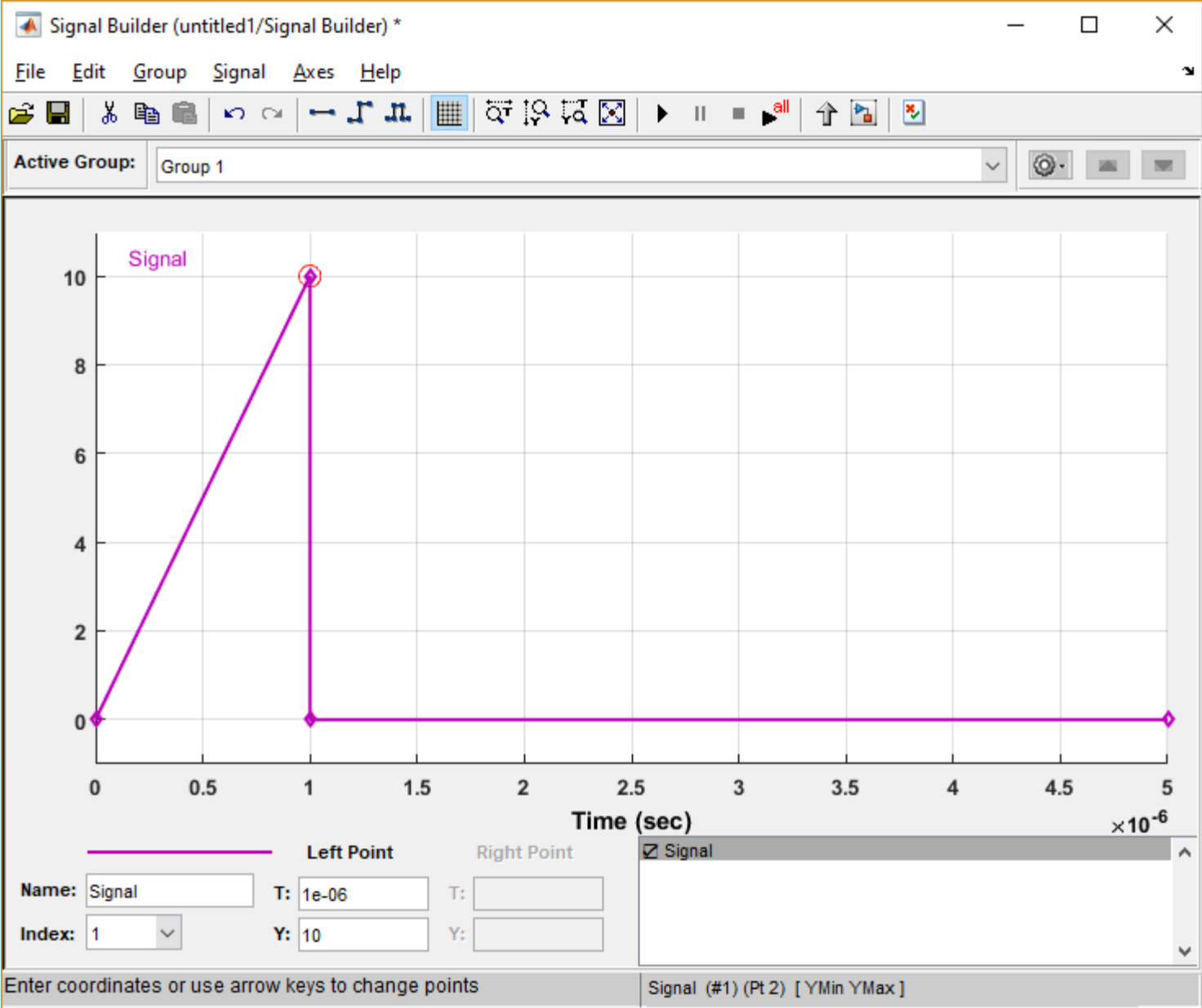

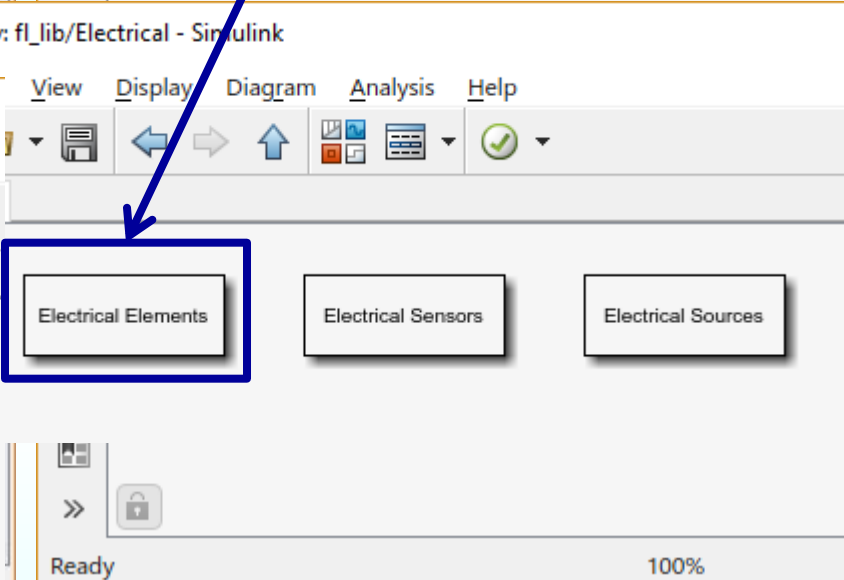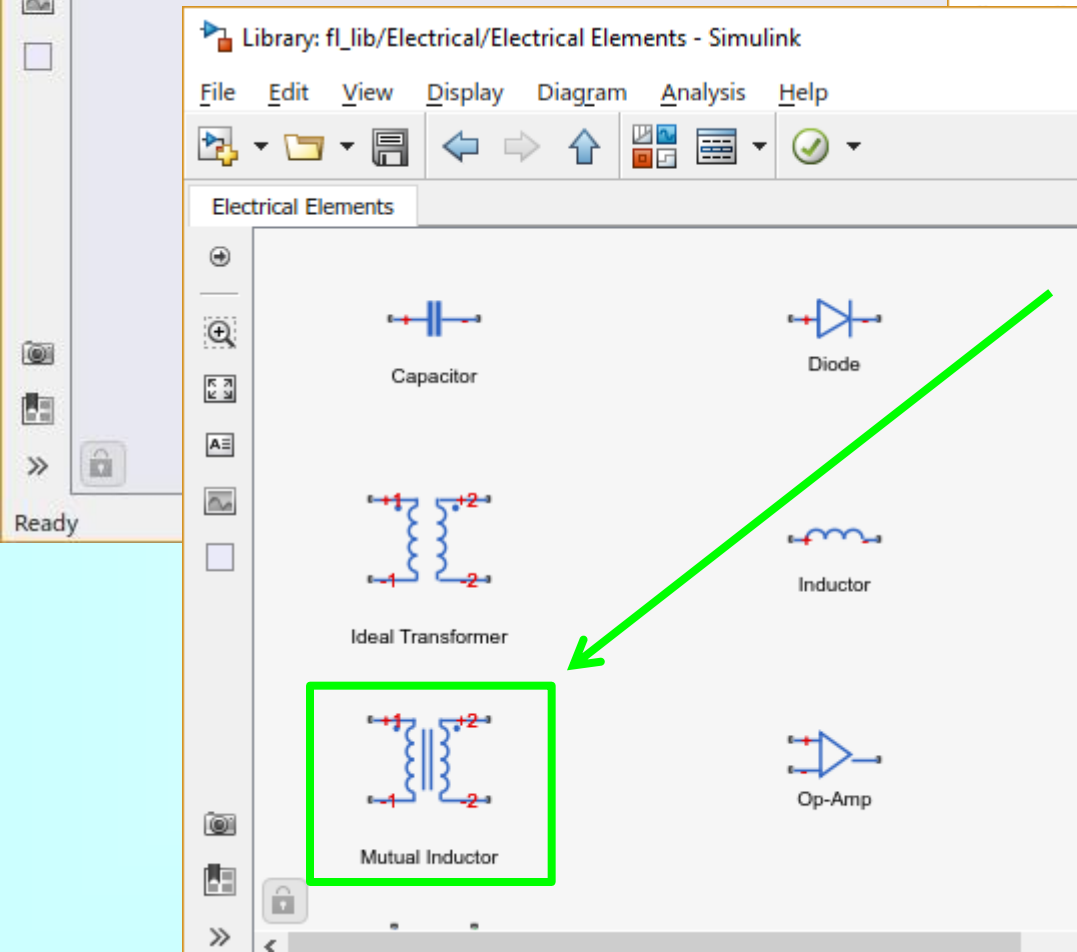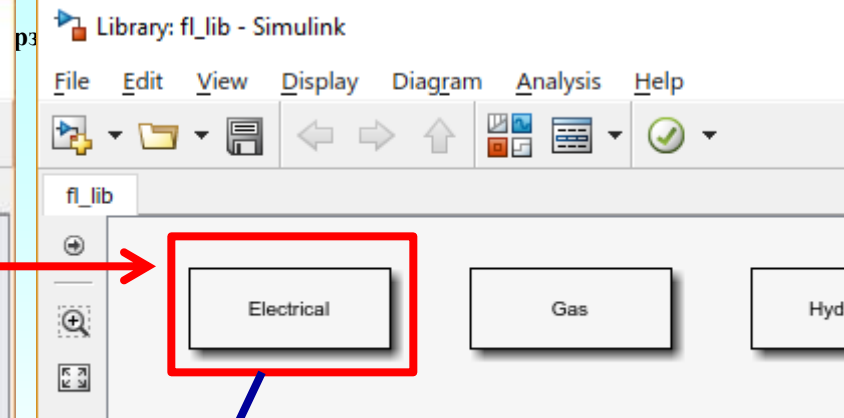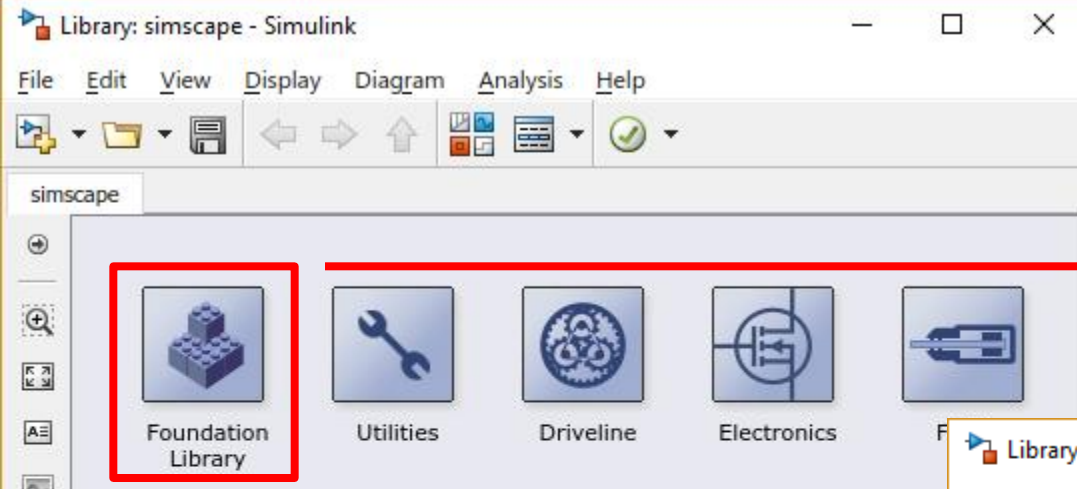

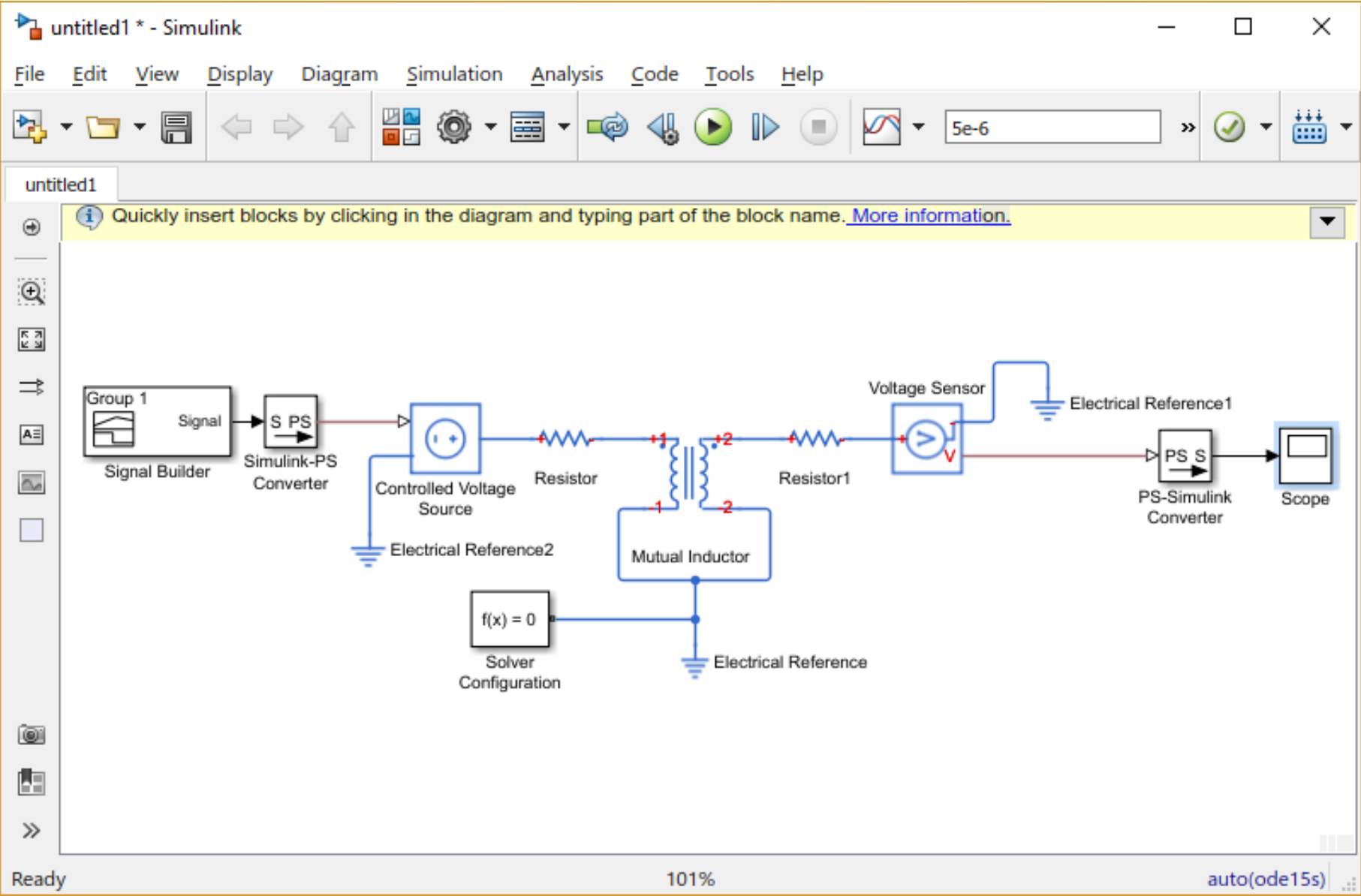

Block Parameters: Mutual Inductor

Mutual Inductor

Models a mutual inductor. If winding 1 has voltage V1 across it and current I1 flowing into its + terminal, and winding 2 has voltage V2 across it and current I2 flowing into its + terminal, then

$$V1 = L1 \cdot dI1/dt + M \cdot dI2/dt$$

$$V2 = L2 \cdot dI2/dt + M \cdot dI1/dt$$

where parameters L1 and L2 are the winding self-inductances, and M is the mutual inductance. M is defined in terms of the Coefficient of coupling k by $M = k \cdot \sqrt{L1 \cdot L2}$. Hence k should be greater than zero and less than one.

[Source code](#)

Settings

Parameters Variables

Inductance L1:	1	mH
Inductance L2:	4	mH
Coefficient of coupling:	0.5	

Block Parameters: Resistor

Resistor

The voltage-current (V-I) relationship for a linear resistor is $V = I \cdot R$, where R is the constant resistance in ohms.

The positive and negative terminals of the resistor are denoted by the + and - signs respectively. By convention, the voltage across the resistor is given by $V(+)-V(-)$, and the sign of the current is positive when flowing through the device from the positive to the negative terminal. This convention ensures that the power absorbed by a resistor is always positive.

[Source code](#)

Settings

Parameters Variables

Resistance:	1	kOhm
-------------	--------------------------------	-----------------------------------

Block Parameters: Resistor1

Resistor

The voltage-current (V-I) relationship

The positive and negative terminals of the voltage across the resistor is given the device from the positive to the neg resistor is always positive.

[Source code](#)

Settings

Parameters Variables


Resistance:	2	kOhm
-------------	--------------------------------	-----------------------------------



Scope



File Tools View Simulation Help

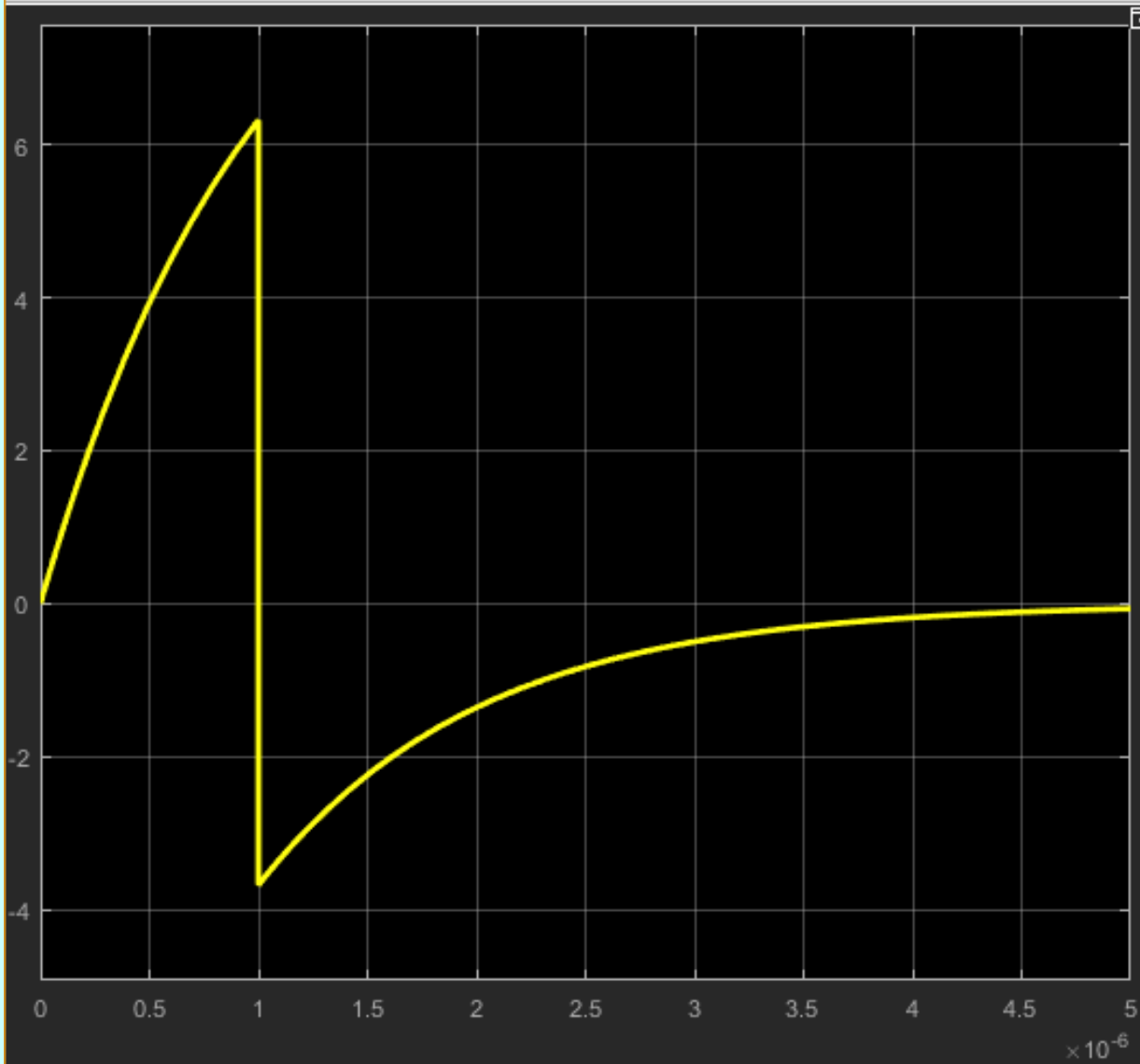

Signal Statistics		
	Value	Time
Max	6.321e+00	1.000e-06
Min	-3.679e+00	1.000e-06
Peak to Peak	1.000e+01	
Mean	-1.700e-03	
Median	-2.586e-01	
RMS	2.367e+00	

Ready

Sample based T=5e-06